

**Nanyang Technological University**  
**School of Electrical & Electronic Engineering**  
**EE2002 Analog Electronics – Tutorial 12**

1. In the common-base circuit shown in Figure 1, the transistor has  $\beta = 100$ ,  $V_A = \infty$ ,  $C_\mu = 1\text{pF}$  and  $f_T = 285\text{ MHz}$ . Assume  $V_T = 25\text{ mV}$ . Using open-circuit time constant method, determine the upper 3-dB frequency of the amplifier.

(Ans: 813 Mrad/s)

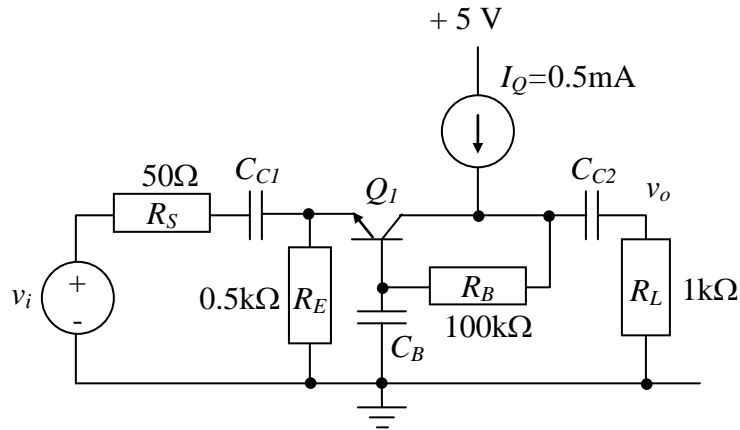


Figure 1

2. Using the open-circuit short-circuit time constant method, determine the lower -3dB frequency ( $\omega_L$ ) for the amplifier circuit shown in Figure 2. Assume that a signal source  $v_s$  with a series resistance  $R_S = 1\text{ M}\Omega$  is connected to the input at G through a coupling capacitor  $C_1 = 1\mu\text{F}$ , while a load resistor  $R_L = 10\text{ k}\Omega$  is connected to the output at D through a coupling capacitor  $C_2 = 1\mu\text{F}$ . The resistance  $R_I = 5\text{ M}\Omega$ . For the transistors  $Q_1$  and  $Q_2$ ,  $\mu_n C_{ox1}(W_1/L_1) = \mu_p C_{ox2}(W_2/L_2) = 50\text{ }\mu\text{A/V}^2$ ,  $|V_{TP}| = V_{TN} = 2\text{V}$ , and  $\lambda = 0.005\text{ V}^{-1}$ .

Ans: 34.9 rad/s

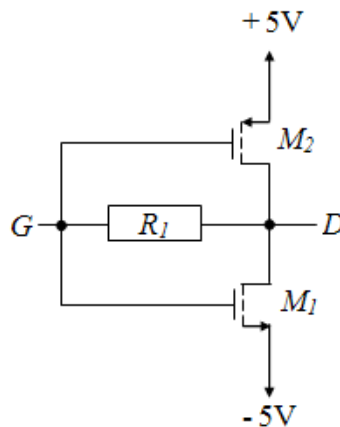


Figure 2