

Nanyang Technological University
School of Electrical & Electronic Engineering
EE2002 Analog Electronics – Tutorial 09

1. (a) Let the drain currents of the 2 transistors in Figure 1a be I_{D1} and I_{D2} respectively. Find the ratio I_{D2}/I_{D1} for the ideal case where (i) $\lambda = 0$ and the non-ideal case (ii) $\lambda = 0.015 \text{ V}^{-1}$ respectively. Does this ratio depend on the magnitude of V_{GS} ? Do the absolute values of I_{D1} and I_{D2} depend on V_{GS} ?
 (Ans: (i) $I_{D2}/I_{D1} = 2$ (ii) $I_{D2}/I_{D1} = 1.947$. The ratio is independent of V_{GS} but absolute values depend on V_{GS} .)

- (b) Figure 1b shows a current mirror where the V_{GS} in the earlier picture is generated by a diode connected transistor M_0 that is identical to M_1 . Derive the algebraic expression for the ratio I_{D1}/I_{D0} for the ideal case where (i) $\lambda = 0$ and the non-ideal case (ii) $\lambda = 0.015 \text{ V}^{-1}$ respectively.
 (Ans: (i) $I_{D1}/I_{D0} = 1$ (ii) $I_{D1}/I_{D0} = 1.15/(1 + 0.015 \cdot V_{GS})$)

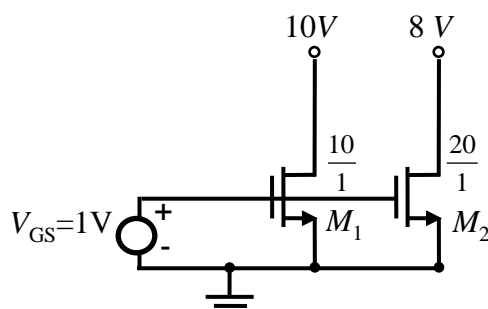


Figure 1a

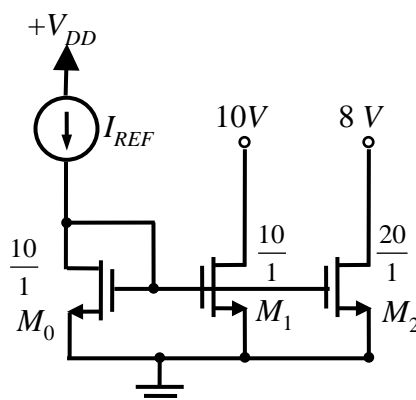


Figure 1b

2. What are the output currents and output resistances for the current sources in Figure 2, if $I_{REF} = 30 \mu\text{A}$, $K'_n = 25 \mu\text{A}/\text{V}^2$, $V_{TN} = 0.75 \text{ V}$ and $\lambda = 0.015 \text{ V}^{-1}$?
 (Ans: $84.3 \mu\text{A}$, $909 \text{ k}\Omega$; $164 \mu\text{A}$, $455 \text{ k}\Omega$; $346 \mu\text{A}$, $227 \text{ k}\Omega$)

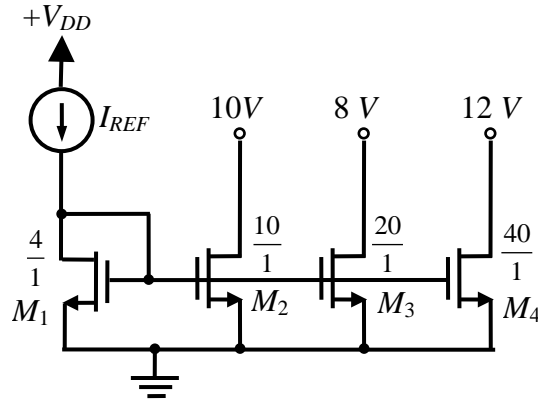


Figure 2

3. (a) What is the reference current I_o in Figure 3(a) if $R=43\text{ k}\Omega$ and $V_{EE}=5\text{V}$? What is the current if $V_{EE}=7.5\text{V}$? Assume $V_{BE}=0.7\text{V}$, base currents are negligible and both transistors are identical.
- (b) What is the reference current I_o in Figure 3(b) if $K_n=K_p=400\text{ }\mu\text{A/V}^2$, $V_{TN}=-V_{TP}=1\text{ V}$, $V_{DD}=0\text{V}$ and $V_{ss}=5\text{V}$? What is the current when $V_{ss}=7.5\text{V}$? Assume all NMOS transistors are identical.
- (Ans: (a) $100\text{ }\mu\text{A}$, $158\text{ }\mu\text{A}$ (b) $88.9\text{ }\mu\text{A}$, $450\text{ }\mu\text{A}$)

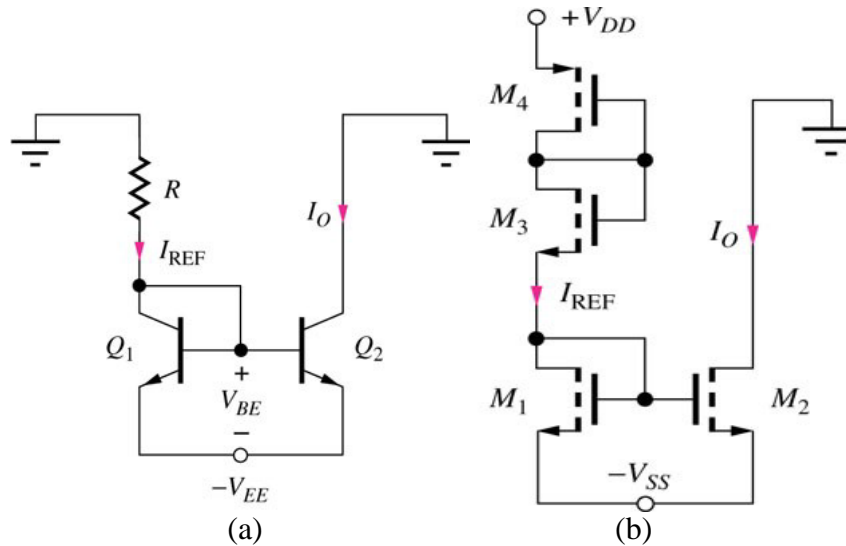


Figure 3