

Nanyang Technological University
School of Electrical & Electronic Engineering
EE2002 Analog Electronics – Tutorial 10

- What are the output currents and output resistances for the current sources in Figure 1, if $I_{REF} = 100 \mu A$, $\beta = 50$ and $V_A = 50 V$?
 (Ans: $216.57 \mu A$, $277 k\Omega$; $418.7 \mu A$, $138.5 k\Omega$; $895.1 \mu A$, $69.2 k\Omega$)

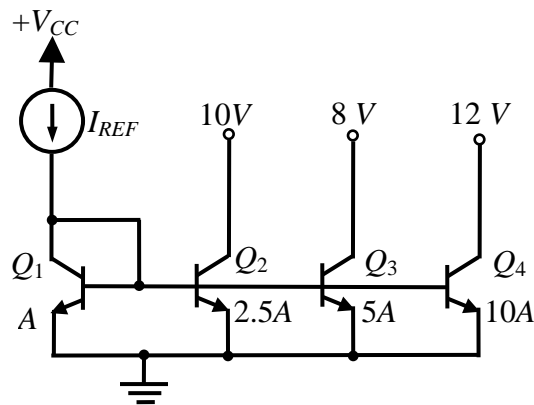


Figure 1

- Find the output current in the current source of Figure 2 if $A_{E3} = 10A_{E4}$, $A_{E2} = 10A_{E1}$ and $R = 1 k\Omega$. Here A_{EX} refers to the emitter area of transistor QX. Assume infinite current gain of the transistors ($\beta \rightarrow \infty$) and ignore Early effect.
 (Ans: $115 \mu A$)

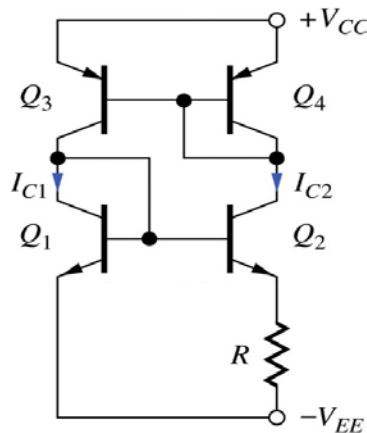


Figure 2