

$$\begin{aligned}
 I_{REF} &= I_{C1} + \frac{1}{50(1+\frac{0.7}{50})} I_{C1} + \frac{2.5}{1(1+\frac{0.7}{50})(50)} I_{C1} + \frac{5}{1(1+\frac{0.7}{50})(50)} I_{C1} + \frac{10}{1(1+\frac{0.7}{50})(50)} I_{C1} \\
 &= I_{C1} + \frac{10}{507} I_{C1} + \frac{25}{507} I_{C1} + \frac{50}{507} I_{C1} + \frac{100}{507} I_{C1} \\
 &= 1.364891519 I_{C1}
 \end{aligned}$$

$$\begin{aligned}
 I_{C1} &= \frac{I_{REF}}{1.364891519} \\
 &= \frac{100 \mu A}{1.364891519} \\
 &= 73.26589595 \times 10^{-6} A \\
 &\approx 73.3 \mu A
 \end{aligned}$$

$$\begin{aligned}
 I_{C2} &= \frac{A_2(1+\frac{V_{CE2}}{V_A})}{A_1(1+\frac{V_{CE1}}{V_A})} I_{C1} \\
 &= \frac{2.5(1+\frac{10}{50})}{1(1+\frac{0.7}{50})} \cdot 73.3 \mu A \\
 &= 216.7630058 \times 10^{-6} A \\
 &\approx 216.76 \mu A
 \end{aligned}$$

$$\begin{aligned}
 r_{o2} &= \frac{V_A + V_{CE2}}{I_{C2}} \\
 &= \frac{50 + 10}{216.76 \mu A} \\
 &= 276.8 k\Omega
 \end{aligned}$$

$$\begin{aligned}
 I_{C3} &= \frac{A_3(1+\frac{V_{CE3}}{V_A})}{A_1(1+\frac{V_{CE1}}{V_A})} I_{C1} \\
 &= \frac{5(1+\frac{8}{50})}{1(1+\frac{0.7}{50})} \cdot 73.3 \mu A \\
 &= 419.0751445 \times 10^{-6} A \\
 &\approx 419.08 \mu A
 \end{aligned}$$

$$\begin{aligned}
 r_{o3} &= \frac{V_A + V_{CE3}}{I_{C3}} \\
 &= \frac{50 + 8}{419.08 \mu A} \\
 &= 138.4 k\Omega
 \end{aligned}$$

$$\begin{aligned}
 I_{C4} &= \frac{A_4(1+\frac{V_{CE4}}{V_A})}{A_1(1+\frac{V_{CE1}}{V_A})} I_{C1} \\
 &= \frac{10(1+\frac{12}{50})}{1(1+\frac{0.7}{50})} \cdot 73.3 \mu A \\
 &= 895.9537572 \times 10^{-6} A \\
 &\approx 895.95 \mu A
 \end{aligned}$$


$$\begin{aligned}
 r_{o4} &= \frac{V_A + V_{CE4}}{I_{C4}} \\
 &= \frac{50 + 12}{895.95 \mu A} \\
 &= 69.2 k\Omega
 \end{aligned}$$

Note that the accuracy of the current mirror is dependent on β , V_A and the number of mirror transistors connected to the same diode-connected transistor

→ more base current, less accurate

↳ MOS don't have this problem → no gate current

2)

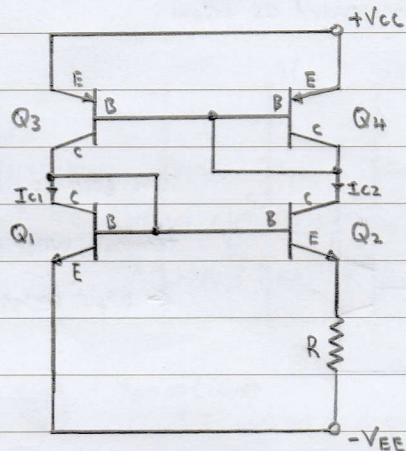

$$A_{E3} = 10 A_{E4}$$

$$A_{E2} = 10 A_{E1}$$

$$R = 1 \text{ k}\Omega$$

$$\beta \rightarrow \infty$$

ignore Early effect

Since $\beta \rightarrow \infty$, no I_B

$$I_{C1} = I_{C3}$$

$$I_{C2} = I_{C4}$$

ignore Early effect

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)}$$

$$\text{Since } A_{E3} = 10 A_{E4}$$

$$\text{since } I_{C3} = I_{C1}$$

$$A_{E2} = 10 A_{E1}$$

$$I_{C3} = 10 I_{C4}$$

$$I_{C1} = 10 I_{C2}$$

$$I_{S2} = 10 I_{S1}$$

The voltage across R is $V_{BE1} - V_{BE2}$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$

$$V_{BE1} - V_{BE2} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) - V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right)$$

$$= V_T \left[\ln\left(\frac{I_{C1}}{I_{S1}}\right) - \ln\left(\frac{I_{C2}}{I_{S2}}\right) \right]$$

$$= V_T \ln\left(\frac{I_{C1}}{I_{S1}} \times \frac{I_{S2}}{I_{C2}}\right)$$

$$= V_T \ln\left(\frac{I_{S2}}{I_{S1}} \times \frac{I_{C1}}{I_{C2}}\right)$$

$$= V_T \ln(10 \times 10)$$

$$= 0.025 \ln(100)$$

$$= 0.1151292546$$


$$\approx 0.115$$

$$I_{C2} \approx I_{E2} = \frac{V_{BE1} - V_{BE2}}{R}$$

$$= \frac{0.115}{1000}$$

$$= 115 \mu\text{A}$$

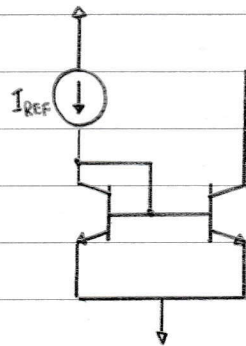
a simple current mirror can be constructed as below :



How good is this current mirror depends on across the terminal, what is output resistance

← output resistance = r_o

By adding a resistor

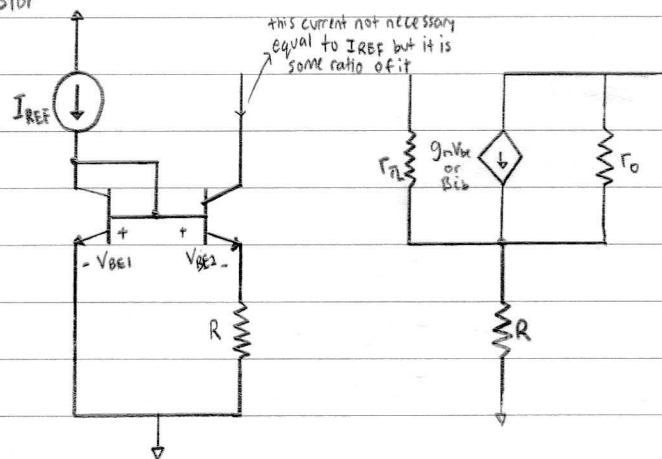

output resistance = $(1 + g_m V_{be}) r_o$

$$V_{BE1} = V_{BE2} + V_R$$

$$V_R = V_{BE1} - V_{BE2}$$

$$I_c = I_s e^{\left(\frac{V_{BE}}{V_T}\right)} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$I_c / \left(1 + \frac{V_{CE}}{V_A}\right) = I_s e^{\left(\frac{V_{BE}}{V_T}\right)}$$

$$I_c / \left(1 + \frac{V_{CE}}{V_A}\right) \cdot I_s = e^{\left(\frac{V_{BE}}{V_T}\right)}$$

$$\ln \left(\frac{I_c}{I_s} \cdot \frac{1}{1 + \frac{V_{CE}}{V_A}} \right) = \frac{V_{BE}}{V_T}$$

$$V_{BE} = V_T \ln \left(\frac{I_c}{I_s} \cdot \frac{1}{1 + \frac{V_{CE}}{V_A}} \right)$$

$$\downarrow$$

$$V_T = \frac{kT}{q}$$