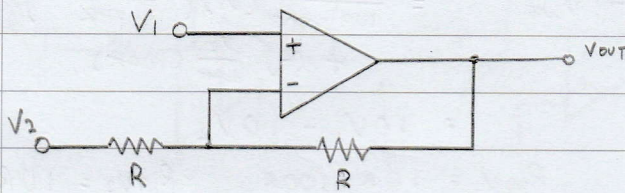


Esmund Lim

AE Tutorial 1

1a)



$$V_{OUT} = V_{OUT}|_{V_1} + V_{OUT}|_{V_2}$$

$$= V_1 \left(1 + \frac{R}{R}\right) + (-) \frac{V_2}{R} (R)$$

$$= 2V_1 - V_2$$


$$\text{or } V_1 + \left(\frac{V_1}{R} R\right) + (-) \frac{V_2}{R} R$$

$$= V_1 \left(1 + \frac{R}{R}\right) - V_2$$

$$= 2V_1 - V_2$$

$$R_{in V_1} = \infty$$

$$R_{in V_2} = R$$

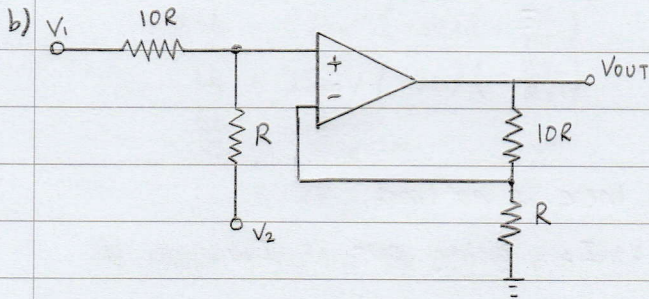

$$V_{OUT} = V_{OUT}|_{V_1} + V_{OUT}|_{V_2}$$

$$= \frac{R}{R+10R} (V_1) \left(\frac{R+10R}{R}\right) + \frac{10R}{R+10R} (V_2) \left(\frac{10R+R}{R}\right)$$


$$= V_1 + 10V_2$$

$$R_{in V_1} = 10R + R$$

$$= 11R$$

$$R_{in V_2} = 10R + R$$

$$= 11R$$

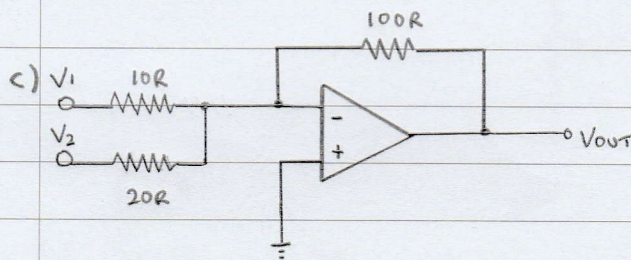


$$V_{OUT} = V_{OUT}|_{V_1} + V_{OUT}|_{V_2}$$

$$= - \left(\frac{V_1}{10R}\right) 100R - \frac{V_2}{20R} \left(\frac{5}{100R}\right)$$

$$= -10V_1 - 5V_2$$

$$R_{in V_1} = 10R$$

$$R_{in V_2} = 20R$$

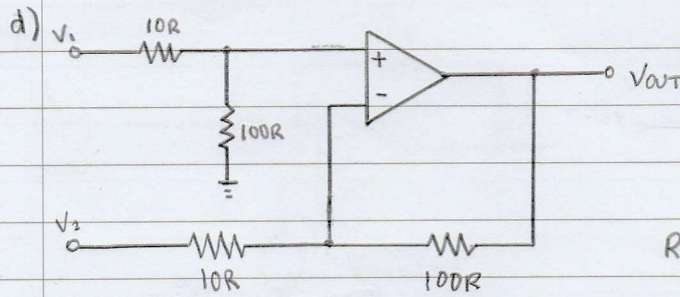

$$V_{out} = V_{out}|_{V_1} + V_{out}|_{V_2}$$


$$= \frac{100R}{100R+100R} (V_1) \left(\frac{100R+100R}{100R} \right)$$

$$+ (-) \frac{V_2}{100R} (100R)$$

$$= 10V_1 - 10V_2$$

$$R_{in} V_1 = 100R + 100R \quad R_{in} V_2 = 100R$$

$$= 110R$$

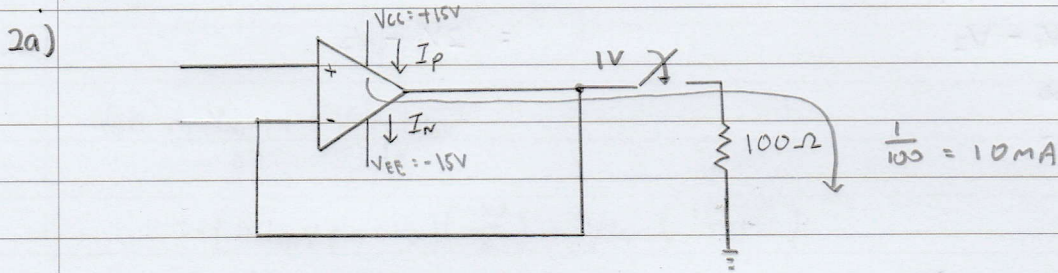

$$\frac{1}{100} = 10mA$$

b) $I_p = I_n$

1. No current going in the input

2. output not going out current because there is no load

3. only current going in op-amp is I_p , going out is I_n

When R_L is connected

$$I_p' = I_p + 10mA$$

$$I_n' = I_n$$

c) Additional power drawn

$$P = IV$$

$$= 15V (10mA)$$

$$= 150mW$$

output power


$$P = 1V \times 10mA$$

$$= 10mW$$

* efficiency poor

140mW turns to heat energy

3)

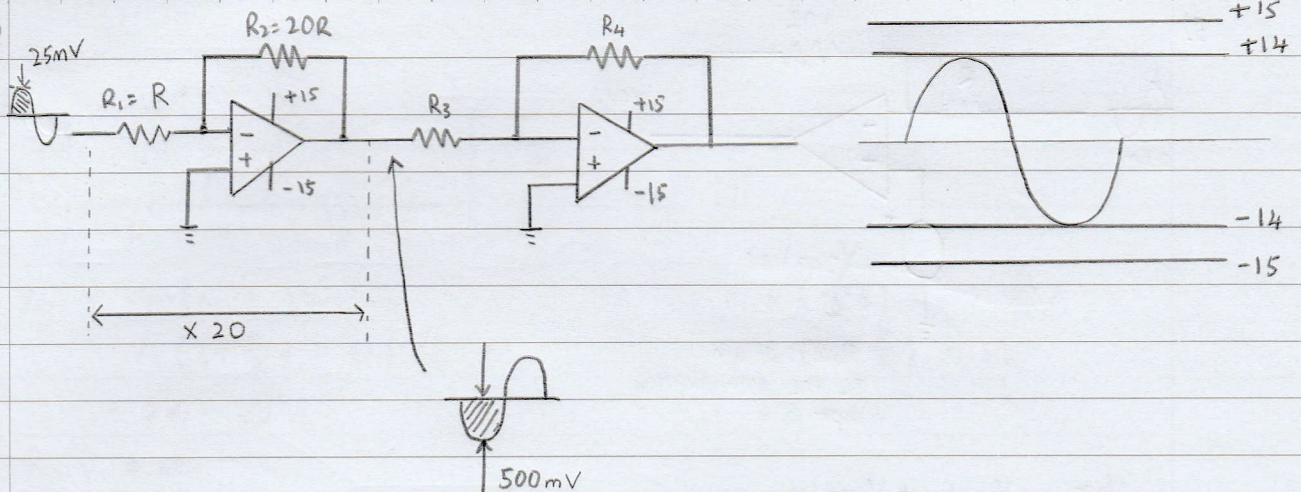

$$V_{OUT} = V_{in} \left(-\frac{R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right)$$

$$\pm 14 = \pm 25\text{mV} (-20) \left(-\frac{R_4}{R_3} \right)$$


$$14 = 25\text{mV} (-20) \left(-\frac{R_4}{R_3} \right)$$

$$\frac{R_4}{R_3} = \frac{14}{25\text{mV}(20)}$$

$$= 28$$

The maximum permissible gain of the second stage is 28


4)

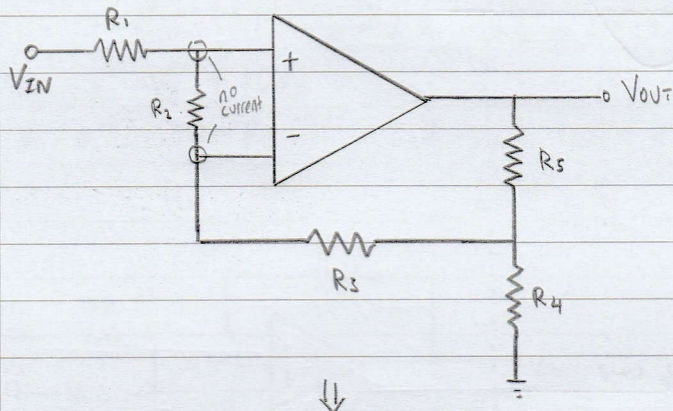

$$R_1 = 0$$

$$R_2 = \infty$$


$$R_3 = 0$$

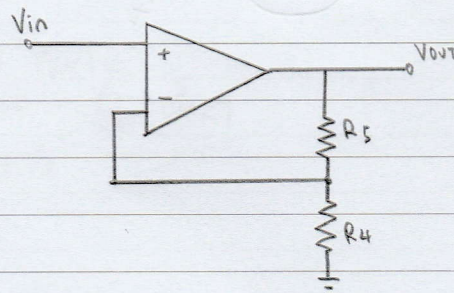

$$V_{OUT} = \frac{R_5 + R_4}{R_4} (V_{in})$$

$$\frac{V_{OUT}}{V_{in}} = \frac{R_5 + R_4}{R_4}$$

5)

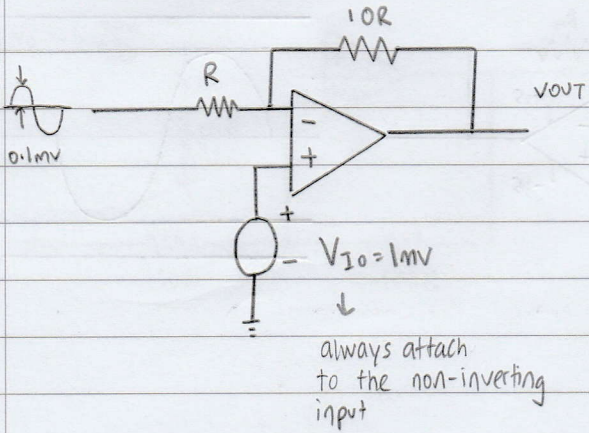

$$V_{OUT} = \underbrace{V_{OUT}|_n}_{ac} + \underbrace{V_{OUT}|_{V_{I0}}}_{dc}$$

$$= -(0.1mV \sin \omega t) \left(\frac{10k}{R} \right) + V_{I0} \cdot \left(\frac{10k + R}{R} \right)$$

$$= -1mV \sin \omega t + 1mV (11)$$

$$= \underbrace{(-1 \sin \omega t)}_{ac} + \underbrace{11}_{dc} mV$$

