

ESMUND LIM


A.E Tutorial 5

1)

a) PNP

$$|V_{BE}| = 0.7V$$

$$\beta = 100$$

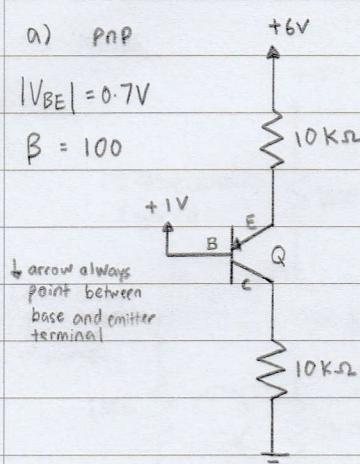

↳ arrow always point between base and emitter terminal

Assume Q is active

$$V_E = V_{EB} + V_B$$

$$= 0.7V + 1V$$

$$= 1.7V$$

$$I_E = \frac{6V - 1.7V}{10 k\Omega}$$

$$= 0.43mA$$

$$I_C = \beta I_B$$

$$= \alpha I_E$$

$$= \frac{\beta}{\beta+1} I_E$$

$$= \frac{100}{100+1} (0.43mA)$$

$$= 0.425742574 \times 10^{-3} mA$$

$$V_C = I_C R_C$$


$$= 0.425742574 \times 10^{-3} (10 k\Omega)$$

$$= 4.257425743V$$

$$\approx 4.3V$$

$$V_{BC} = 0.4V \sim 0.5V$$

$$V_{CE(SAT)} = 0.2 \sim 0.3V$$

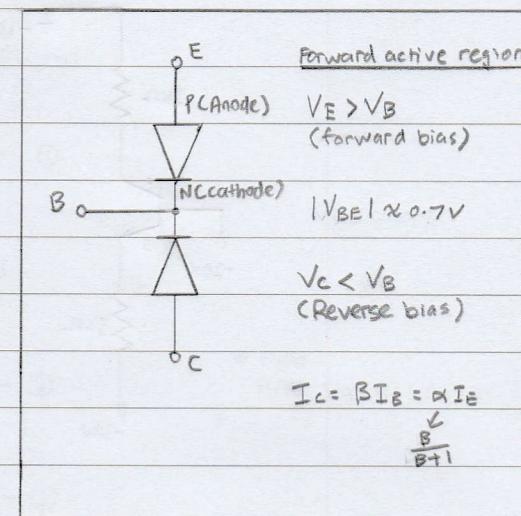Since $V_C > V_B$, device will be saturated \therefore Assumption is invalid

$$V_E = V_{EB} + V_B$$

$$= 0.7V + 1V$$

$$= 1.7V$$

$$V_C = V_E - V_{CE(SAT)}$$


$$= 1.7V - 0.3V$$

$$= 1.4V$$

$$I_C = \frac{V_C}{R_C}$$

$$= \frac{1.4V}{10 k\Omega}$$

$$= 0.14mA$$

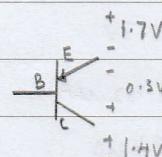

$$\therefore V_C = 1.4V$$

$$V_E = 1.7V$$

KCL

$$I_B = 0.29mA$$

$$I_E = I_B + I_C$$

$$I_C = 0.14mA$$


$$I_B = I_E - I_C$$

$$I_E = 0.43mA$$

$$= 0.43mA - 0.14mA$$

$$= 0.29mA$$

b)

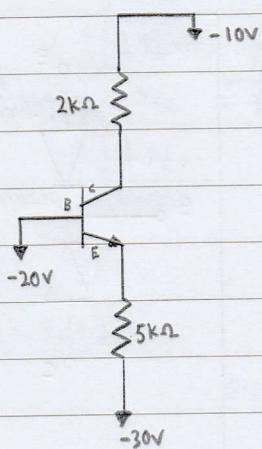

Assume Q is active

$$V_E = V_B - V_{BE}$$

$$= -20V - 0.7V$$

$$= -20.7V$$

$$I_E = \frac{V_E - V_{EE}}{R_E}$$

$$= \frac{-20.7V - (-30V)}{5k\Omega}$$

$$= 1.86mA$$

$$I_C = \alpha I_E$$

$$= \left(\frac{\beta}{\beta+1} \right) (I_E)$$

$$= \frac{100}{101} (1.86mA)$$

$$= 1.841584158mA$$

$$V_C = V_{CC} - I_C R_C$$

$$= -10V - (1.841584158mA)(2k\Omega)$$

$$= -13.68316832V$$

since $V_C > V_B$ (Reversed Bias)

∴ First assumption is valid, Q is active

$$I_C = \beta I_B$$

$$I_B = \frac{I_C}{\beta}$$

$$= \frac{1.841584158mA}{100}$$

$$= 18.41584158 \times 10^{-6} mA$$

$$= 18.42 \mu A$$

$$\therefore V_C = -13.68V$$

$$V_E = -20.7V$$


$$I_B = 18.42 \mu A$$

$$I_C = 1.84mA$$

$$I_E = 1.86mA$$

2)

a) NMOS

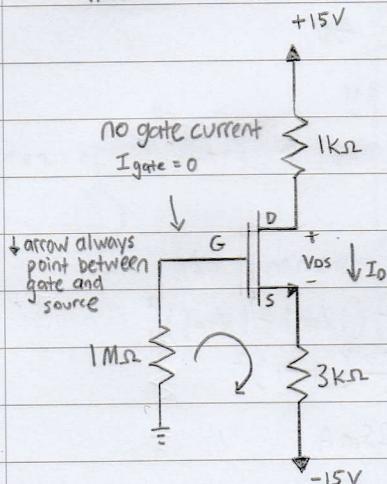

Assume saturation mode

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2$$

$$= \frac{0.5m}{2} (V_{GS} - 1)^2 \quad \text{--- ①}$$

KVL

$$V_{GS} + I_D R_S + (-15) = 0$$

$$V_{GS} + I_D R_S = 15$$

$$V_{GS} + 3K_I_D = 15 \quad \text{--- ②}$$

* Note
since $I_g = 0$, $I_o = I_s$

$$\text{② : } V_{GS} = 15 - 3K_I_D \quad \text{--- ③}$$

Sub ③ into ①

$$I_D = \frac{0.5m}{2} (15 - 3K_I_D - 1)^2$$

$$= 0.25m (14 - 3K_I_D)^2$$

$$= 0.25m (14 - 3K_I_D)(14 - 3K_I_D)$$

$$= 0.25m [196 - 84K_I_D + 9K_I_D^2]$$

$$= 0.049 - 21I_D + 2250I_D^2$$

$$2250I_D^2 - 22I_D + 0.049 = 0$$

$$I_D = 6.34609745\text{mA} \text{ or } 3.431680328\text{mA}$$

For $I_D = 6.34609745\text{mA}$

$$V_{GS} = 15 - 3K(6.34609745\text{mA})$$

$$= -4.03829235\text{V}$$

Since $V_{GS} < V_{TN}$ For $I_D = 3.431680328\text{mA}$

$$V_{GS} = 15 - 3K(3.431680328\text{mA})$$

$$= 4.704959016\text{V}$$

 $V_{GS} > V_{TN}$

This answer is unacceptable

KVL

$$-15 + I_D R_D + V_{DS} + I_D R_S + (-15) = 0$$

$$V_{DS} = 30 - I_D R_D - I_D R_S$$

$$= 30 - 3.43\text{mA}(1\text{k}\Omega + 3\text{k}\Omega)$$


$$= 16.28\text{V}$$

For saturation mode

$$V_{DS} \geq V_{GS} - V_{TN}$$

$$16.28\text{V} \geq 4.7\text{V} - 1\text{V} \quad (\text{First assumption is correct})$$

b) PMOS

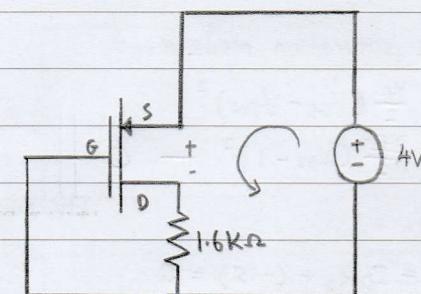

$$|V_{GS}| = |-4V|$$

$$= 4V$$

$$|V_{TP}| = 1V$$

since $|V_{GS}| > |V_{TP}|$, it is not cut-off

$$V_{TP} = -1V$$

$$k_p = 250 \mu A/V^2$$

Assume saturation mode

$$\begin{aligned} I_D &= \frac{k_p}{2} (|V_{GS}| - |V_{TP}|)^2 \\ &= \frac{250\mu}{2} (4-1)^2 \\ &= 1.125mA \end{aligned}$$

KVL

$$-4 + |V_{DS}| + 1.6k(I_D) = 0$$

$$|V_{DS}| = 4 - 1.6k(I_D)$$

$$= 4 - 1.6k(1.125mA)$$

$$= 2.2V$$

For saturation mode

$$|V_{DS}| \geq |V_{GS}| - |V_{TP}|$$


Since

$$|V_{DS}| \leq |V_{GS}| - |V_{TP}|$$

$$2.2V \leq 4V - 1V$$

\therefore It is not in saturation but it is in triode region, which is also known as ohmic or linear region

3) PNP transistor

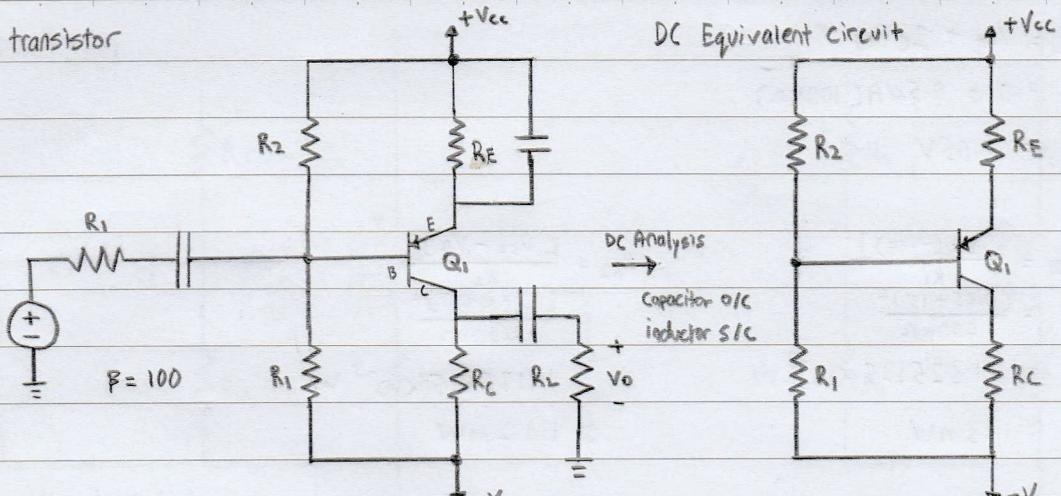

$$R_{eq} = R_{TH} = R_1 // R_2$$

$$= \frac{200\text{k}\Omega \times 200\text{k}\Omega}{200\text{k}\Omega + 200\text{k}\Omega}$$

$$= 100\text{k}\Omega$$

$$V_{eq} = V_{TH} = \frac{R_1}{R_1+R_2} (15 - 15) \quad \text{or by superposition}$$

$$= 0\text{V}$$

$$V_{eq} = \frac{R_1}{R_1+R_2} V_{cc} + \frac{R_2}{R_1+R_2} (-V_{EE})$$


\downarrow $-V_{EE}$ ground V_{cc} ground

$$= \frac{200\text{k}\Omega}{200\text{k}\Omega + 200\text{k}\Omega} (15\text{V}) + \frac{200\text{k}\Omega}{200\text{k}\Omega + 200\text{k}\Omega} (-15\text{V})$$

$$= 0\text{V}$$

Simplify by Thevenin theorem

Find R_{TH}
→ Turn off source

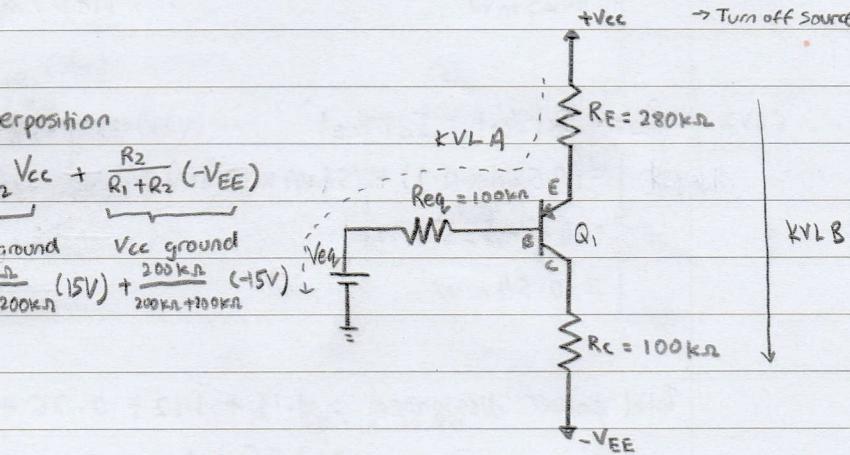

KVL A

$$-15 + I_E R_E + V_{EB} + I_B R_{eq} = 0$$

$$I_E R_E + V_{EB} + I_B R_{eq} = 15$$

$$(B+1) I_B R_E + V_{EB} + I_B R_{eq} = 15$$

$$(101)(280\text{k}\Omega) I_B + 100\text{k}\Omega I_B = 15 - 0.7$$

$$28.38 \times 10^6 I_B = 14.3$$

$$I_B = 0.503875969 \times 10^{-6} \text{ A}$$

$$\approx 0.5\text{mA}$$

$$I_C = B I_B$$

$$= 100 (0.5\text{mA})$$

$$= 50\text{mA}$$

$$I_E = (100+1) I_B$$

$$= 50.5\text{mA}$$

KVL B

$$-15 + I_E R_E + V_{EC} + I_C R_C + (-15) = 0$$

$$V_{EC} = 30 - I_E R_E - I_C R_C$$


$$= 30 - 50.5\text{mA} (280\text{k}\Omega) - 50\text{mA} (100\text{k}\Omega)$$

$$= 10.86\text{V}$$

∴ Q-point (I_C, V_{EC})

$$(50\text{mA}, 10.86\text{V})$$

Thevenin Equivalent

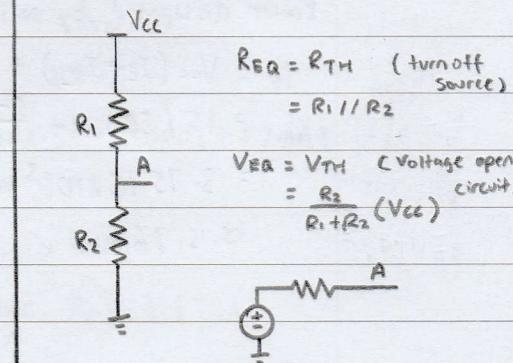

$$R_{eq} = R_{TH} \quad (\text{turnoff source}) \\ = R_1 // R_2$$

$$V_{TH} = V_{cc} \quad (\text{voltage open circuit}) \\ = \frac{R_2}{R_1+R_2} (V_{cc})$$

$$\begin{aligned} V_B &= V_{eq} + I_B R_{eq} \\ &= 0 + 0.5\mu A (100k\Omega) \\ &= 0.05V \end{aligned}$$

$$\begin{aligned} P_{R1} &= \frac{[V_B - (-V_{EE})]^2}{R_1} & P_{R2} &= \frac{[V_{cc} - V_B]^2}{R_2} \\ &= \frac{(0.05 + 15)^2}{200k\Omega} & &= \frac{[15 - 0.05]^2}{200k\Omega} \\ &= 1.1325125 \times 10^{-3} W & &= 1.1175125 \times 10^{-3} W \\ &\approx 1.13mW & &\approx 1.12mW \end{aligned}$$

$$\begin{aligned} P_{Re} &= I_c^2 R_e & P_{RE} &= I_E^2 R_E \\ &= (50\mu A)^2 (100k\Omega) & &= (50.5\mu A)^2 (280k\Omega) \\ &= 0.25mW & &= 0.71407mW \end{aligned}$$


$$\begin{aligned} P_{BJT} &= I_B |V_{BE}| + I_C |V_{CE}| \\ &= (0.5\mu A \times 0.7) + (50\mu A \times 10.86) \\ &= 0.54335mW \\ &\approx 0.54mW \end{aligned}$$

$$\begin{aligned} \text{Total power dissipated} &= 1.13 + 1.12 + 0.25 + 0.71 + 0.54 \\ &= 3.75mW \end{aligned}$$

Power dissipated by source :

$$\begin{aligned} P_S &= V_{cc} (I_E + I_{R2}) + |V_{EE}| (I_C + I_{R1}) \\ &= 15 \left(50.5\mu A + \frac{15 - 0.05}{200k\Omega} \right) + 15 \left(50\mu A + \frac{0.05 - (-15)}{200k\Omega} \right) \\ &= 3.7575 \times 10^{-3} W \\ &\approx 3.76mW \end{aligned}$$

4) NMOS

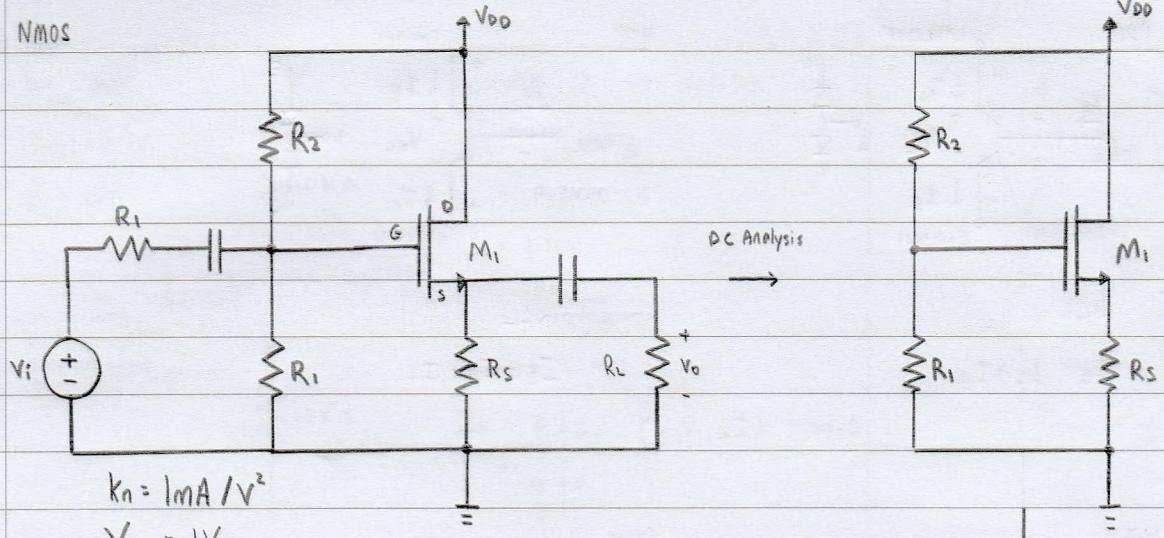


$$R_{eq} = R_{TH}$$

$$\begin{aligned} &= R_2 || R_1 \\ &= \frac{1.2 \text{ M}\Omega \times 910 \text{ k}\Omega}{1.2 \text{ M}\Omega + 910 \text{ k}\Omega} \\ &= 517.535545 \text{ k}\Omega \\ &\approx 518 \text{ k}\Omega \end{aligned}$$

$$V_{eq} = V_{TH}$$
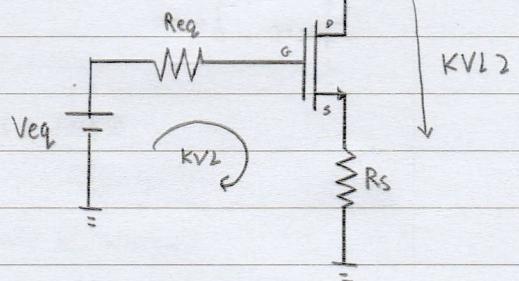
$$\begin{aligned} &= \frac{R_1}{R_1 + R_2} (V_{DD}) \\ &= \frac{1.2 \text{ M}\Omega}{1.2 \text{ M}\Omega + 910 \text{ k}\Omega} (15 \text{ V}) \\ &= 8.530805687 \text{ V} \\ &\approx 8.53 \text{ V} \end{aligned}$$



KVL

$$-V_{eq} + V_{GS} + I_D R_S = 0$$

$$\text{if } I_D = 3.38 \text{ mA}$$

$$V_{eq} = V_{GS} + I_D R_S$$

$$V_{GS} = 8.53 - 3000(3.38 \text{ mA})$$

$$V_{GS} = V_{eq} - I_D R_S$$

$$= -1.61 \text{ V} \quad (\text{reject})$$

$$= 8.53 \text{ V} - 3000 I_D \quad \text{--- ①}$$

$$V_{GS} < V_{TN}$$

$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \quad \text{--- ②}$$

$$\text{if } I_D = 1.87 \text{ mA}$$

sub ① into ②

$$V_{GS} = 8.53 - 3000(1.87 \text{ mA})$$

$$I_D = \frac{1}{2} (8.53 \text{ V} - 3000 I_D - 1)^2$$

$$= 2.92 \text{ V}$$

$$= 0.5m (7.53 \text{ V} - 3000 I_D)^2$$

$$V_{GS} > V_{TN}$$

$$= 0.5m [(7.53 - 3000 I_D)(7.53 - 3000 I_D)]$$

$$\text{Hence, } I_D = 1.87 \text{ mA}$$

$$= 0.5m [56.7009 - 22590 I_D - 22590 I_D + 9000000 I_D^2]$$

$$= 4500 I_D^2 - 22.59 I_D + 0.02835045$$

KVL2 :

$$4500 I_D^2 - 23.59 I_D + 0.02835045 = 0$$

$$-V_{DD} + V_{DS} + I_D R_S = 0$$

$$I_D = 3.376176311 \text{ mA} \quad \text{or} \quad 1.866045911 \text{ mA}$$

$$V_{DS} = V_{DD} - I_D R_S$$



$$\approx 3.38 \text{ mA}$$

$$\approx 1.87 \text{ mA}$$

$$= 15 - (1.87 \text{ mA})(3 \text{ k}\Omega)$$

$$= 9.39 \text{ V}$$
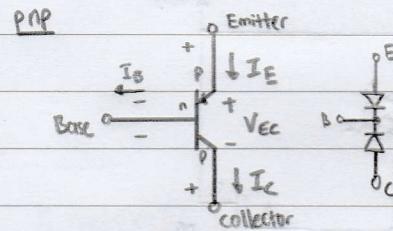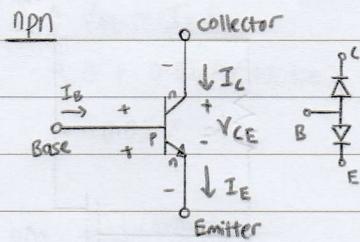
$$\therefore I_D = 1.87 \text{ mA}, \quad V_{DS} = 9.39 \text{ V}$$



KCL


$$I_E = I_C + I_B$$

KCL


$$I_E = I_B + I_C$$

Q-point (I_C , V_{CE})

NMOS

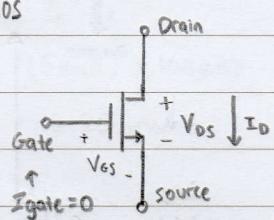

PMOS

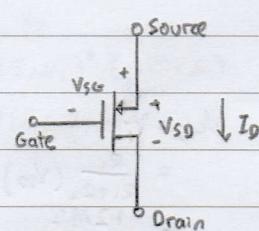Q-point (I_D , V_{SD})