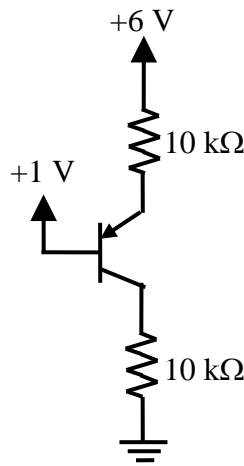



Nanyang Technological University
School of Electrical & Electronic Engineering
E2002 Analog Electronics – Tutorial 5

1. Identify the region of operation for the following circuits. What is the V_C , V_E , I_B , I_C and I_E in each case. If active, what is the collector voltage? Assume $|V_{BE}| = 0.7$ V and $\beta = 100$.

(Ans: (a) Saturation, $V_C = 1.4$ V, $V_E = 1.7$ V, $I_B = 0.29$ mA, $I_C = 0.14$ mA, $I_E = 0.43$ mA;
(b) Active, $V_C = -13.68$ V, $V_E = -20.7$ V, $I_B = 18.4$ μ A, $I_C = 1.86$ mA, $I_E = 1.86$ mA)



(a)

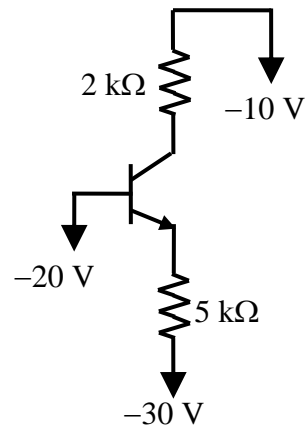


(b)


Figure 1

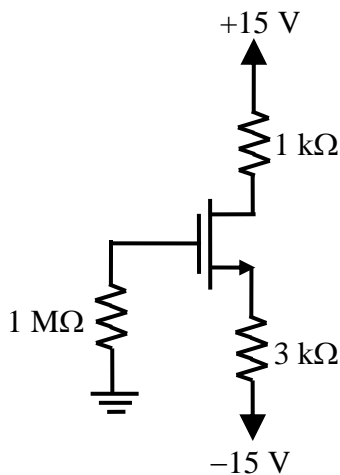2. Check if the region of operation for the following circuits. Determine the operating point if it is in saturation. Assume $\lambda = 0$. $V_{TN} = 1$ V and $K_n = 0.5$ mA/V⁻¹ for NMOS and $V_{TP} = -1$ V and $K_p = 250$ μ A/V⁻¹ for PMOS.

(Ans: (a) Saturation region, $V_{DS} = 16.28$ V, $I_D = 3.43$ mA; (b) triode region)



(a)

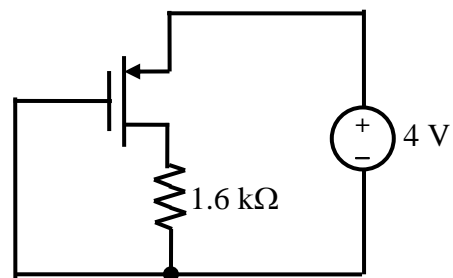

(b)

Figure 2

3. A common-emitter amplifier circuit is shown in Figure 3. Assume that the capacitors have infinite value, $\beta = 100$, $V_{CC} = V_{EE} = 15\text{ V}$, $R_I = 750\ \Omega$, $R_1 = R_2 = 200\text{ k}\Omega$, $R_L = 100\text{ k}\Omega$, $R_E = 280\text{ k}\Omega$, and $R_C = 100\text{ k}\Omega$. Calculate the DC operating point of the amplifier. (Ans: $I_C = 50\ \mu\text{A}$, $V_{EC} = 10.86\text{ V}$).

Calculate the dc power dissipation in each element in the amplifier circuit. Compare the result to the total power delivered by the sources.

(Ans: $P_{R1} = 1.125\text{ mW}$, $P_{R2} = 1.125\text{ mW}$, $P_{Rc} = 0.25\text{ mW}$, $P_{RE} = 0.71\text{ mW}$, $P_{BJT} = 0.54\text{ mW}$. $P_S = 3.76\text{ mW}$)

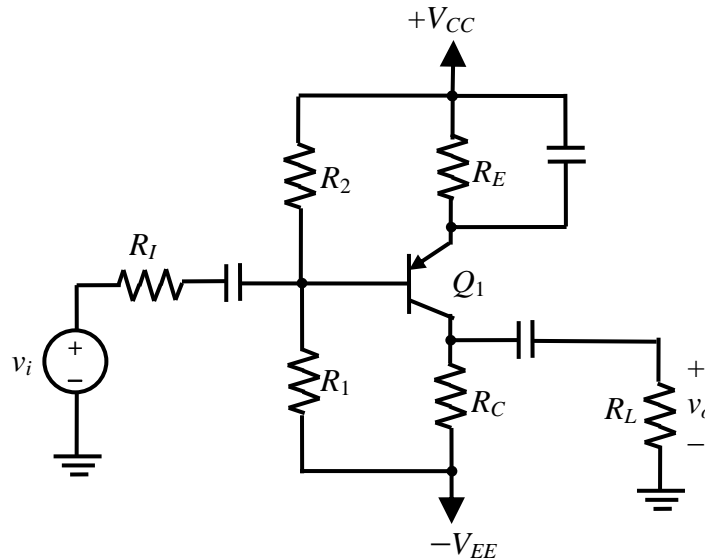


Figure 3

4. Draw the DC equivalent circuit for the common drain amplifier of Figure 4. Assume that the capacitors have infinite value, $K_n = 1\text{ mA/V}^2$, $V_{TN} = 1\text{ V}$, $R_I = 100\ \Omega$, $R_1 = 1.2\text{ M}\Omega$, $R_2 = 910\text{ k}\Omega$, $R_L = 250\ \Omega$, $R_S = 3\text{ k}\Omega$ and $V_{DD} = 15\text{ V}$, calculate the DC operating point of the amplifier. (Ans: $I_D = 1.87\text{ mA}$, $V_{DS} = 9.39\text{ V}$).

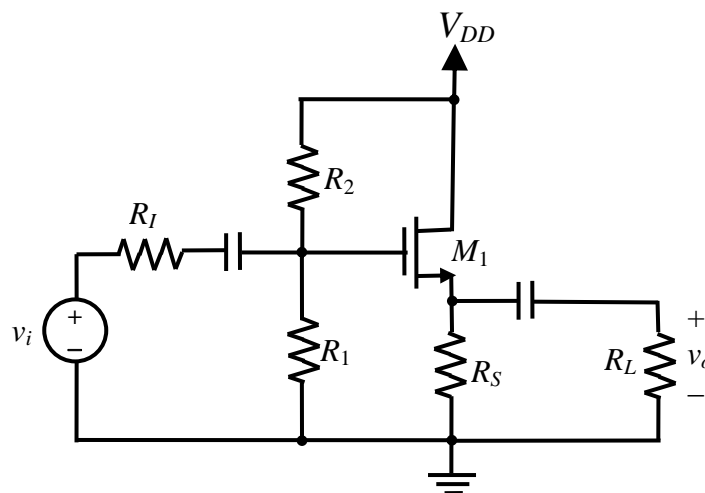


Figure 4