

**TUTORIAL 1** (with answers at the back)

- Find an expression for  $v_{OUT}$  as a function of  $v_1$  and  $v_2$  in each of the op-amp circuits of Fig.T1-1 and also determine the input resistance(s) with respect to ground for each of the op-amp circuits. Assume op-amps used are ideal.

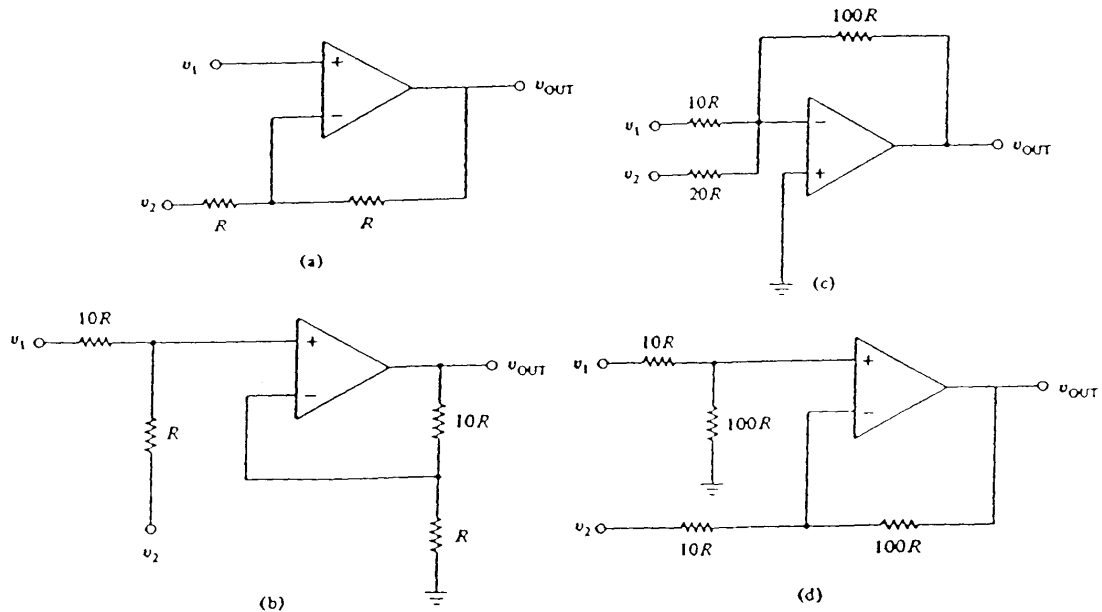



Fig T.1-1

- Consider an op-amp follower (i.e. the output is connected to the negative input) powered by  $\pm 15V$  supplies. The input voltage is set to  $1V$  and the output feeds a  $100\ \Omega$  resistive load  $R_L$  to ground. With  $R_L$  disconnected, the current  $I_P$  from  $V_{CC}$  into the op-amp equals the current  $I_N$  from the op-amp into  $V_{EE}$ . The op-amp used is assumed to be ideal. (Note:  $V_{CC}$  is the positive supply voltage of  $+15V$  and  $V_{EE}$  is the negative supply voltage of  $-15V$ ).

  - Draw a diagram of this circuit. Label the current  $I_P$  and  $I_N$ .
  - What is the difference between the power supply currents  $I_P$  and  $I_N$  when  $R_L$  is connected?
  - Find the additional power drawn from the power supplies when  $R_L$  is connected.

- A high-gain op-amp circuit is formed by cascading two inverting amplifiers in series. Both op-amps are connected to  $\pm 15V$  power supplies. The first stage has gain of 20. The cascade is to be designed so that the peak output voltage of the second stage comes no closer than  $1V$  to either power supply voltage. If the input is equal to a  $25\text{-mV}$  peak sinusoid, what is the maximum permissible gain of the second stage if its output is to remain within its allowed swing limits? Assume op-amps used are ideal.

4. Find an expression for  $v_{OUT}$  in the circuit shown in Fig T1-2. Assume the op-amp used is ideal.

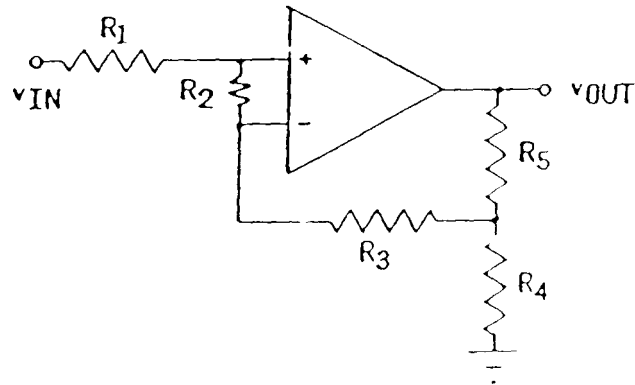

**Fig. T 1-2**

5. An inverting amplifier with a gain of -10 is made from a non-ideal op-amp having an input offset voltage of 1mV. A sinusoidal input voltage of 0.1mV peak amplitude is applied. What are the resulting ac and dc components of the output voltage?

## Partial Answers to Tutorial 1

1

(a)  $V_{OUT} = 2v_1 - v_2$

$$R_{in1} = \infty$$

$$R_{in2} = R$$

(b)  $V_{OUT} = v_1 + 10 v_2$

$$R_{in1} = 11R$$

$$R_{in2} = 11R$$

(c)  $V_{OUT} = -(10v_1 + 5 v_2)$

$$R_{in1} = 10R$$

$$R_{in2} = 20R$$

(d)  $V_{OUT} = 10(v_1 - v_2)$

$$R_{in1} = 110R$$

$$R_{in2} = 10R$$

2. (b)  $I_P - I_N = 10 \text{ mA}$

(c) The additional power drawn from  $V_{CC}$  is

$$\Delta P = 150 \text{ mW}$$

No additional power is drawn from  $V_{EE}$ , the negative supply.

3. The maximum permissible gain of the second stage is 28.

4. 
$$v_{OUT} = \left( \frac{R_5 + R_4}{R_4} \right) v_{IN}$$

5. 
$$v_{OUT} = \sum_{i=1}^2 (v_{OUT})_i = (-1 \sin \omega t + 11) \text{ mV}$$