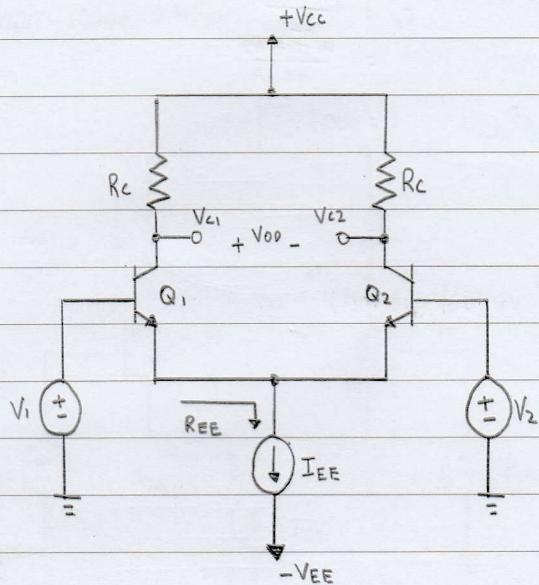


Esmund Lim

A.E Tutorial 8

1)



$$V_{CC} = V_{EE} = 12V$$

$$\beta = 100$$



$$I_{EE} = 400 \mu A$$

$$R_{EE} = 200 k\Omega$$

$$R_C = 39 k\Omega$$

$$V_A = \infty$$

DC Analysis

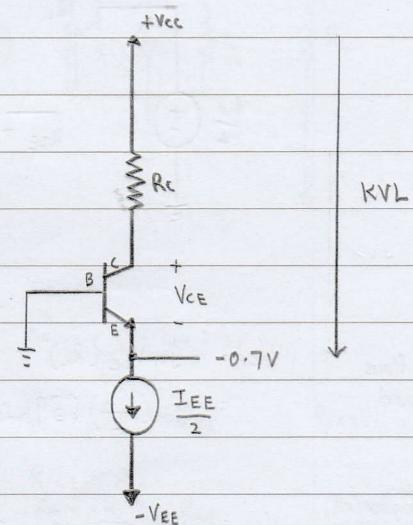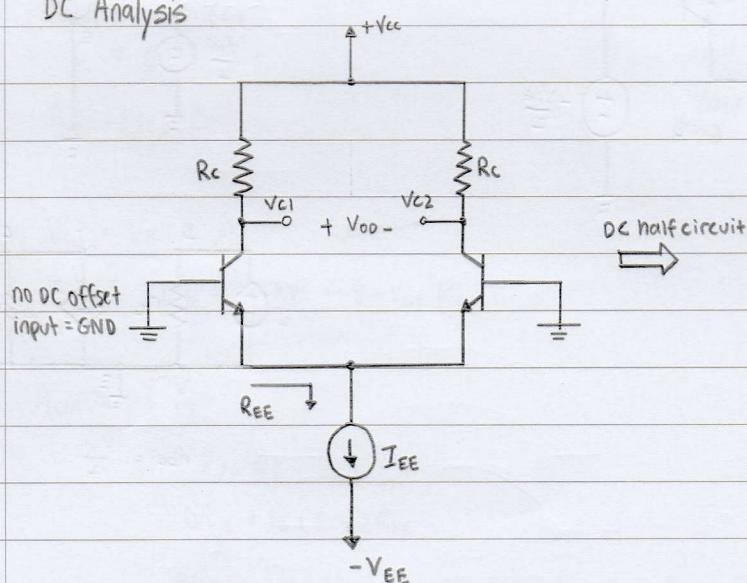

$$I_C = \alpha I_E$$

$$= \frac{\beta}{\beta+1} \left(\frac{I_{EE}}{2} \right)$$

$$= \frac{100}{100+1} \left(\frac{400 \mu A}{2} \right)$$

$$= 198.019802 \times 10^{-6} A$$

$$\approx 198 \mu A$$

By KVL

$$-V_{CC} + R_C I_C + V_{CE} + (-0.7) = 0$$

$$V_{CE} = V_{CC} - R_C I_C + 0.7$$

$$= 12 - 39 k\Omega (198 \mu A) + 0.7$$

$$= 4.977227722 V$$

$$\approx 4.98 V$$

∴ Q-point




$$(198 \mu A, 4.98 V)$$

$$\begin{aligned}
 b) \quad g_m &= 40 I_C & r_{\pi} &= \frac{B}{g_m} & R_o &= \frac{V_A + V_{CE}}{I_C} \\
 &= 40 (198 \mu A) & &= \frac{100}{7.92 \text{ mS}} & &= \frac{\infty + 4.98}{198 \mu A} \\
 &= 7.92 \text{ mS} & &= 12.62626263 \times 10^3 \Omega & &= \infty \\
 & & & \approx 12.63 \text{ k}\Omega & &
 \end{aligned}$$

AC Analysis \rightarrow Differential-mode (with virtual ground)

\rightarrow Common-mode

Differential mode analysis

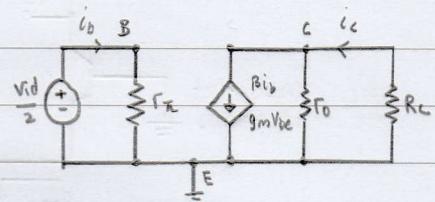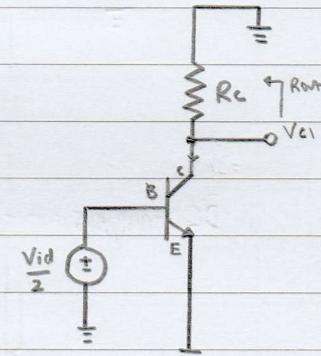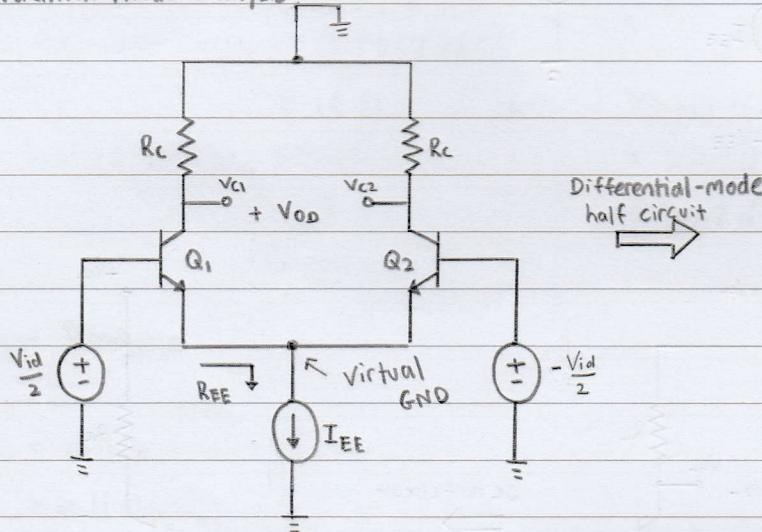

$$\begin{aligned}
 V_{c1} &= -g_m V_{be} (R_c) \\
 &= -g_m \left(\frac{V_{id}}{2}\right) (39 \text{ k}\Omega)
 \end{aligned}$$

$$V_{be} = \frac{V_{id}}{2}$$

$$V_{c2} = g_m \left(\frac{V_{id}}{2}\right) (39 \text{ k}\Omega)$$


same magnitude
but 180° out of
phase as compared
to Vc1

$$\begin{aligned}
 V_{od} &= V_{c1} - V_{c2} \\
 &= -g_m \left(\frac{V_{id}}{2}\right) (39 \text{ k}\Omega) - g_m \left(\frac{V_{id}}{2}\right) (39 \text{ k}\Omega) \\
 &= -g_m V_{id} (39 \text{ k}\Omega)
 \end{aligned}$$


$$\begin{aligned}
 \text{Adm-diff} &= \frac{V_{od}}{V_{id}} \\
 &= \frac{-g_m V_{id} (39 \text{ k}\Omega)}{V_{id}} \\
 &= -g_m (39 \text{ k}\Omega) \\
 &= -7.92 \text{ mS} (39 \text{ k}\Omega) \\
 &= -308.88
 \end{aligned}$$

$$\begin{aligned}
 \text{Adm-se1} &= \frac{V_{c1}}{V_{id}} \\
 &= \frac{-g_m \left(\frac{V_{id}}{2}\right) (R_c)}{V_{id}} \\
 &= -g_m \frac{R_c}{2} \\
 &= -\frac{308.88}{2} \\
 &= -154.44
 \end{aligned}$$
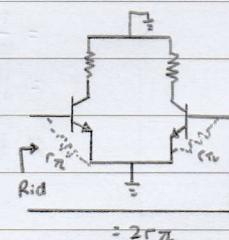
$$\begin{aligned}
 R_{id} &= 2 r_{\pi} \\
 &= 2 (12.63 \text{ k}\Omega) \\
 &= 25.26 \text{ k}\Omega
 \end{aligned}$$



Common-mode analysis

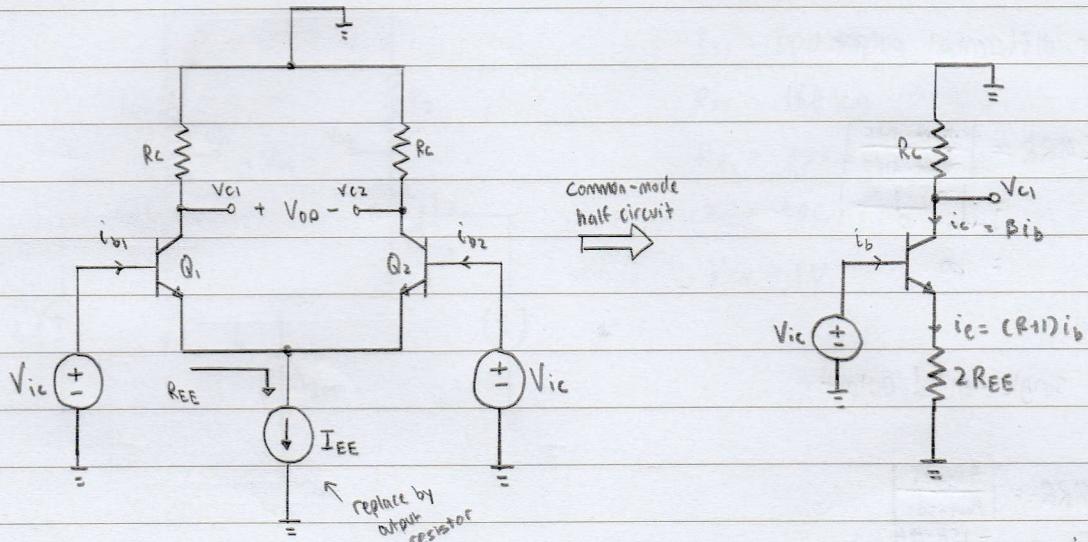

$$\begin{aligned} V_{od} &= V_{c1} - V_{c2} \\ &= 0 \end{aligned}$$

$$A_{cm-diff} = 0$$

$$V_{c1} = V_{c2}$$

$$= -\beta i_b R_c \text{ or } -g_m V_{be} R_c$$

$$A_{cm-se1} = \frac{V_{c1}}{V_{ic}}$$

$$= -\beta j_B R_c$$

$$j_B r_n + j_B (\beta+1) 2R_{EE}$$

$$= -\beta R_c$$

$$r_n + (\beta+1) 2R_{EE}$$

$$= -100 (39 k\Omega)$$

$$= 12.63 k\Omega + (101 \times 2 \times 200 k\Omega)$$

$$= -0.09650448387$$

$$\approx -0.0965$$

$$\begin{aligned} R_{ic1} &= \frac{V_{ic}}{i_{ic}} \\ &= \frac{r_n i_b + (\beta+1) i_b 2R_{EE}}{i_{ic}} \end{aligned}$$

$$= r_n + (\beta+1) 2R_{EE} = R_{ic2}$$

$$R_{ic} = R_{ic1} // R_{ic2}$$


$$= \frac{r_n + (\beta+1) 2R_{EE}}{2}$$

$$= \frac{12.63 k\Omega + (101 \times 2 \times 200 k\Omega)}{2}$$

$$= 20.206315 \times 10^6 \Omega$$

$$\approx 20.2 M\Omega$$

$$\frac{A \times A}{2A} = \frac{A}{2}$$

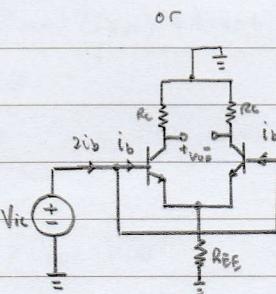

$$R_{ic} = \frac{V_{ic}}{2i_D}$$

CMRR (Common mode rejection ratio)

For differential output

$$\begin{aligned} CMRR &= \left| \frac{A_{dm-diff}}{A_{cm-diff}} \right| \\ &= \left| \frac{-308.88}{0} \right| \\ &= \infty \end{aligned}$$

For single-ended output


$$\begin{aligned} CMRR &= \left| \frac{A_{dm-sei}}{A_{cm-sei}} \right| \\ &= \frac{-154.44}{-0.0965} \\ &= 1600,414508 \\ &\approx 1600 \quad \text{or} \quad \text{convert to dB} \\ &= 20 \log 1600 \\ &= 64.08239965 \\ &\approx 64.1 \text{ dB} \end{aligned}$$

Output Resistance


$$\begin{aligned} R_{o1} &= R_{o2} \\ &= 11139 \text{ k}\Omega \\ &= 39 \text{ k}\Omega \end{aligned}$$

$$\begin{aligned} R_{od} &= R_{o1} + R_{o2} \\ &= 39 \text{ k}\Omega \times 2 \\ &= 78 \text{ k}\Omega \end{aligned}$$

2)

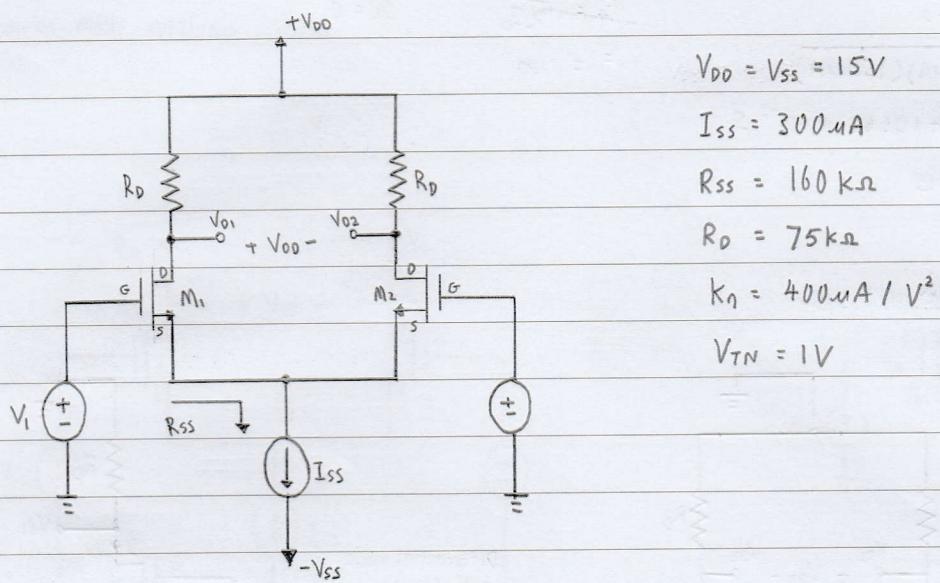

DC Analysis

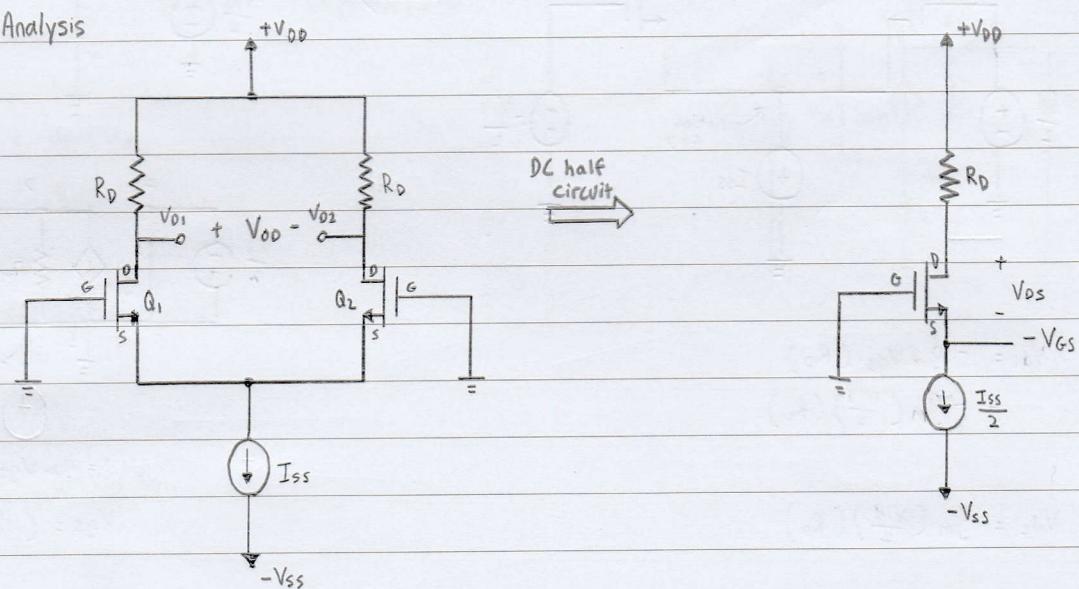

Same as source current

$$I_D = \frac{I_{SS}}{2}$$

$$= \frac{300\mu A}{2}$$

$$= 150\mu A$$

By KVL

$$-15 + I_D R_D + V_{DS} + (-1.866) = 0$$

$$V_{DS} = 15 - I_D R_D + 1.866$$

$$= 15 - 150\mu A (75k\Omega) + 1.866$$

$$= 5.616 V$$

$$\approx 5.62 V$$

$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2$$

$$(V_{GS} - V_{TN})^2 = I_D \div \frac{k_n}{2}$$

$$V_{GS} - V_{TN} = \sqrt{I_D \times \frac{2}{k_n}}$$

$$V_{GS} = \sqrt{\frac{2 I_D}{k_n}} + V_{TN}$$

$$= \sqrt{\frac{2(150\mu A)}{400\mu A}} + 1$$

$$= 1.866025404 V$$

$$\approx 1.866 V$$

The MOSFETs are in saturation region

$$\therefore V_{DS} = 5.62 V > V_{GS} - V_{TN}$$


Q-point

$$= 0.866 V$$

(150μA, 5.62V)

b) $g_m = \sqrt{2k_n I_D}$ $r_o = \frac{1}{2k_n I_D}$ $\pi = 0$
 $= \sqrt{2(400\text{mA})(150\text{mA})} = \infty$
 $= 0.346410161 \times 10^{-3} \text{s}$
 $\approx 0.346 \text{ms}$

Differential mode analysis

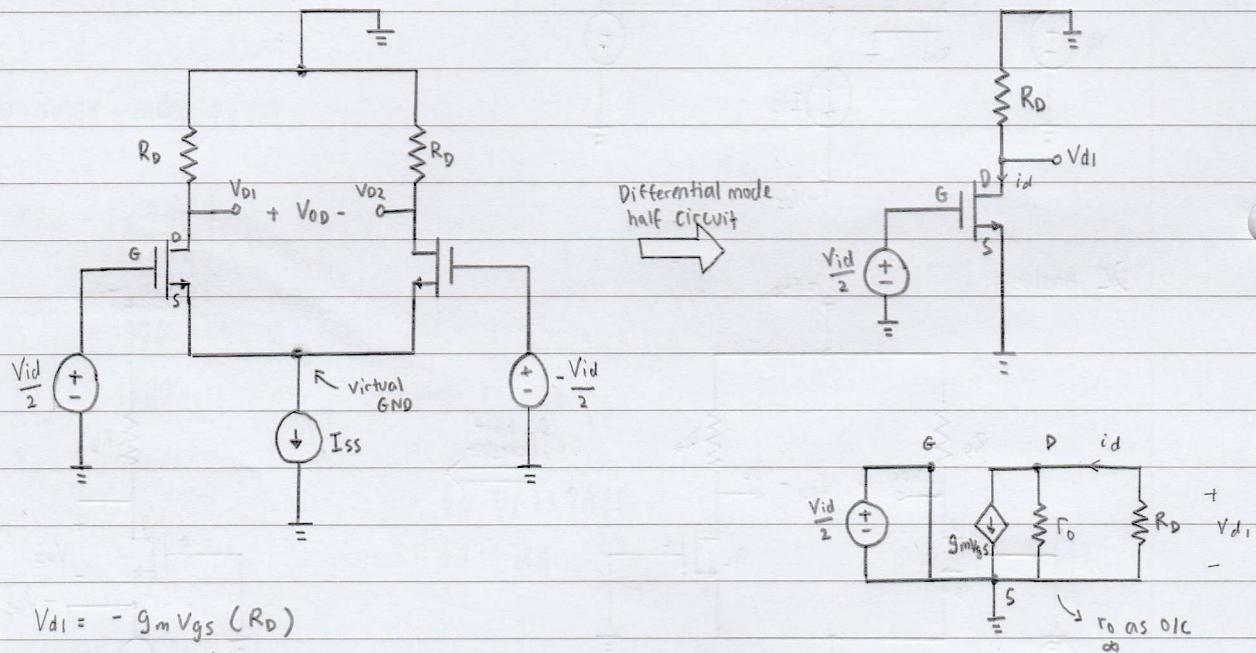

$$i_d = g_m V_{gs}$$

$$V_{d2} = g_m \left(\frac{V_{id}}{2}\right) (R_D)$$

$$V_{gs} = \left(\frac{V_{id}}{2}\right)$$

$$V_{od} = V_{d1} - V_{d2}$$


$$= -g_m (V_{id}) (R_D)$$

$$\begin{aligned} A_{dm-diff} &= \frac{V_{od}}{V_{id}} \\ &= -\frac{g_m (V_{id}) R_D}{V_{id}} \\ &= -g_m R_D \\ &= -(0.346\text{ms})(75\text{k}\Omega) \\ &= -25.95 \end{aligned}$$


$$\begin{aligned} A_{dm-se} &= \frac{V_{d1}}{V_{id}} \\ &= -\frac{g_m \left(\frac{V_{id}}{2}\right) (R_D)}{V_{id}} \\ &= -\frac{g_m R_D}{2} \\ &= -\frac{-25.95}{2} \\ &= -12.975 \end{aligned}$$

$$R_{id} = \infty \quad (I_{gate} = 0) \therefore R = \frac{V}{I} = \frac{V}{0} = \infty$$

Common mode analysis

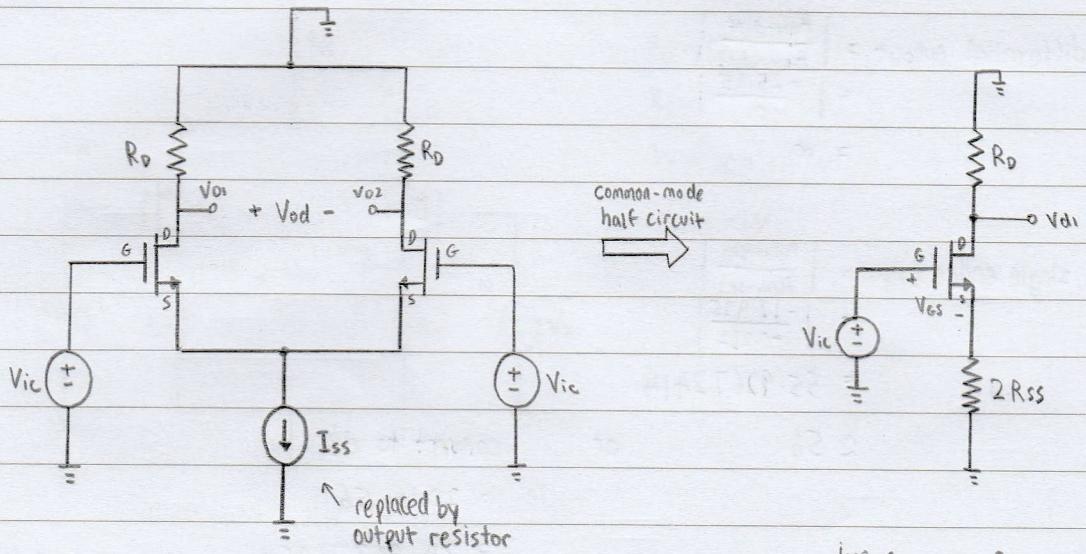
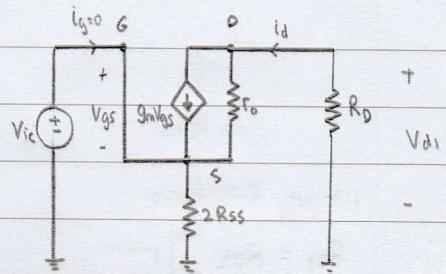
$$\begin{aligned} V_{od} &= V_{d1} - V_{d2} \\ &= 0 \end{aligned}$$



$$A_{cm-diff} = 0$$

$$V_{d1} = V_{d2}$$

$$= -g_m V_{gs} R_o$$

$$\begin{aligned} A_{cm-sei} &= \frac{V_{d1}}{V_{ic}} \\ &= -g_m V_{gs} R_o \end{aligned}$$

$$\begin{aligned} &V_{gs} + g_m V_{gs} (2R_{ss}) \\ &= -g_m V_{gs} R_o \\ &= \frac{V_{gs}(1+g_m 2R_{ss})}{(1+0.346m \times 2 \times 160k\Omega)} \\ &= -0.346m \times 75k\Omega \\ &= -0.2322771214 \end{aligned}$$

$$\approx -0.232$$

$$R_{ic} = \infty$$

CMRR

$$\text{For differential output} = \left| \frac{\text{Adm-diff}}{\text{Acm-diff}} \right| \\ = \left| \frac{-25.95}{0} \right| \\ = \infty$$

$$\text{For single ended output} = \left| \frac{\text{Adm-sei}}{\text{Acm-sei}} \right| \\ = \left| \frac{-12.975}{-0.232} \right| \\ = 55.92672414$$


$$\approx 56 \quad \text{or} \quad \text{convert to dB} \\ = 20 \log 56 \\ = 34.96376054 \\ \approx 35 \text{ dB}$$

Output Resistance

$$R_{o1} = R_{o2} \\ = r_o \parallel R_D \\ = \infty \parallel 75\text{k}\Omega \\ = 75\text{k}\Omega$$

$$R_{od} = R_{o1} + R_{o2} \\ = 2 \times 75\text{k}\Omega \\ = 150\text{k}\Omega$$

3)

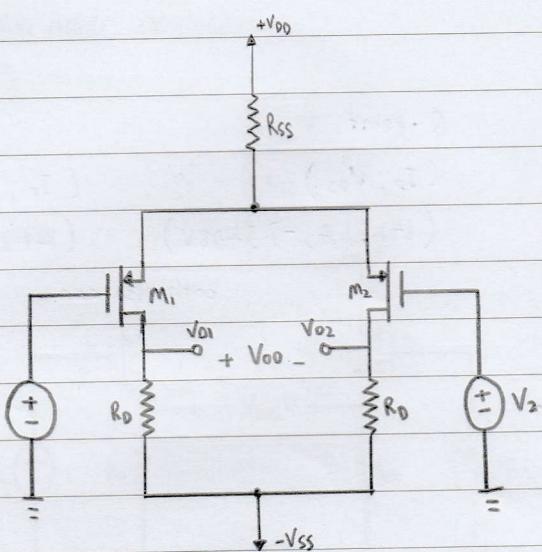

$$V_{DD} = V_{SS} = 18V$$


$$R_{SS} = 56k\Omega$$

$$R_D = 91k\Omega$$

$$k_p = 200 \mu A/V^2$$

$$V_{TP} = -1V$$

DC analysis

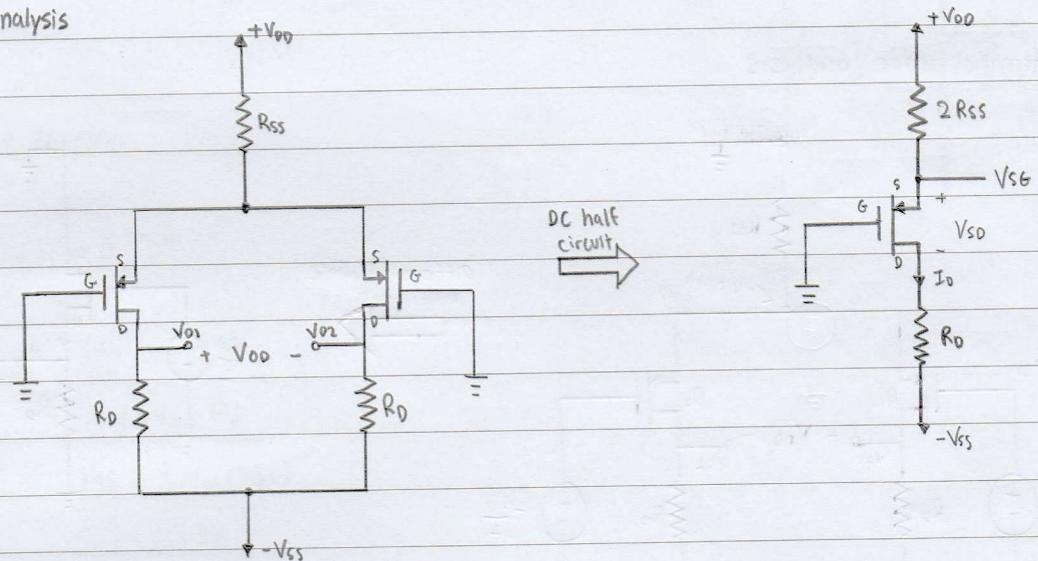

$$I_D = \frac{V_{DD} - V_{GS}}{2R_{SS}}$$

$$= \frac{18 - V_{GS}}{2(56k\Omega)} \quad - \textcircled{1}$$

$$100\mu A (V_{GS} + 1)^2 (2R_{SS}) = 18 + V_{GS}$$

$$100\mu A (2 \times 56k\Omega) (V_{GS} + 1)(V_{GS} + 1) = 18 + V_{GS}$$

$$11.2 [V_{GS}^2 + 2V_{GS} + 1] = 18 + V_{GS}$$

$$I_D = \frac{k_p}{2} (V_{GS} - V_{TP})^2$$

$$= \frac{200\mu A}{2} (V_{GS} - (-1))^2 \quad - \textcircled{2}$$

$$11.2 V_{GS}^2 + 22.4 V_{GS} - V_{GS} + 11.2 - 18 = 0$$

$$11.2 V_{GS}^2 + 21.4 V_{GS} - 6.8 = 0$$

$$V_{GS} = 0.2774648749V$$

$$\approx 0.28V \quad (\text{infeasible})$$

$$\textcircled{1}: \frac{18 - (-V_{GS})}{2R_{SS}} \quad - \textcircled{3}$$

$$\text{or} = -2.188179161V$$

$$\textcircled{3} = \textcircled{2}$$

$$\approx -2.19V$$

$$\frac{18 + V_{GS}}{2R_{SS}} = \frac{200\mu A}{2} (V_{GS} + 1)^2$$

$$I_D = \frac{18 + 2.19}{2(56k\Omega)}$$

$$= 141.1607143 \times 10^{-6} A$$

$$\approx 141.2 \mu A$$

By KVL

$$-V_{SG} + V_{SD} + I_o R_o + (-V_{SS}) = 0$$

Q-point

$$V_{SD} = V_{SG} + V_{SS} - I_o R_o$$

(I_o, V_{DS})(I_o, V_{SD})

$$= 2.19 + 18 - 141.2 \mu A (91 k\Omega)$$

(141.2 μA, -7.3408V)

(141.2 μA, 7.3408V)

$$= 7.3408 V$$

both also can

b) $g_m = \sqrt{2k_p I_o}$


$$r_o = \infty$$

$$= \sqrt{2(200 \mu A)(141.2 \mu A)}$$

$$= 0.237655212 \times 10^{-3} S$$

$$\approx 0.2376 ms$$

Differential mode analysis

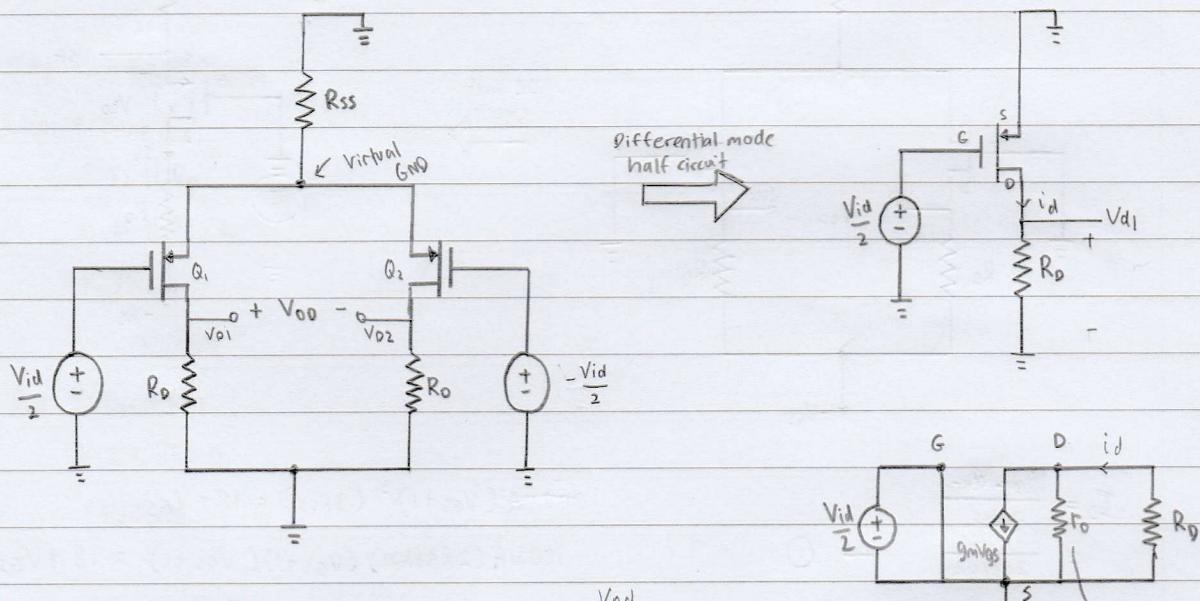

$$V_{d1} = -g_m V_{gs} R_o$$

$$= -g_m \left(\frac{Vid}{2}\right) R_o$$

$$V_{d2} = g_m \left(\frac{Vid}{2}\right) R_o$$

$$\text{Adm-diff} = \frac{V_{d1}}{Vid}$$

$$= -\frac{g_m V_{gs} R_o}{Vid}$$

$$= -g_m R_o$$

$$= -0.2376ms \times 91k\Omega$$

$$V_{od} = V_{d1} - V_{d2}$$

$$= -21.6216$$

$$V_{gs} = \frac{Vid}{2}$$

$$= -g_m \left(\frac{Vid}{2}\right) R_o - g_m \left(\frac{Vid}{2}\right) R_o$$

$$= -2g_m \left(\frac{Vid}{2}\right) R_o$$

$$= -g_m Vid R_o$$

$$\text{Adm-se1} = \frac{V_{d1}}{Vid}$$


$$= \frac{\text{Adm-diff}}{2}$$

$$= -\frac{21.6216}{2}$$

$$= -10.8108$$

$$R_{id} = \infty$$

common mode analysis

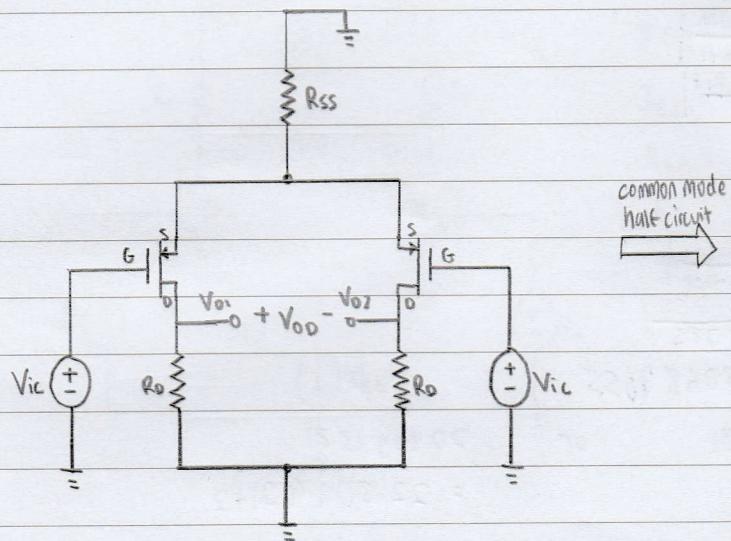


$$V_{od} = V_{d1} - V_{d2} \\ = 0$$

$$A_{cm-diff} = 0$$

$$\begin{aligned} A_{cm-sel} &= \frac{V_{d1}}{V_{IC}} \\ &= -g_m V_{gs} R_D \\ &= -g_m V_{gs} (2R_{SS}) \\ &= -g_m V_{gs} R_D \\ &= \frac{V_{gs}(1 + g_m(2R_{SS}))}{1 + g_m(2R_{SS})} \\ &= \frac{-g_m R_D}{1 + g_m(2R_{SS})} \\ &= \frac{-0.2276mS(91k\Omega)}{1 + 0.2376mS(2 \times 56k\Omega)} \\ &= -0.7830735354 \\ &\approx -0.783 \end{aligned}$$

$$R_{IC} = \infty$$

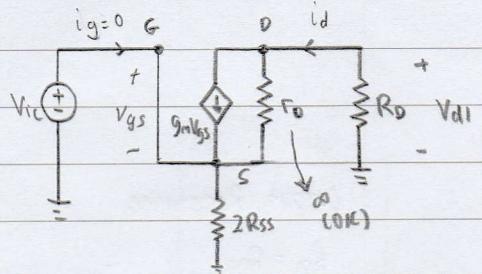

CMRR

$$\text{For differential output} = \left| \frac{\text{Adm-diff}}{\text{Acm-diff}} \right| \\ = \left| \frac{-21.6216}{0} \right| \\ = \infty$$

$$\text{For single ended output} = \left| \frac{\text{Adm-sei}}{\text{Acm-sei}} \right| \\ = \left| \frac{-10.8108}{-0.783} \right| \\ = 13.80689655 \\ \approx 13.81 \quad \text{or} \quad 20 \log 13.81 \\ = 22.80192142 \\ \approx 22.8 \text{ dB}$$

Output Resistance

$$R_{o1} = R_{o2} \\ = r_o \parallel R_p \\ = \infty \parallel 91k\Omega \\ = 91k\Omega$$

$$R_{od} = 2 \times 91k\Omega \\ = 182k\Omega$$