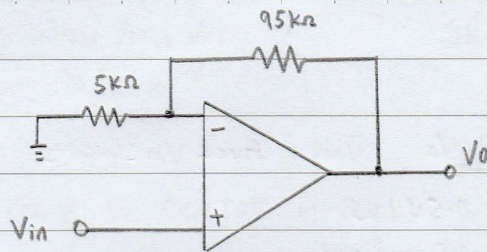


Esmund Lim

AE Tutorial 3

1a)

unity gain frequency $f_0 = 1.2 \text{ MHz}$


$$A_{vCL} = \frac{5\text{k}\Omega + 95\text{k}\Omega}{5\text{k}\Omega}$$

$$= 20$$

$$= \frac{R_1 + R_2}{R_1}$$

$$= \frac{1}{\beta}$$

$$\beta = \frac{R_1}{R_1 + R_2}$$

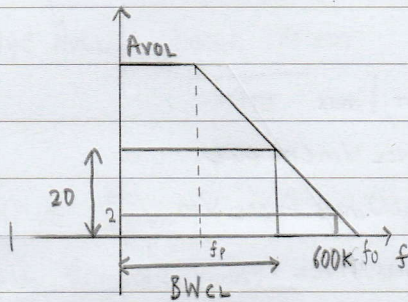gain decrease \rightarrow BW increase

$$i) f_0 = A_{vOL} f_p \leftarrow \text{dominant pole frequency}$$

$$= A_1 f_1$$

$$= A_2 f_2$$

$$= \frac{1}{\beta} BW_{CL}$$

$$ii) \frac{1}{\beta} BW_{CL} = f_0$$

$$\frac{f_0}{BW_{CL}} = \frac{1}{\beta}$$

$$\frac{1.2 \text{ MHz}}{600 \text{ kHz}} = 2$$


$$A_{vCL} = \frac{1}{\beta}$$

$$= 2 \text{ V/V}$$

$$1.2 \text{ MHz} = 20 BW_{CL}$$

$$BW_{CL} = 60 \text{ kHz}$$

b)

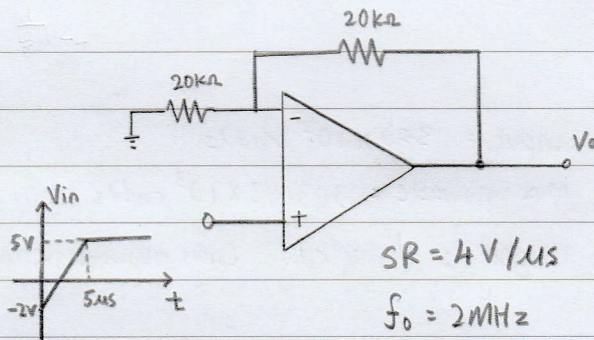

$$SR = 4 \text{ V}/\mu\text{s}$$

$$f_0 = 2 \text{ MHz}$$

$$A_{vCL} = \frac{20\text{k}\Omega + 20\text{k}\Omega}{20\text{k}\Omega}$$

$$= 2$$

$$SR \geq \frac{d}{dt} V_{OUT} |_{\text{max}}$$

$$= \frac{10 - (-4)}{5 \mu\text{s}}$$


$$= 2.8 \times 10^6 / \text{s}$$

$$= 2.8 \text{ V}/\mu\text{s}$$

 \therefore SR is $2.8 \text{ V}/\mu\text{s}$ which is smaller than the limitation

therefore no distortion of signal will occur

2)

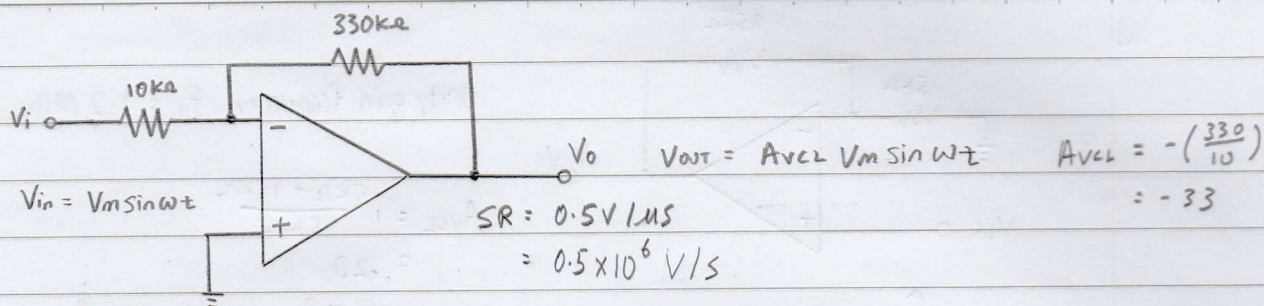

$$V_1 = 0.01 \sin(10^6 t)$$

$$SR \geq \left. \frac{d}{dt} V_{out} \right|_{max}$$

$$V_2 = 0.05 \sin(350 \times 10^3 t)$$

$$\frac{d}{dt} V_{out} = \omega A_{vcl} V_m \cos \omega t$$

$$V_3 = 0.10 \sin(200 \times 10^3 t)$$

$$\left| \frac{d}{dt} V_{out} \right|_{max} = \omega_{max} A_{vcl} V_m$$

$$V_4 = 0.20 \sin(50 \times 10^3 t)$$

$$SR \geq \omega_{max} A_{vcl} V_m$$

$$\omega_{max V_1} \leq \frac{SR}{A_{vcl} V_m}$$

$$input = 1 \times 10^6 \text{ rad/s}$$

$$Max \text{ allowable} = 1.5 \times 10^6 \text{ rad/s}$$

$$= 1515151.515$$

No distortion

$$= 1.515 \times 10^6 \text{ rad/s}$$

$$\omega_{max V_2} \leq \frac{0.5 \times 10^6}{13310.05}$$

$$input = 350 \times 10^3 \text{ rad/s}$$

$$= 303030.303 \text{ rad/s}$$

$$max \text{ allowable} = 303.03 \times 10^3 \text{ rad/s}$$

$$= 303.03 \times 10^3 \text{ rad/s}$$

signal is distorted (max allowable < input)

$$\omega_{max V_3} \leq \frac{0.5 \times 10^6}{13310.10}$$

$$input = 200 \times 10^3 \text{ rad/s}$$

$$= 151515.1515 \text{ rad/s}$$

$$max \text{ allowable} = 151.51 \times 10^3 \text{ rad/s}$$

$$= 151.51 \times 10^3 \text{ rad/s}$$

Signal is distorted (max allowable < input)

$$\omega_{max V_4} \leq \frac{0.5 \times 10^6}{13310.2}$$

$$input = 50 \times 10^3 \text{ rad/s}$$

$$= 75757.57576 \text{ rad/s}$$

$$max \text{ allowable} = 75.76 \times 10^3 \text{ rad/s}$$

$$= 75.76 \times 10^3 \text{ rad/s}$$

No distortion

The output due to V_2 and V_3 will be distorted

b) $SR \geq W_{\max} A_{vCL} V_m$

↳ cannot change

$$SR_{V_2} \geq 350 \times 10^3 | 133 | (0.05)$$

$$= 0.5775 \text{ V}/\mu\text{s}$$

$$SR_{V_3} \geq 200 \times 10^3 | 133 | (0.1)$$

$$= 0.66 \text{ V}/\mu\text{s}$$

either change the slew rate of A_{vCL}

change SR = change op-amp

change A_{vCL} = change resistor
better

choose op-amp with $0.66 \text{ V}/\mu\text{s}$ SR

ii) $A_{vCL} \leq \frac{SR}{W_{\max} V_m}$

$$A_{vCL V_2} \leq \frac{0.5 \times 10^6}{350 \times 10^3 (0.05)}$$

$$= 28.57142857$$


$$= 28.57$$

$$A_{vCL V_3} \leq \frac{0.5 \times 10^6}{200 \times 10^3 (0.1)}$$

$$= 25$$

Reduce the A_{vCL} of the present amplifier to $25 \text{ V}/\text{V}$



* gain larger, slope = steeper

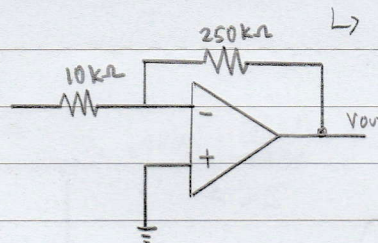

↳ exceed slew rate

change resistor instead of the whole op-amp

3a)

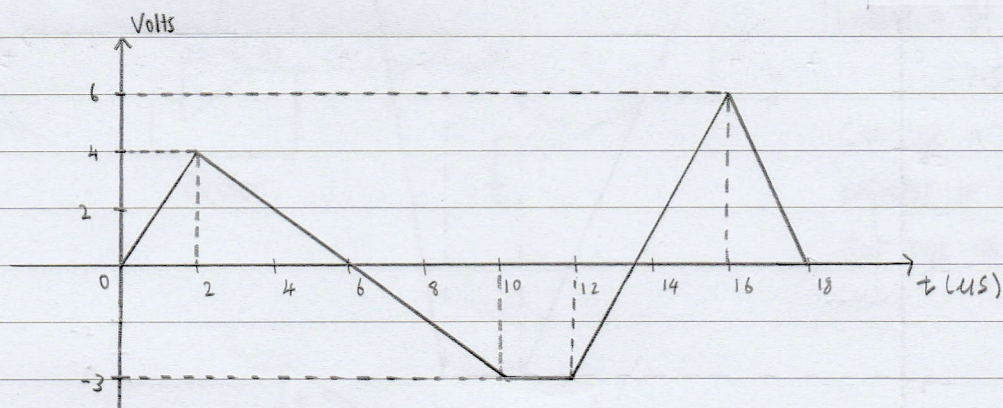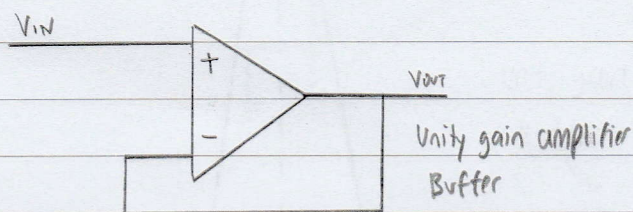

a) $SR \geq \frac{d}{dt} V_{out} |_{\max}$


$$= \frac{6-0}{2\mu\text{s}}$$

$$= 3 \text{ V}/\mu\text{s}$$


The minimum SR is $3 \text{ V}/\mu\text{s}$

The slew rate that we need for this op-amp must be at least $3 \text{ V}/\mu\text{s}$

b)

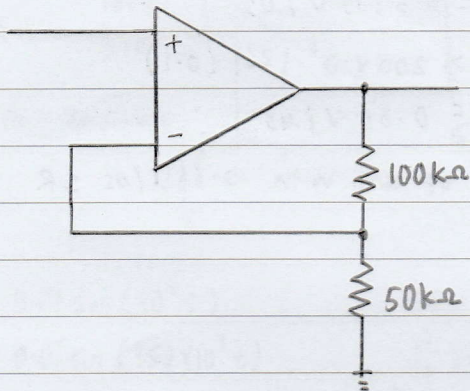

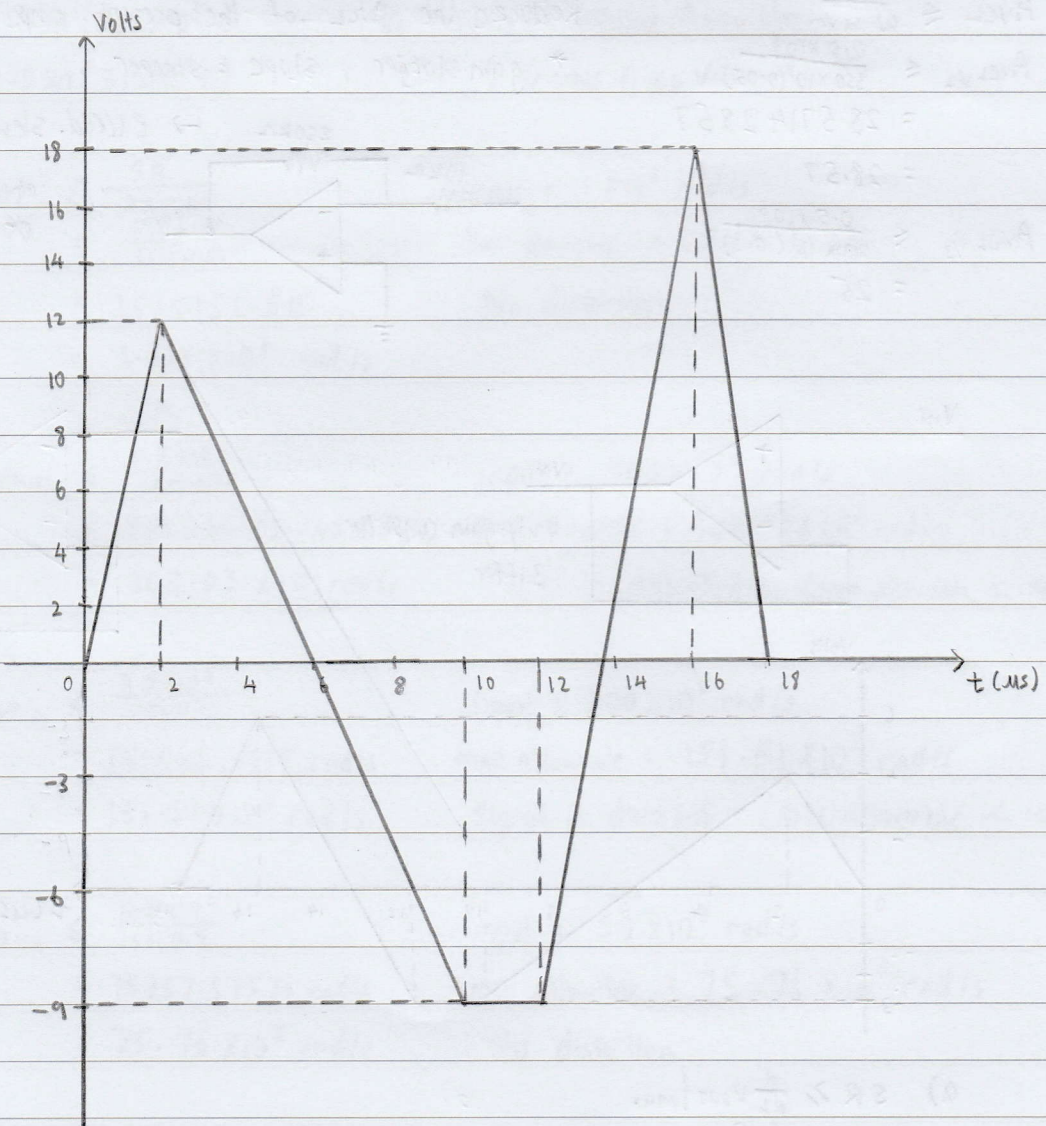
$$A_{vcl} = \frac{50k\Omega + 100k\Omega}{50k\Omega} = 3$$





$$\begin{aligned} SR &> \frac{d}{dt} V_{out} |_{max} \\ &= \frac{18-0}{2\mu s} \\ &= 9V/\mu s \end{aligned}$$

The minimum SR is 9V/μs

4)

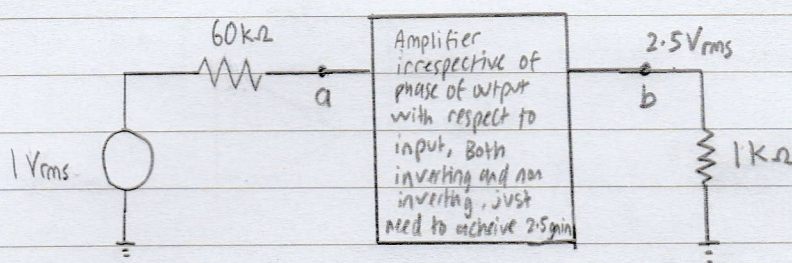


a)

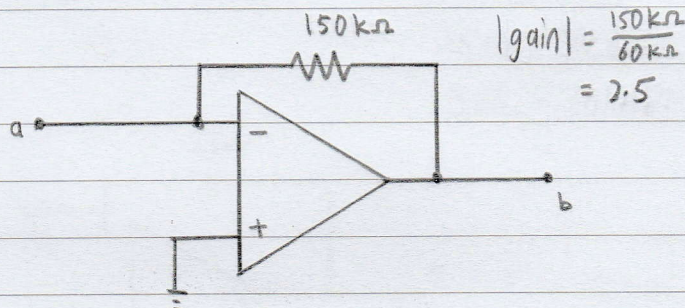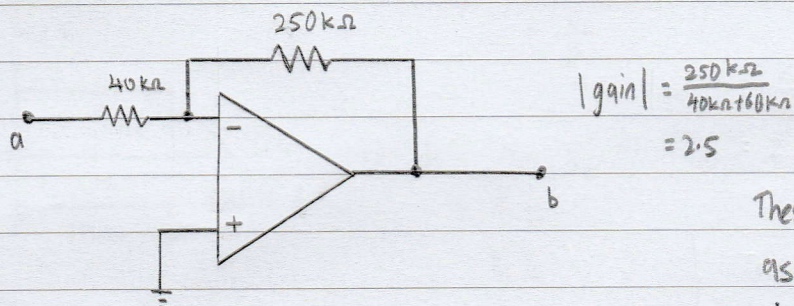

These designs are very restrictive as the gain is pre-determined by the 60kΩ resistor, and it reduces the variety of values of resistor we could use for designing the op-amp


b)

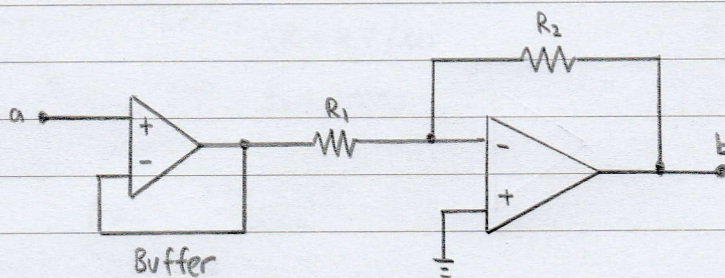

$$|gain| = \frac{R_2}{R_1} = 2.5$$

Can use a lot of values of resistor to achieve gain of 2.5
But one more op-amp is used

c)

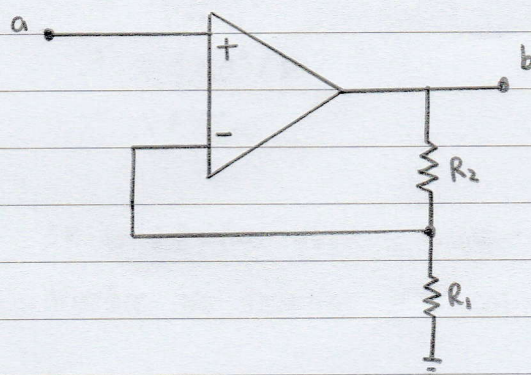

$$|gain| = 1 + \frac{R_2}{R_1} = 1.5$$

Best solution (60kΩ does not play a part in finding of gain)