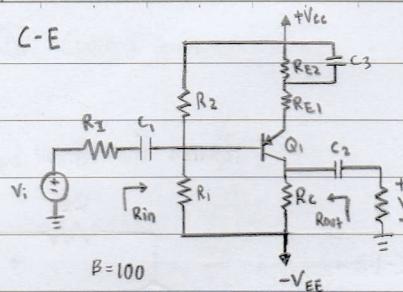


Esmund Lim


A-E Tutorial 6

1) C-E




DC Analysis

DC Equivalent circuit

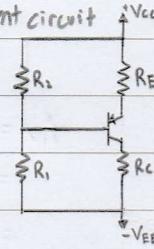


simplify by theorem

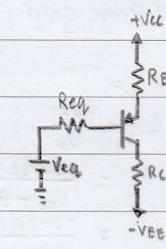


$$V_{eq} = 0V$$

Q-pt solve by KV
(I_C, V_{EC}) in TSG
($50\mu\text{A}, 10.86\text{V}$)

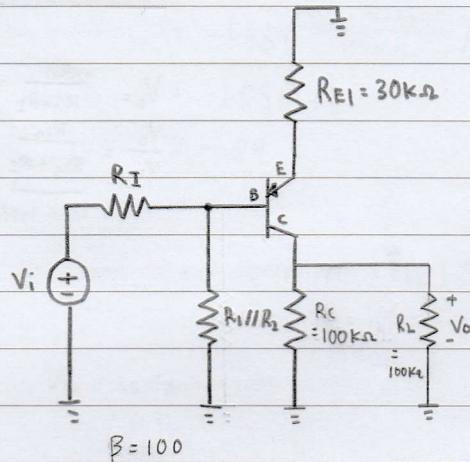AC Equivalent circuit (Cap SIC, DC voltage GND)



Small signal ac equivalent circuit

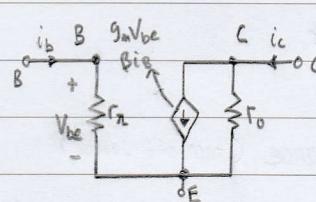

- ① input: left common
output: Right : down
② r_π : between B & E

- ③ β & r_o parallel
 r_o : between C & E
Flow from C to E
 r_o very huge
From E to C
 i_o very small

$$V_{be} = i_b r_\pi$$

$$g_m V_{be} = g_m i_b r_\pi$$

$$= \beta i_b$$

$$i_c = \beta i_b + \frac{V_{ce}}{r_o}$$

very small

very large


$$r_\pi = \frac{\beta}{g_m} \quad g_m r_\pi = \beta$$

$$g_m = \frac{i_c}{V_T} \approx 40 I_c$$


$$V_T = \frac{kT}{q} \approx 25\text{mV}$$

$$r_\pi = \frac{B}{g_m} \quad (r_\pi = \text{input})$$

$$r_o = \frac{V_A + V_{ce}}{I_c} \approx \frac{V_A}{I_c}$$

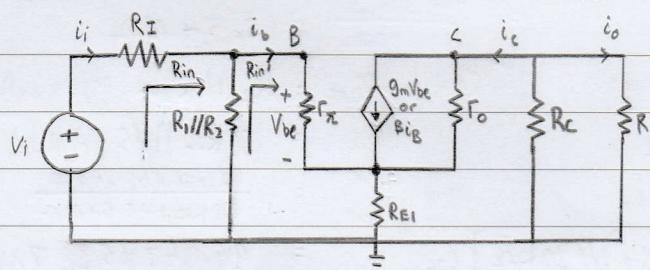

Method 2:

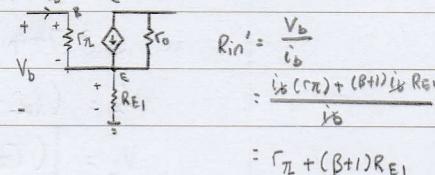

$$R_{in}' = R_1 // R_2 // R_{in}$$

$$= \frac{V_b}{i_b}$$


$$= \frac{i_b (r_\pi + (\beta + 1) i_b R_E)}{i_b}$$

$$= r_\pi + (\beta + 1) R_E$$

$$R_{in} = R_{in}' // r_\pi // R_2$$

① Input Resistance (2 methods)

Method 1: By inspection

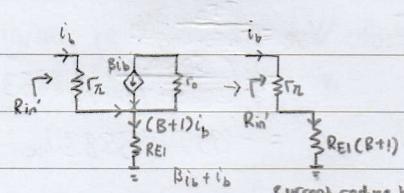

current reduce by $(\beta + 1)$ time
= voltage smaller by $(\beta + 1)$ time
∴ in order to keep the structure
increase R_E by $(\beta + 1)$ time

$$g_m = 40 I_c \quad \text{or } = \frac{I_c}{V_T}$$

$$= 40 (50\mu\text{A}) \quad = \frac{50\mu\text{A}}{25\text{mV}}$$

$$= 2\text{mS}$$

$$= 2\text{mS}$$

$$r_\pi = \frac{B}{g_m}$$

$$= \frac{100}{2\text{mS}}$$

$$= 50\text{k}\Omega$$

$$r_o = \frac{V_A + V_{ce}}{I_c}$$

$$= \frac{75\text{V} + 10.86\text{V}}{50\mu\text{A}}$$

$$= 1.7172\text{M}\Omega$$

$$\text{if } V_{CE} \ll V_A$$

$$R_{in}' = R_1 // R_2 // R_{in}$$

$$= 50\text{k}\Omega + (101)30\text{k}\Omega$$

$$= 100\text{k}\Omega \times 3.08\text{m}\Omega$$

$$= 3.08\text{m}\Omega$$

$$= 96.8553459 \times 10^3 \Omega$$

$$\approx 96.86\text{k}\Omega$$


② Voltage gain

Terminal voltage gain

$$\begin{aligned} A_{vt} &= \frac{V_o}{V_b} \\ &= \frac{-g_m V_{be} (R_c || R_L)}{V_{be} + g_m V_{be} (R_E)} \\ &= \frac{-g_m V_{be} (R_c / R_L)}{V_{be} (1 + g_m R_E)} \\ &= \frac{-g_m (R_c / R_L)}{1 + g_m R_E} \\ &= \frac{-2 \times 10^{-3} (50 \text{ k}\Omega)}{1 + (2 \times 10^{-3} \times 30 \times 10^3)} \\ &= -1.639344262 \\ &\approx -1.64 \end{aligned}$$

$$\begin{aligned} A_v &= \frac{V_b}{V_i} \times \frac{V_o}{V_b} \\ &= \left(\frac{R_{in}}{R_{in} + R_I} \right) A_{vt} \\ &= \frac{96.86 \text{ k}\Omega}{96.86 \text{ k}\Omega + 750 \text{ }\Omega} \times (-1.64) \\ &= -1.627398832 \\ &\approx -1.63 \end{aligned}$$


replaced whole circuit by R_{in}

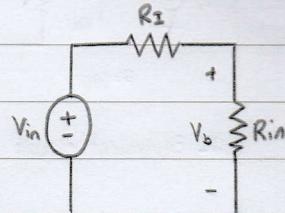

$$\begin{aligned} V_b &= \frac{R_{in}}{R_{in} + R_I} V_{in} \\ \frac{V_b}{V_i} &= \frac{R_{in}}{R_{in} + R_I} \end{aligned}$$

input loading factor

③ Output resistance (turn off source)

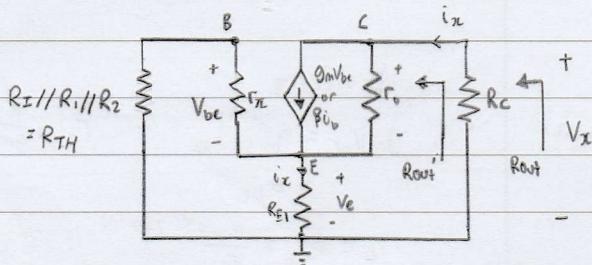

$$R_{TH} = R_L // R_1 // R_2$$

$$= R_L // 100 \text{ k}\Omega$$

$$= 750 // 100 \text{ k}\Omega$$

$$= 744.4168734 \text{ }\Omega$$

$$V_x = (i_x - g_m V_{be}) r_o + V_e$$

$$V_e = [(r_\pi + R_{TH}) // R_E] i_x$$

$$= [(50 \text{ k}\Omega + 744.4168734) // 30 \text{ k}\Omega] i_x$$

$$= 18853.7185 i_x$$

$$R_{out}' = \frac{V_x}{i_x}$$

$$= 65.53736901 \times 10^6$$

$$\approx 65.54 \text{ M}\Omega$$


$$R_{out} = R_C // R_{out}'$$

$$= 100 \text{ k}\Omega // 65.54 \text{ M}\Omega$$

$$= \frac{100 \text{ k}\Omega \times 65.54 \text{ M}\Omega}{100 \text{ k}\Omega + 65.54 \text{ M}\Omega}$$


$$= 99.84765387 \times 10^3$$

$$\approx 100 \text{ k}\Omega$$

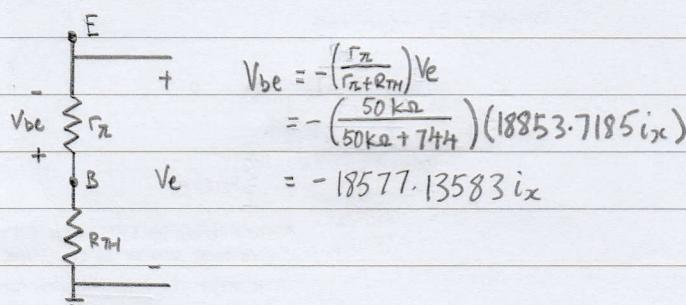

$$\begin{aligned} V_x &= (i_x - 2 \times 10^{-3} (-18577.13583 i_x)) 1.7172 \text{ M}\Omega + 18853.7185 i_x \\ &= (i_x + 37.15427166 i_x) 1.7172 \text{ M}\Omega + 18853.7185 i_x \\ &= 65.53736901 \times 10^6 i_x \end{aligned}$$

(4) Current gain

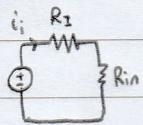

$$\begin{aligned}
 A_i &= \frac{i_o}{i_i} = \frac{\frac{V_o}{R_L}}{\frac{V_i}{R_L + R_{in}}} \\
 &= \frac{V_o}{V_i} \times \frac{R_L + R_{in}}{R_L} \\
 &= \frac{V_o}{V_i} \times \frac{R_L + R_{in}}{R_L} \\
 &= A_V \times \frac{R_L + R_{in}}{R_L} \\
 &= -1.63 \left(\frac{750 + 96.86 \text{ k}\Omega}{100 \text{ k}\Omega} \right) \\
 &= -1.591043 \\
 &\approx -1.59
 \end{aligned}$$

For small-signal operation $|V_{be}| \leq 5 \text{ mV}$

$$\begin{aligned}
 V_{be} &= i_b r_\pi \\
 &= \left(\frac{V_b}{R_{in}} \right) r_\pi \\
 &= \frac{50 \text{ k}\Omega}{3.08 \text{ M}\Omega} V_b
 \end{aligned}$$

$$0.01623376623 |V_b| \leq 5 \text{ mV}$$


$$\begin{aligned}
 |V_b| &\leq 0.308 \text{ V} \\
 &\leq 308 \text{ mV}
 \end{aligned}$$

$$A_{vt} = \frac{V_o}{V_b}$$



$$\begin{aligned}
 |V_o| &= |A_{vt} V_b| \\
 &= 1.64 |V_b| \\
 &= 1.64 \times 308 \text{ mV} \\
 &= 505.12 \text{ mV}
 \end{aligned}$$

\therefore The maximum ac output signal is 505.12 mV for small-signal operation


2)

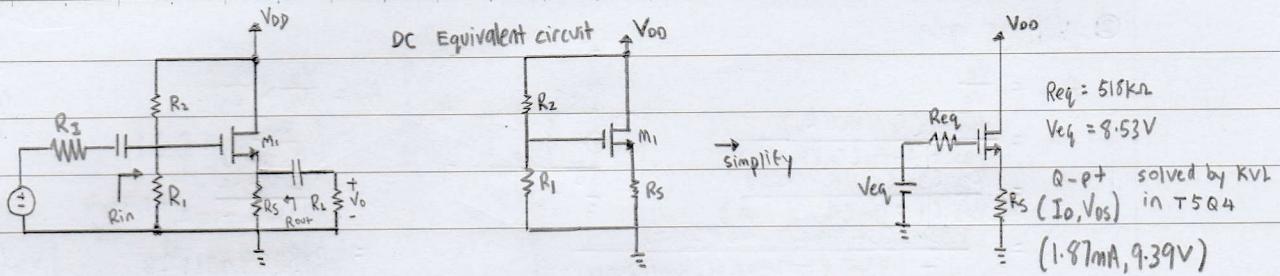

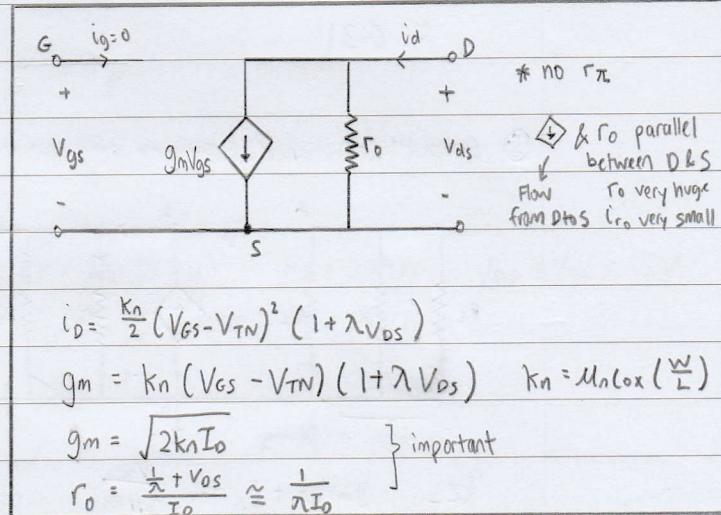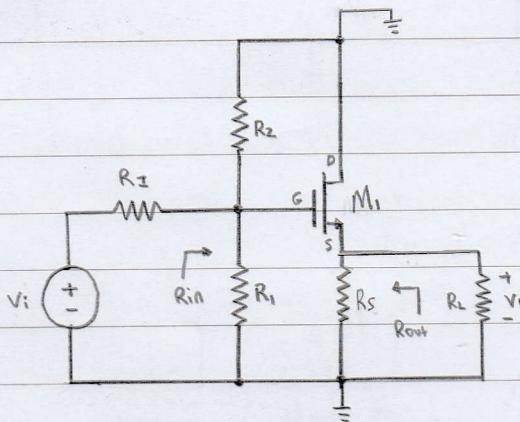ac equivalent circuit (cap SIC, DC voltage GND)



Small signal ac equivalent circuit

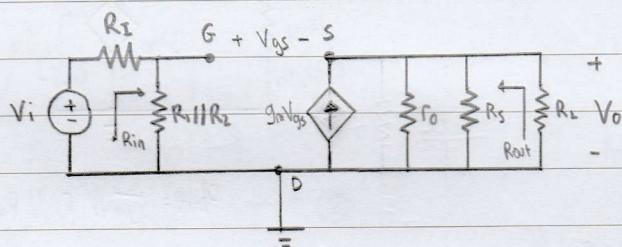

$$k_n = 1\text{mA/V}^2 \quad R_i = 100\Omega \quad R_L = 250\Omega$$

$$V_{TN} = 1\text{V} \quad R_i = 1.2\text{M}\Omega \quad V_{DD} = 15\text{V}$$

$$\lambda = 0.02\text{V}^{-1} \quad R_2 = 910\text{k}\Omega$$

$$R_s = 3\text{k}\Omega$$

$$g_m = \sqrt{2k_n I_0}$$

$$= \sqrt{2(1 \times 10^{-3})(1.87 \times 10^{-3})}$$

$$= 1.933907961 \times 10^{-3}$$

$$\approx 1.93\text{mS}$$

$$r_0 = \frac{1}{\lambda I_0}$$

$$= \frac{1}{0.02(1.87 \times 10^{-3})}$$

$$= 26.73796791 \times 10^3 \Omega$$

$$\approx 26.74\text{k}\Omega$$

① Input Resistance

$$R_{in} = R_1 // R_2$$


$$= \frac{1.2\text{M}\Omega \times 910\text{k}\Omega}{1.2\text{M}\Omega + 910\text{k}\Omega}$$

$$= 517.535545 \times 10^3 \Omega$$


$$\approx 517.54\text{k}\Omega$$

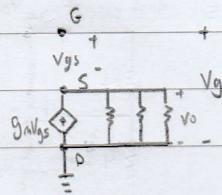(2) Voltage gain

$$\begin{aligned}
 A_{vt} &= \frac{V_o}{V_g} \\
 &= \frac{g_m V_{gs} (r_o \parallel R_s \parallel R_L)}{V_{gs} + g_m V_{gs} (r_o \parallel R_s \parallel R_L)} \\
 &= \frac{V_{gs} (g_m (r_o \parallel R_s \parallel R_L))}{V_{gs} (1 + g_m (r_o \parallel R_s \parallel R_L))} \\
 &= \frac{1.93mS (26.74k\Omega / 3k\Omega / 1250\Omega)}{1 + 1.93mS (26.74k\Omega / 3k\Omega / 1250\Omega)} \\
 &= 0.306313689 \\
 &\approx 0.31
 \end{aligned}$$



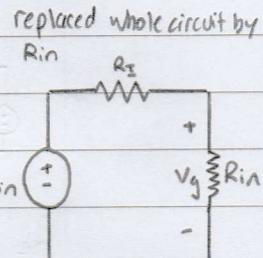
$$\begin{aligned}
 A_v &= \frac{V_o}{V_i} \times \frac{V_i}{V_g} \\
 &= \left(\frac{R_{in}}{R_{in} + R_L} \right) \times 0.31 \\
 &= \frac{517.54k\Omega}{517.54k\Omega + 100\Omega} \times 0.31 \\
 &= 0.3099401128 \\
 &\approx 0.31
 \end{aligned}$$



$$V_g = \frac{R_{in}}{R_{in} + R_L} V_{in}$$

$$\frac{V_o}{V_{in}} = \frac{R_{in}}{R_{in} + R_L}$$

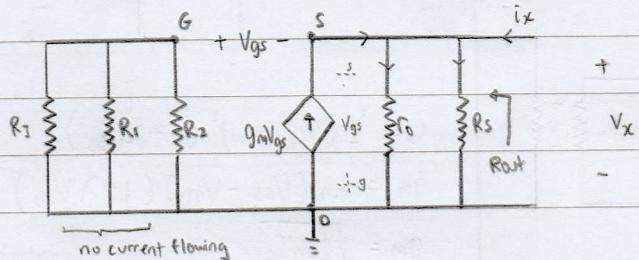(3) Output Resistance (switch off source)



$$KCL: g_m V_{gs} + i_x = \frac{V_x}{r_o \parallel R_s}$$

$$\therefore V_{gs} = -V_x$$

$$g_m (-V_x) + i_x = \frac{V_x}{r_o \parallel R_s}$$

$$i_x = \frac{V_x}{r_o \parallel R_s} + g_m V_x$$

$$= V_x \left(\frac{1}{r_o \parallel R_s} + g_m \right)$$

$$R_{out} = \frac{V_x}{i_x}$$


$$= \frac{1}{\frac{1}{r_o \parallel R_s} + g_m}$$

$$= 1 \div \left(\frac{1}{26.74k\Omega / 3k\Omega} + 1.93mS \right)$$

$$= 434.6445635 \Omega$$

$$\approx 434.64 \Omega$$

by inspection

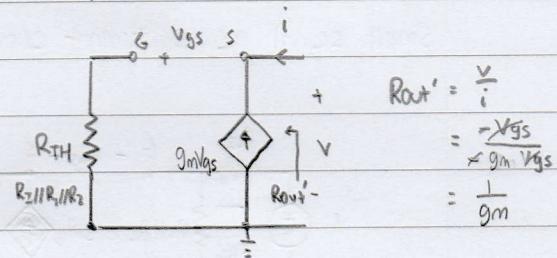

$$R_{out} = \frac{1}{g_m \parallel r_o \parallel R_s}$$

For small signal operation $V_{gs} \leq 0.2(V_{GS} - V_{TN})$

$$\text{Start with } V_{gs} = 2.92V \quad (\text{calculated in T5Q4})$$

$$\text{express in } V_g \quad V_{gs} = V_g - V_s, \quad A_{vt} = \frac{V_s}{V_g} \rightarrow V_s = V_g A_{vt}$$

$$V_{gs} \leq 0.2(2.92 - 1)$$

$$\text{express in } V_i \quad = V_g - V_g A_{vt}$$

$$\leq 0.384$$

$$= V_g (1 - A_{vt})$$

$$0.6898667027 V_i \leq 0.384$$

$$= \left(\frac{R_{in}}{R_{in} + R_L} V_{in} \right) (1 - A_{vt})$$

$$V_i \leq \frac{0.384}{0.6898667027}$$


$$= \frac{517.54k\Omega}{517.54k\Omega + 100\Omega} V_i (1 - 0.31)$$

$$\leq 556.6292713 \text{ mV}$$

$$= 0.6898667027 V_i$$


$$\leq 556.63 \text{ mV}$$

31

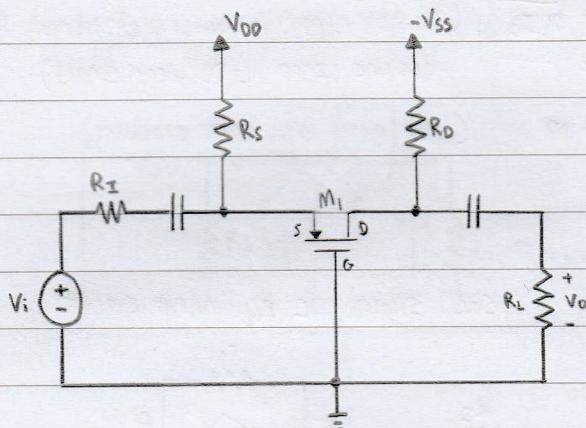

* DC analysis for
MOSFET
solve quadratic
equation

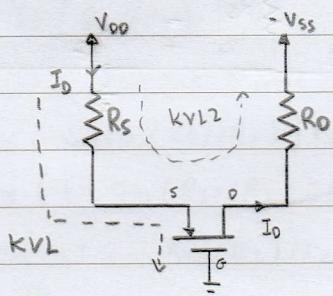DC equivalent circuit (Cap off, AC source off)



$$\begin{aligned}
 k_p &= 200 \mu A/V^2 & R_I &= 250 \Omega & V_{DD} &= V_{SS} = 15V \\
 V_{TP} &= -1V & R_S &= 68k\Omega \\
 R_L &= 200k\Omega \\
 R_D &= 43k\Omega
 \end{aligned}$$

NMOS Normal
PMOS use absolute

but PMOS will
have a negative
V_{GS}

$$I_D = \frac{k_p}{2} (|V_{GS}| - |V_{TP}|)^2$$

$$= \frac{200\mu A}{2} (|V_{GS}| - 1)^2 \quad \text{--- ①}$$

$$J_D = \frac{15 - 2.363}{69 \times 10^3} = 185.838$$

$$-V_{DD} + I_D R_S + |V_{GS}| = 0$$

$$I_D = \frac{V_{DD} - V_{GS}}{R_S}$$

$$= \frac{15 - V_{GS}}{6.8 \times 10^3} \quad \text{--- (2)}$$

sub ② into ①

$$\frac{15 - |V_{GS}|}{68 \times 10^3} = \frac{200 \mu A}{2} (|V_{GS}| - 1)^2$$

$$= 100 \mu\text{A} (|V_{GS}| - 1) (|V_{GS}| - 1)$$

$$= 100 \mu A [|V_{GS}|^2 - 2|V_{GS}| + 1]$$

$$= 100\mu A |V_{CS}|^2 - 200\mu A |V_{CS}| + 100\mu A$$

$$|5 - |V_{CE}| = \left[100\mu A |V_{CE}|^2 - 200\mu A |V_{CE}| + 100\mu A \right] \times 68 \times 10^3$$

$$= 6.8 |V_{GS}|^2 - 13.6 |V_{GS}| + 6.8$$

$$6.8 |V_{GS}|^2 - 12.6 |V_{GS}| - 8.2 = 0$$

$$|V_{S1}| = 2.363213468V \text{ or } -0.510272292V \quad (\text{infeasible because } |V_{S1}| \geq 0)$$


$\approx 2.363\sqrt{}$

$$\sqrt{f_{GS}} = -2.363V \quad (\text{without absolute})$$


$$\begin{aligned} g_m &= \sqrt{2k_p I_D} \\ &= \sqrt{2(200\mu A)(186\mu A)} \\ &= 272.7636339 \times 10^{-6} \text{ S} \\ &\approx 273 \mu \text{S} \end{aligned}$$

$$\begin{aligned} r_o &= \frac{1}{\lambda I_D} \quad (\lambda \text{ not given in this question}) \\ &\text{assume zero } (\lambda \text{ very small}) \\ &= \infty \quad (\text{as good as open circuit}) \end{aligned}$$


ac equivalent circuit

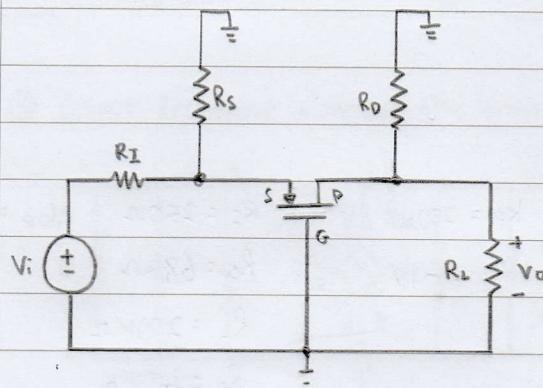

small signal ac equivalent circuit

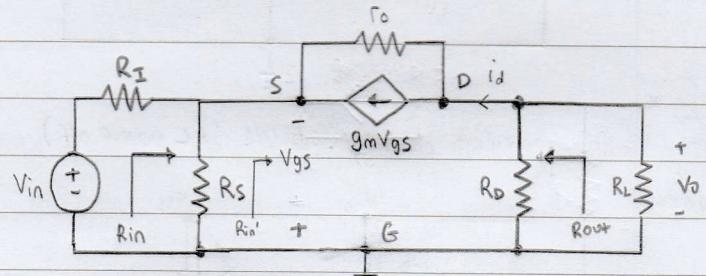

① Input Resistance

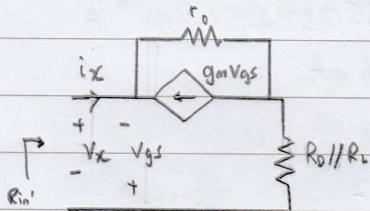

$$\begin{aligned} R_{in'} &= \frac{V_x}{i_x} \\ &= \frac{V_{GS}}{g_m V_{GS}} \end{aligned}$$

$$\begin{aligned} R_{in} &= R_S // R_{in'} \\ &= 68 \text{ k}\Omega // \frac{1}{273.4 \mu \text{s}} \\ &= 3.475771826 \times 10^3 \text{ }\Omega \\ &\approx 3.476 \text{ k}\Omega \end{aligned}$$

② Voltage gain

$$\begin{aligned} A_{vt} &= \frac{V_o}{V_s} \\ &= \frac{g_m V_{GS} (R_L // R_2)}{V_{GS}} \\ &= g_m (R_L // R_2) \\ &= 273 \mu \text{s} \left(\frac{43 \text{ k}\Omega \times 200 \text{ k}\Omega}{43 \text{ k}\Omega + 200 \text{ k}\Omega} \right) \\ &= 9.661728395 \end{aligned}$$


$$\begin{aligned} V_s &= \frac{R_{in}}{R_{in} + R_2} V_{in} \\ \frac{V_s}{V_{in}} &= \frac{R_{in}}{R_{in} + R_2} \end{aligned}$$

$$\begin{aligned} A_v &= \frac{V_o}{V_i} \times \frac{V_o}{V_s} \\ &= \left(\frac{R_{in}}{R_{in} + R_2} \right) (9.661728395) \\ &= \left(\frac{3.476 \text{ k}\Omega}{3.476 \text{ k}\Omega + 250} \right) (9.661728395) \\ &= 9.013464278 \\ &\approx 9.01 \end{aligned}$$

Current gain

$$\begin{aligned} A_i &= \frac{i_o}{i_i} \\ &= \frac{\frac{V_o}{R_L}}{\frac{V_i}{R_{in}}} \\ &= \left(\frac{V_o}{R_L} \times \frac{R_{in}}{V_i} \right) \\ &= \left(\frac{V_o}{R_L} \times \frac{R_2 + R_{in}}{V_i} \right) \\ &= \frac{V_o}{V_i} \left(\frac{R_2 + R_{in}}{R_L} \right) \\ &= 9.01 \left(\frac{250 + 3.476 \text{ k}\Omega}{200 \text{ k}\Omega} \right) \\ &= 0.1678563 \\ &\approx 0.168 \end{aligned}$$

(3) Output Resistance (turn-off source)

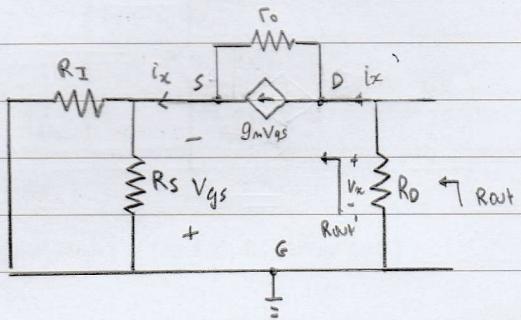

$$V_x = (i_x - g_m V_{GS}) R_0 + i_x (R_S // R_I)$$

express in i_x

$$V_{GS} = -i_x (R_S // R_I)$$

$$V_x = (i_x - g_m (-i_x (R_S // R_I))) R_0 + i_x (R_S // R_I)$$

$$= [i_x + g_m i_x (R_S // R_I)] R_0 + i_x (R_S // R_I)$$

$$= i_x (1 + g_m (R_S // R_I)) R_0 \quad \text{ignore this}$$

$$V_x = i_x (1 + g_m (R_S // R_I)) R_0$$

$$R_{out}' = \frac{V_x}{i_x}$$

$$= 1 + g_m (R_S // R_I) R_0 \rightarrow \infty$$

$$R_{out}' = \infty$$

$$R_{out} = R_{out}' // R_D$$

$$= \infty // 43k\Omega$$

$$= 43k\Omega$$

For small signal operation $|V_{GS}| \leq 0.2 (|V_{GS}| - |V_{TP}|)$


$$V_{GS} = 2.363V$$

$$\left(\frac{R_{in}}{R_I + R_{in}} \right) V_i \leq 0.2 (2.363 - 1)$$

$$\frac{3.476k\Omega}{3.476k\Omega + 250} V_i \leq 0.2 (2.363 - 1)$$

$$V_i \leq 292.2058688 \times 10^{-3} V$$

$$\leq 292.21 mV$$

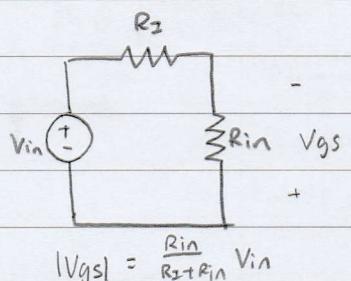

$$|V_{GS}| = \frac{R_{in}}{R_2 + R_{in}} V_{in}$$