

**Nanyang Technological University**  
**School of Electrical & Electronic Engineering**  
**EE2002 Analog Electronics – Tutorial 11**

1. (a) Derive the output resistance  $R_o$  of the cascode current mirror in Figure 1. State your assumptions for the circuit to operate with high output resistance.


(Ans:  $g_{m3}r_{o3}r_{o2}$  )

- (b) What is the lowest voltage limit at the drain of  $M_3$  if all the transistors are in the saturation region.

(Ans:  $V_{TN} + 2\sqrt{\frac{2I_{REF}}{K_n}}$  )

- (c) If  $I_{REF} = 17.5\mu\text{A}$ ,  $V_{DD} = 5\text{V}$ ,  $K_n = 75\mu\text{A/V}^2$ ,  $V_{TN} = 0.75\text{V}$ , and  $\lambda = 0.0125\text{V}^{-1}$ . Find  $R_o$  if the drain voltage of  $M_3$  is connected to  $V_{DD}$ . Calculate also the minimum voltage at the drain of  $M_3$  for all transistors to remain in the saturation region of operation.

(Ans:  $1.16\text{ G}\Omega$ ,  $2.12\text{ V}$ )

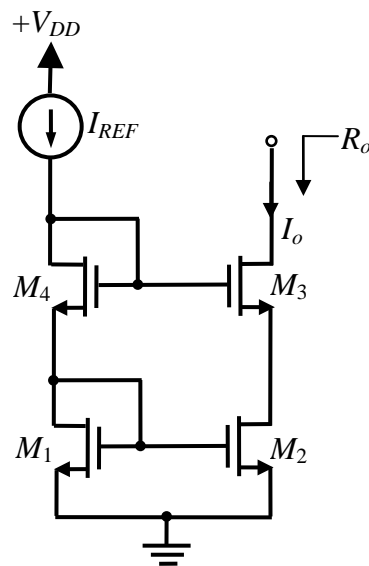

**Figure 1**

2. An amplifier has a transfer function:

$$T(s) = \frac{10^{12} s^2}{(s + 10)(s + 10^3)(s + 10^6)}$$

Sketch the Bode magnitude plot for the gain response. Use the plot to estimate the values for the amplifier gain at  $10^3\text{ rad/s}$  and  $10^6\text{ rad/s}$  respectively. What should be the actual values of the gain at these frequencies? Determine the bandwidth of the response.

(Ans:  $120\text{ dB}$ ,  $120\text{ dB}$ ,  $117\text{ dB}$ ,  $0.999 \times 10^6\text{ rad/s}$ )