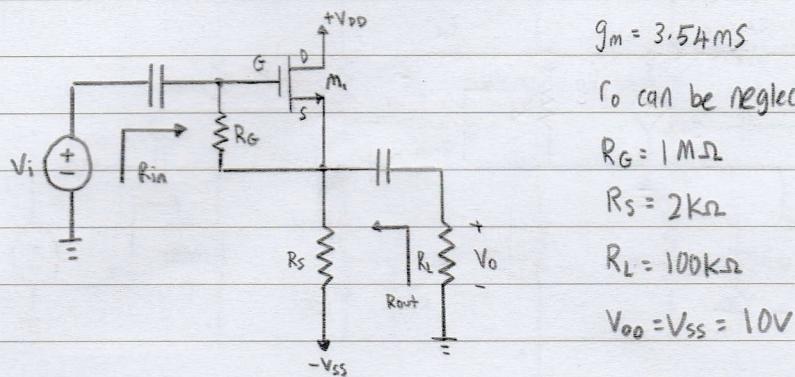



Esmund Lim

A-E Tutorial 7

## 1) Common-drain (Voltage follower)



Small signal ac equivalent circuit

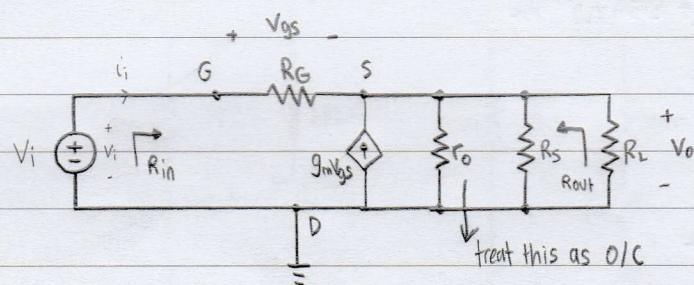

KCL

$$\frac{V_i - V_o}{1 \times 10^6} + g_m V_{gs} = \frac{V_o}{R_S // R_L}$$

$$V_{gs} = V_i - V_o$$

$$\frac{V_i}{1 \times 10^6} - \frac{V_o}{1 \times 10^6} + g_m(V_i - V_o) = \frac{V_o}{2 \text{ k}\Omega // 100 \text{ k}\Omega}$$

$$\frac{1}{1 \times 10^6} V_i - \frac{1}{1 \times 10^6} V_o + 3.54 \times 10^{-3} V_i - 3.54 \times 10^{-3} V_o = \frac{1}{2 \text{ k}\Omega // 100 \text{ k}\Omega} V_o$$

$$\frac{1}{1 \times 10^6} V_i - \frac{1}{1 \times 10^6} V_o + 3.54 \times 10^{-3} V_i - 3.54 \times 10^{-3} V_o = 0.51 \times 10^{-3} V_o$$

$$-\frac{1}{1 \times 10^6} V_o - 3.54 \times 10^{-3} V_o - 0.51 \times 10^{-3} V_o = -\frac{1}{1 \times 10^6} V_i - 3.54 \times 10^{-3} V_i$$

$$-4.051 \times 10^{-3} V_o = -3.541 \times 10^{-3} V_i$$

$$\frac{V_o}{V_i} = \frac{-3.541 \times 10^{-3}}{-4.051 \times 10^{-3}}$$

$$\therefore V_o = 0.874 V_i$$

$$A_v = 0.8741051592$$

$$\approx 0.874$$

$$R_{in} = \frac{V_i}{I_i}$$

$$= \frac{V_i}{\frac{V_i - V_o}{R_G}}$$

$$= V_i \times \frac{R_G}{V_i - V_o}$$

$$= \frac{1 \times 10^6 V_i}{V_i - V_o}$$


$$= \frac{1 \times 10^6 V_i}{V_i - 0.874 V_i}$$

$$= \frac{1 \times 10^6 V_i}{0.126 V_i}$$

$$= 7.936507937 \times 10^6 \Omega$$

$$\approx 7.94 \text{ M}\Omega$$

Output Resistance

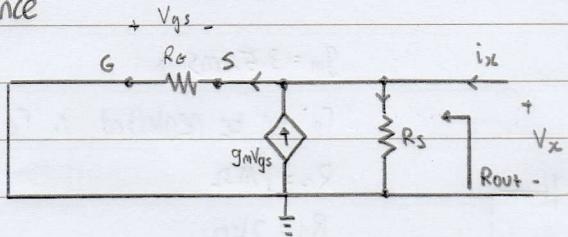

By KCL

$$i_x + g_m V_{gs} = \frac{V_x}{R_s} + \frac{V_x}{R_G}$$

$$V_{gs} = -V_x$$

$$i_x + g_m (-V_x) = \frac{V_x}{R_s} + \frac{V_x}{R_G}$$

$$i_x = \frac{V_x}{R_s} + \frac{V_x}{R_G} + g_m V_x$$

$$i_x = \frac{1}{2 \times 10^3} V_x + \frac{1}{1 \times 10^6} V_x + 3.54 \times 10^{-2} V_x$$

$$i_x = 4.041 \times 10^{-3} V_x$$

$$R_{out} = \frac{V_x}{i_x}$$

$$= \frac{1}{4.041 \times 10^{-3}}$$

$$= 247.463499 \Omega$$

$$\approx 247.46 \Omega$$

b) To achieve  $A_v = 1$ 


$$V_o = V_i$$

$$R_{in} = \frac{V_i}{V_i - V_o}$$


$$= \frac{V_i}{0}$$

$$= \infty$$

2)

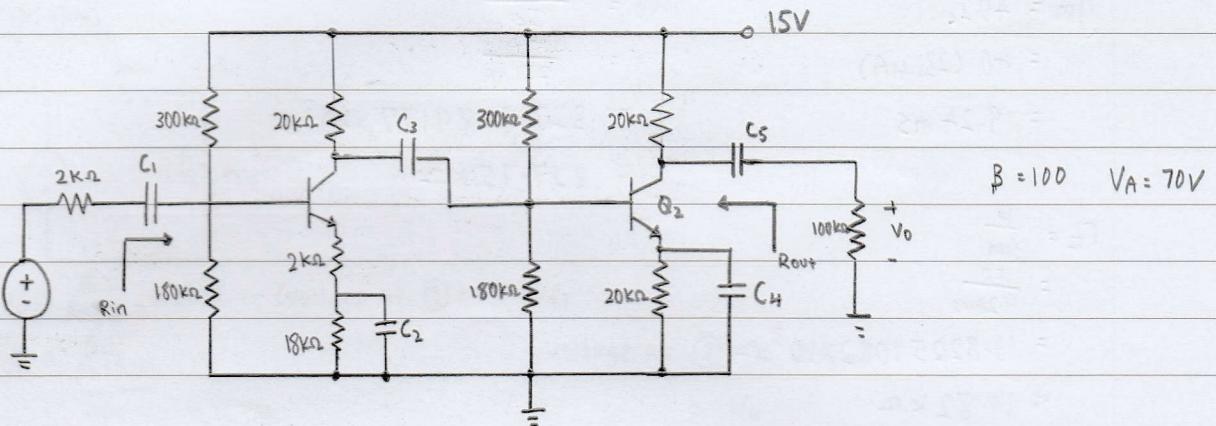


DC equivalent circuit

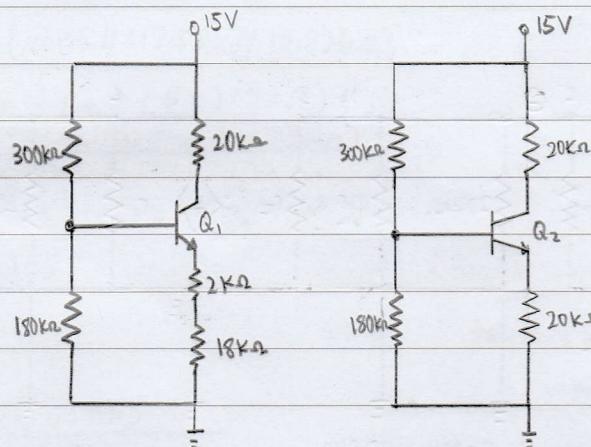

Q<sub>1</sub> and Q<sub>2</sub> will have the same Q-point

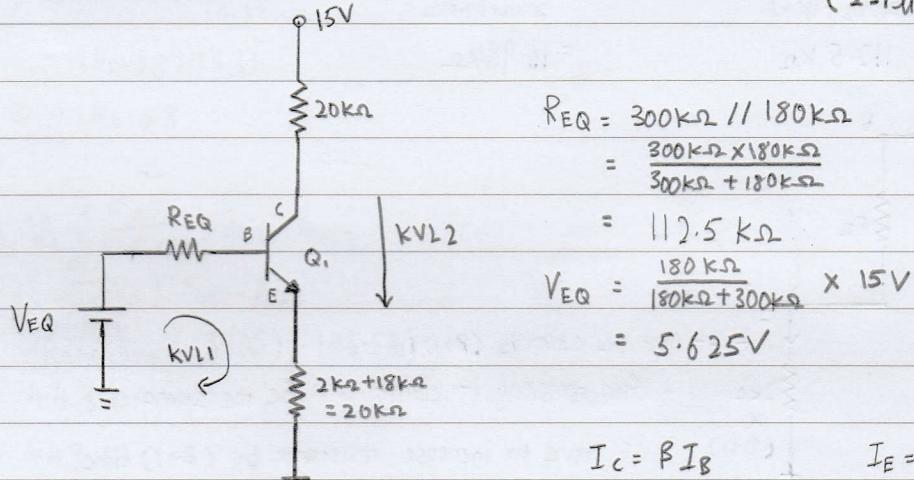Q-point  
(I<sub>c</sub>, V<sub>CE</sub>)  
(231μA, 5.71V)



$$R_{EQ} = 300\text{k}\Omega // 180\text{k}\Omega$$

$$= \frac{300\text{k}\Omega \times 180\text{k}\Omega}{300\text{k}\Omega + 180\text{k}\Omega}$$

$$= 112.5\text{k}\Omega$$

$$V_{EQ} = \frac{180\text{k}\Omega}{180\text{k}\Omega + 300\text{k}\Omega} \times 15\text{V}$$

$$= 5.625\text{V}$$

$$I_c = \beta I_B \quad I_E = (\beta+1) I_B$$

$$= 100(2.31\mu\text{A}) \quad = 101(2.31\mu\text{A})$$

$$= 231\mu\text{A} \quad = 233.31\mu\text{A}$$

By KVL 1

$$-V_{EQ} + I_B R_{EQ} + V_{BE} + I_E (20\text{k}\Omega) = 0$$

By KVL 2

$$I_B (112.5\text{k}\Omega) + I_E (20\text{k}\Omega) = V_{EQ} - V_{BE}$$

$$-15 + I_C R_C + V_{CE} + I_E (20\text{k}\Omega) = 0$$

$$I_B (112.5\text{k}\Omega) + (\beta+1) I_B (20\text{k}\Omega) = 5.625 - 0.7$$

$$V_{CE} = 15 - 231\mu\text{A} (20\text{k}\Omega) - 233.31\mu\text{A} (20\text{k}\Omega)$$

$$2132500 I_B = 4.925$$

$$= 5.7138\text{V}$$

$$I_B = 2.309495897 \times 10^{-6} \text{ A}$$

$$\approx 2.31\mu\text{A}$$

$$\approx 5.71\text{V}$$

$$g_m = 40 I_c$$

$$= 40 (231 \mu A)$$

$$= 9.24 \text{ ms}$$

$$\Gamma_0 = \frac{V_A + V_{CE}}{I_c}$$

$$= \frac{70 + 5.71}{231 \mu A}$$

$$= 327.7489177 \times 10^3 \Omega$$

$$\approx 327.75 \text{ k}\Omega$$



$$\Gamma_\pi = \frac{B}{g_m}$$

$$= \frac{100}{9.24 \text{ ms}}$$

$$= 10.82251082 \times 10^3 \Omega$$

$$\approx 10.82 \text{ k}\Omega$$

small signal ac equivalent circuit

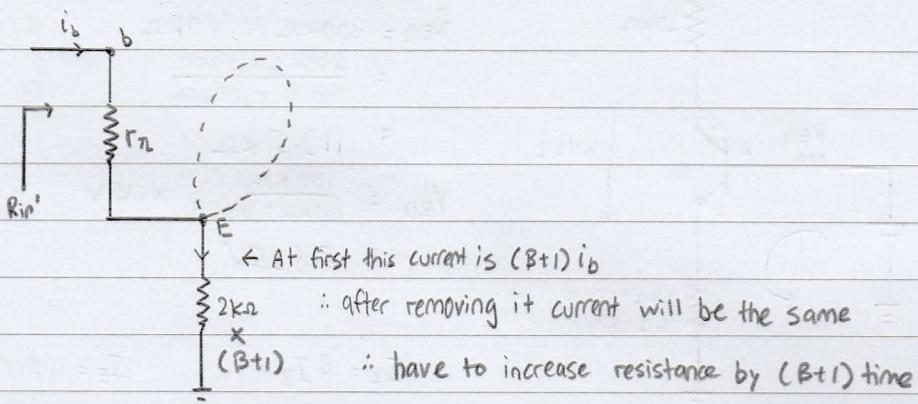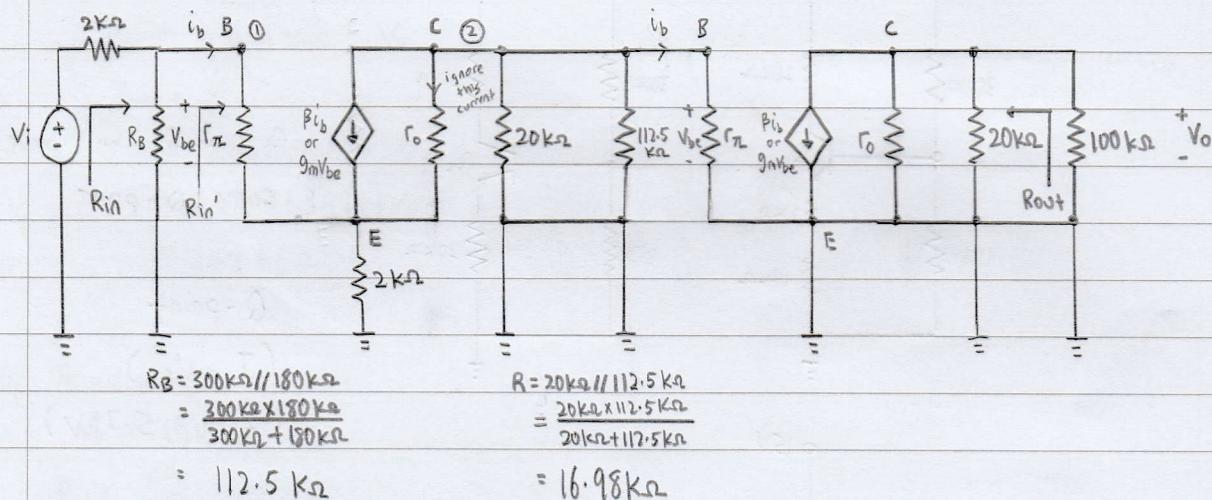


$$R_{in} = R_{in}' // R_b$$

$$= 212.82\text{k}\Omega // 112.5\text{k}\Omega$$

$$= 73.59599779 \times 10^3 \Omega$$

$$\approx 73.6 \text{ k}\Omega$$

Voltage gain

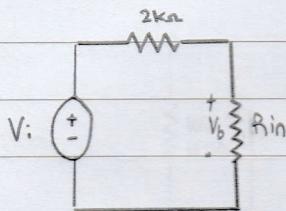

$$V_b = \frac{R_{in}}{R_{in} + 2k\Omega} \times V_i \quad (\text{voltage at } ①) \times A_{vt1}$$

$$\frac{V_b}{V_i} = \frac{R_{in}}{R_{in} + 2k\Omega} \quad = \text{voltage at } ② \times A_{vt2}$$

input loading factor  $= V_o$

$$A_{vt1} = \frac{V_o}{V_b}$$

$$= -\beta_{IE} (20k\Omega // 112.5k\Omega // 10.82k\Omega)$$

$$= -\frac{\beta_{IE} (r_\pi + (\beta+1)(2k\Omega))}{100(20k\Omega // 112.5k\Omega // 10.82k\Omega)}$$

$$= -\frac{100(327.75k\Omega // 20k\Omega // 100k\Omega)}{10.82k\Omega + 101(2k\Omega)}$$

$$= -3.10541024$$

$$\approx -3.105$$

(Reason why this gain is so small as compared

to  $A_{vt2}$  is because there is a resistor at E while the other circuit have that resistor bypassed)

$$A_{vt2} = \frac{V_o}{V_b}$$

$$= -\beta_{IE} (r_0 // 20k\Omega // 100k\Omega)$$

$$= -\frac{\beta_{IE} r_0}{10.82k\Omega}$$

$$= -\frac{100(327.75k\Omega // 20k\Omega // 100k\Omega)}{10.82k\Omega}$$

$$= -146.5817931$$

$$\approx -146.58$$

$$V_o = V_i \left( \frac{R_{in}}{R_{in} + 2k\Omega} \right) A_{vt1} \cdot A_{vt2}$$

$$\frac{V_o}{V_i} = \left( \frac{R_{in}}{R_{in} + 2k\Omega} \right) A_{vt1} \cdot A_{vt2}$$

$$A_v = \frac{73.6k\Omega}{73.6k\Omega + 2k\Omega} (-3.105)(-146.58)$$

$$= 443.0904$$

$$\approx 443.1$$

Output resistance

$$R_{out} = 20k\Omega // r_o$$


$$= 20k\Omega // 327.75k\Omega$$

$$= \frac{20k\Omega \times 327.75k\Omega}{20k\Omega + 327.75k\Omega}$$

$$= 18.84974838 \times 10^3 \Omega$$

$$\approx 18.8k\Omega$$

## 3) DC analysis

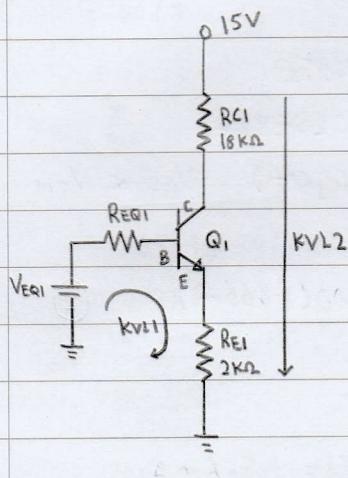

$$\begin{aligned} R_{EQ1} &= R_1 // R_2 \\ &= 820\text{k}\Omega // 100\text{k}\Omega \\ &= \frac{820\text{k}\Omega \times 100\text{k}\Omega}{820\text{k}\Omega + 100\text{k}\Omega} \\ &= 89.13043478 \times 10^3 \Omega \\ &\approx 89.13\text{k}\Omega \end{aligned}$$

$$\begin{aligned} V_{EQ1} &= \frac{R_2}{R_1+R_2} \times V_{CC} \\ &= \frac{100\text{k}\Omega}{100\text{k}\Omega + 820\text{k}\Omega} \times 15 \\ &= 1.630434783\text{V} \\ &\approx 1.63\text{V} \end{aligned}$$

By KVL1

$$\begin{aligned} -V_{EQ1} + I_B R_{EQ1} + V_{BE} + I_E R_{E1} &= 0 \\ I_B R_{EQ1} + (\beta+1) I_B R_{E1} &= V_{EQ1} - V_{BE} \\ I_B (89.13\text{k}\Omega) + (100+1)(2000) I_B &= 1.63 - 0.7 \\ I_B &= 3.194449215 \times 10^{-6} \text{A} \\ &\approx 3.19\mu\text{A} \end{aligned}$$

$I_C = \beta I_B$

$$\begin{aligned} &= 100 \times 3.19\mu\text{A} \\ &= 31.9\mu\text{A} \end{aligned}$$


$I_E = (\beta+1) I_B$

$$\begin{aligned} &= 101 \times 3.19\mu\text{A} \\ &= 322.19\mu\text{A} \end{aligned}$$

By KVL2

$$\begin{aligned} -15 + 18\text{k}\Omega(31.9\mu\text{A}) + V_{CE} + 322.19\mu\text{A}(2\text{k}\Omega) &= 0 \\ V_{CE} &= 15 - 18\text{k}\Omega(31.9\mu\text{A}) - 2\text{k}\Omega(322.19\mu\text{A}) \\ &= 8.61362\text{V} \\ &\approx 8.61\text{V} \end{aligned}$$

Q-point (31.9μA, 8.61V)

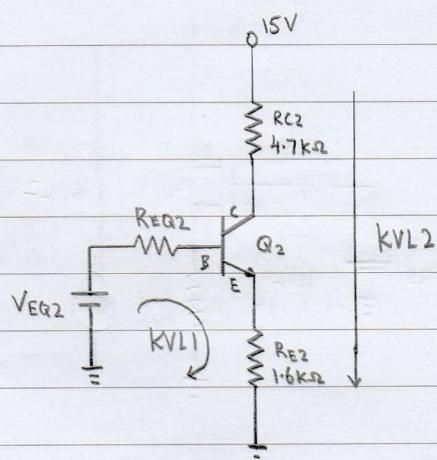

$$\begin{aligned} R_{EQ2} &= R_3 // R_4 \\ &= 160\text{k}\Omega // 43\text{k}\Omega \\ &= \frac{160\text{k}\Omega \times 43\text{k}\Omega}{160\text{k}\Omega + 43\text{k}\Omega} \\ &= 33.89162562 \times 10^3 \Omega \\ &\approx 33.89\text{k}\Omega \end{aligned}$$

$$\begin{aligned} V_{EQ2} &= \frac{R_4}{R_3+R_4} \times 15\text{V} \\ &= \frac{43\text{k}\Omega}{43\text{k}\Omega + 160\text{k}\Omega} \times 15\text{V} \\ &= 3.177339901\text{V} \\ &\approx 3.18\text{V} \end{aligned}$$

By KVL1

$$\begin{aligned} -V_{EQ2} + I_B R_{EQ2} + V_{BE} + I_E R_{E2} &= 0 \\ I_B R_{EQ2} + (\beta+1) I_B R_{E2} &= V_{EQ2} - V_{BE} \\ I_B (33.89\text{k}\Omega) + (100+1)(1600) I_B &= 3.18 - 0.7 \\ I_B &= 12.6860709 \times 10^{-6} \text{A} \\ &\approx 12.69\mu\text{A} \end{aligned}$$

$I_C = \beta I_B$

$= 100 \times 12.69\mu\text{A}$

$= 1.269\text{mA}$

$I_E = (\beta+1) I_B$


$= 101 \times 12.69\mu\text{A}$

$= 1.28\text{mA}$

By KVL2

$$\begin{aligned} -15 + 4.7\text{k}\Omega(1.269\text{mA}) + V_{CE} + 1.6\text{k}\Omega(1.28\text{mA}) &= 0 \\ V_{CE} &= 15 - 4.7\text{k}\Omega(1.269\text{mA}) - 1.6\text{k}\Omega(1.28\text{mA}) \\ &= 6.9877\text{V} \\ &\approx 6.99\text{V} \end{aligned}$$

Q-point (1.269mA, 6.99V)

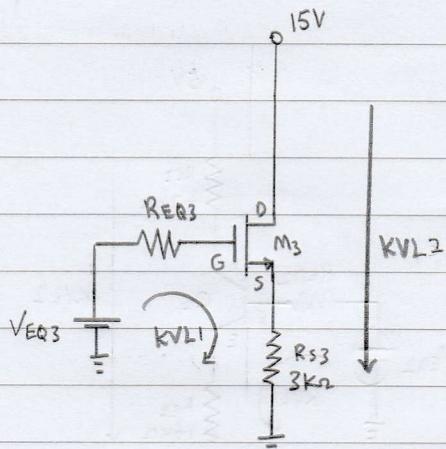 $* I_G = 0$ 

$$\text{if } I_D = 3.38 \text{ mA}$$

$$V_{GS} = 8.53 - 3000 I_D$$

$$= 8.53 - 3000(3.38 \text{ mA})$$

$$= -1.61 \text{ V} \text{ (reject)} \quad V_{GS} < V_{TN}$$

$$\text{if } I_D = 1.866 \text{ mA}$$

$$V_{GS} = 8.53 - 3000(1.866 \text{ mA})$$

$$= 2.932 \text{ V}$$

$$V_{GS} > V_{TN}$$

$$R_{EQ3} = R_S3 / R_EQ3$$

$$\therefore \text{Hence, } I_D = 1.866 \text{ mA}$$

$$= 910 \text{ k}\Omega / 1.2 \text{ M}\Omega$$

$$= \frac{910 \text{ k}\Omega \times 1.2 \text{ M}\Omega}{910 \text{ k}\Omega + 1.2 \text{ M}\Omega}$$

$$= 517.535545 \times 10^3 \text{ }\Omega$$

$$-15 + V_{DS} + I_D(3000) = 0$$

$$\approx 517.54 \text{ k}\Omega$$

$$V_{DS} = 15 - 3000(1.866 \text{ mA})$$

$$V_{EQ3} = \frac{R_EQ3}{R_S3 + R_EQ3} \times 15 \text{ V}$$

$$= 9.402 \text{ V}$$

$$= \frac{1.2 \text{ M}\Omega}{1.2 \text{ M}\Omega + 910 \text{ k}\Omega} \times 15 \text{ V}$$

$$= 8.530805687 \text{ V}$$

$$\text{Q-point } (1.866 \text{ mA}, 9.402 \text{ V})$$

$$\approx 8.53 \text{ V}$$

By KVL 1

$$-V_{EQ3} + V_{GS} + I_D R_S3 = 0$$

$$V_{GS} = V_{EQ3} - I_D R_S3$$

$$= 8.53 - 3000 I_D \quad \text{--- (1)}$$

$$I_D = \frac{k_n}{2} (V_{GS} - V_{TN})^2 \quad \text{--- (2)}$$

Sub (1) into (2)

$$I_D = \frac{k_n}{2} (8.53 - 3000 I_D - 1)^2$$

$$= \frac{1 \times 10^{-3}}{2} (7.53 - 3000 I_D)^2$$

$$= 5 \times 10^{-4} [(7.53 - 3000 I_D)(7.53 - 3000 I_D)]$$

$$= 5 \times 10^{-4} [56.7009 - 45180 I_D + 9 \times 10^6 I_D^2]$$

$$= 0.02835045 - 22.59 I_D + 4500 I_D^2$$

$$4500 I_D^2 - 22.59 I_D + 0.02835045 = 0$$


$$I_D = 3.376176311 \times 10^{-3} \text{ A} \quad \text{or} \quad 1.866045911 \times 10^{-3} \text{ A}$$

$$\approx 3.38 \text{ mA}$$

$$\approx 1.866 \text{ mA}$$

$$\begin{aligned}
 g_{m1} &= 40 I_c \\
 &= 40 (319 \mu A) \\
 &= 12.76 \text{ mS} \\
 r_{\pi 1} &= \frac{B}{g_m} \\
 &= \frac{100}{12.76 \text{ mS}} \\
 &= 7.836990596 \times 10^3 \Omega \\
 &\approx 7.84 \text{ k}\Omega \\
 \Gamma_{01} &= \frac{V_A + V_{CE}}{I_C} \\
 &= \frac{70 + 8.61}{319 \mu A} \\
 &= 246.4263323 \times 10^3 \Omega \\
 &\approx 246.43 \text{ k}\Omega \\
 g_{m2} &= 40 I_c \\
 &= 40 (1.269 \text{ mA}) \\
 &= 50.76 \text{ mS} \\
 r_{\pi 2} &= \frac{B}{g_m} \\
 &= \frac{100}{50.76 \text{ mS}} \\
 &= 1.970055162 \times 10^3 \Omega \\
 &\approx 1.97 \text{ k}\Omega \\
 \Gamma_{02} &= \frac{V_A + V_{CE}}{I_C} \\
 &= \frac{70 + 6.99}{1.269 \text{ mA}} \\
 &= 60.66981875 \times 10^3 \Omega \\
 &\approx 60.67 \text{ k}\Omega \\
 g_{m3} &= \sqrt{2k_n I_o} \\
 &= \sqrt{2(1 \times 10^{-3})(1.866 \text{ mA})} \\
 &= 1.93 \text{ mS} \\
 r_{\pi 3} &= \frac{1}{2 I_o} \\
 &= \frac{1}{0.02(1.866 \text{ mA})} \\
 &= 26.79528403 \times 10^3 \Omega \\
 &\approx 26.8 \text{ k}\Omega
 \end{aligned}$$

Small signal ac equivalent circuit

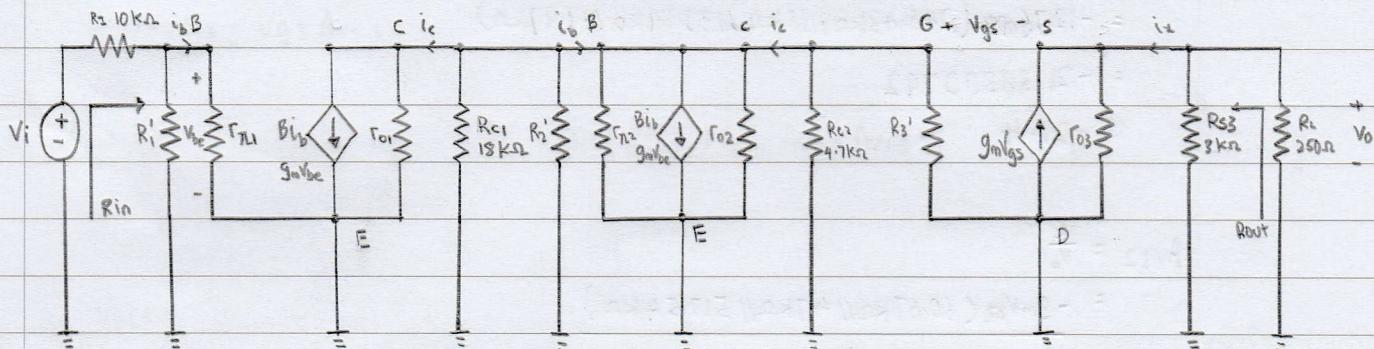

$$R_1' = R_1 // R_2$$

$$= 820 \text{ k}\Omega // 100 \text{ k}\Omega$$

$$= \frac{820 \text{ k}\Omega \times 100 \text{ k}\Omega}{820 \text{ k}\Omega + 100 \text{ k}\Omega}$$

$$= 89.13043478 \times 10^3 \Omega$$

$$\approx 89.13 \text{ k}\Omega$$

$$R_2' = R_3 // R_4$$

$$= 160 \text{ k}\Omega // 43 \text{ k}\Omega$$

$$= \frac{160 \text{ k}\Omega \times 43 \text{ k}\Omega}{160 \text{ k}\Omega + 43 \text{ k}\Omega}$$

$$= 33.89162562 \times 10^3 \Omega$$

$$\approx 33.89 \text{ k}\Omega$$

$$R_3' = R_5 // R_6$$

$$= 910 \text{ k}\Omega // 1.2 \text{ M}\Omega$$

$$= \frac{910 \text{ k}\Omega \times 1.2 \text{ M}\Omega}{910 \text{ k}\Omega + 1.2 \text{ M}\Omega}$$

$$= 517.535545 \times 10^3 \Omega$$

$$\approx 517.54 \text{ k}\Omega$$

### ① Input Resistance

$$R_{in} = R_1' // r_{\pi 1}$$


$$= 89.13 \text{ k}\Omega // 7.84 \text{ k}\Omega$$

$$= \frac{89.13 \text{ k}\Omega \times 7.84 \text{ k}\Omega}{89.13 \text{ k}\Omega + 7.84 \text{ k}\Omega}$$

$$= 7.206137981 \times 10^3 \Omega$$

$$\approx 7.21 \text{ k}\Omega$$

② Voltage gain

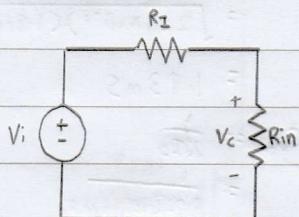

$$V_c = \frac{R_{in}}{R_{in} + R_1} \times V_i$$

$$\hookrightarrow \times A_{vt1} \times A_{vt2} \times A_{vt3} = V_o$$

$$\therefore A_v = \frac{V_o}{V_i}$$

$$= \left( \frac{R_{in}}{R_{in} + R_1} \right) A_{vt1} A_{vt2} A_{vt3}$$

$$A_{vt1} = \frac{V_c}{V_b}$$

$$= -9mV_{be} (246.43k\Omega // 18k\Omega // 33.89k\Omega // 1.97k\Omega)$$

$V_{be}$

$$= -12.76ms (246.43k\Omega // 18k\Omega // 33.89k\Omega // 1.97k\Omega)$$

$$= -21.38302792$$

$$\approx -21.4$$

$$A_{vt2} = \frac{V_c}{V_b}$$

$$= -9mV_{be} (60.67k\Omega // 4.7k\Omega // 517.54k\Omega)$$

$V_{be}$

$$= -50.76ms (60.67k\Omega // 4.7k\Omega // 517.54k\Omega)$$

$$= -219.5684203$$

$$\approx -220$$

$$\therefore A_v = \left( \frac{R_{in}}{R_{in} + R_1} \right) A_{vt1} A_{vt2} A_{vt3}$$

$$= \frac{7.21k\Omega}{7.21k\Omega + 10k\Omega} (-21.4)(-220)(0.306)$$

$$= 603.5486392$$

$$\approx 603.55$$

$$A_{vt3} = \frac{V_o}{V_g}$$

$$= g_m V_{gs} (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$V_{gs} + g_m V_{gs} (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$= g_m (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$1 + g_m (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$= 1.93ms (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$1 + 1.93ms (26.8k\Omega // 3k\Omega // 250\Omega)$$

$$= 0.3063177594$$

$$\approx 0.306$$

③ output resistance

By KCL

$$i_x + g_m V_{gs} = \frac{V_{zc}}{3k\Omega || 26.8k\Omega} \quad V_{gs} = -V_{zc}$$

$$i_x + g_m (-V_x) = \frac{V_{zc}}{3k\Omega || 26.8k\Omega}$$

$$i_{zc} - g_m V_x = \frac{V_{zc}}{3k\Omega || 26.8k\Omega}$$

$$i_{zc} = 3.706467662 \times 10^{-4} V_{zc} + 1.93 \text{ mS} (V_x)$$

$$\begin{aligned} R_{out} &= \frac{V_{zc}}{i_x} \\ &= 434.6 \Omega \end{aligned}$$

For small signal operation  $V_{gs3} \leq 0.2 (V_{G53} - V_{TN3})$

$$Av_{t3} = \frac{V_o}{V_{g3}}, \quad V_o = g_m V_{gs3} (26.8k\Omega || 3k\Omega || 250\Omega)$$

$$V_{g3} = V_{gs3} + V_o$$

$$\begin{aligned} V_{gs3} &= V_{g3} - V_o \\ &= V_{g3} - V_{g3} Av_{t3} \end{aligned}$$

$$A_V = \frac{V_o}{V_i}$$

$$= \left( \frac{R_{in}}{R_{in} + R_2} \right) Av_{t1} Av_{t2} Av_{t3}$$

$$V_o = \left( \frac{R_{in}}{R_{in} + R_2} \right) Av_{t1} Av_{t2} Av_{t3} V_i$$

$$V_{gs3} = V_{g3} (1 - Av_{t3})$$

$$= \frac{V_o}{Av_{t3}} (1 - Av_{t3})$$

$$= \left( \frac{R_{in}}{R_{in} + R_2} \right) Av_{t1} Av_{t2} V_i (1 - Av_{t3})$$

$$V_{gs3} \leq 0.2 (2.932 V - 1)$$

$$\leq 0.3864$$

$$V_i \leq 0.3864 \div \left( \frac{R_{in}}{R_{in} + R_2} \right) (Av_{t1})(Av_{t2})(1 - Av_{t3})$$

$$V_i \leq 0.3864 \div \left( \frac{7.21k\Omega}{7.21k\Omega + 10k\Omega} \right) (-21.4)(-220)(1 - 0.306)$$

$$V_i \leq 282.2843483 \mu V$$

$$\leq 282.3 \mu V$$