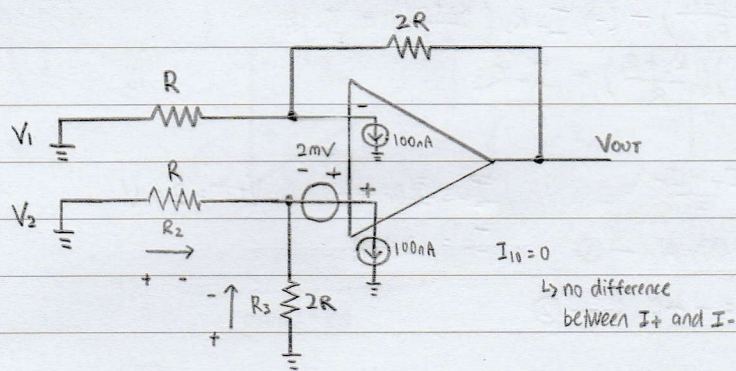


Esmund Lim

AE Tutorial 2

1) Difference Amplifier with a gain of 2 ($\frac{R_F}{R_I}$)

* Difference amplifier (Pg 43)

= scaling subtractor

$$R_F = R_3 \quad R_I = R_2$$

$$V_{OUT} = V_{OUT}|_{V_{I0}} + V_{OUT}|_{I_+} + V_{OUT}|_{I_-}$$

$$= V_{I0} \left(\frac{2R+R}{R} \right) + (-) I_+ (2R||R) \left(\frac{2R+R}{R} \right) + I_- (2R)$$

$$= V_{I0} \left(\frac{2R+R}{R} \right) - I_+ \left(\frac{2R(R)}{2R+R} \right) \left(\frac{2R+R}{R} \right) + I_- (2R)$$

$$= V_{I0} \left(\frac{2R+R}{R} \right) - I_+ (2R) + I_- (2R)$$

$$= V_{I0} \left(\frac{2R}{R} + \frac{R}{R} \right) - I_+ (2R) + I_- (2R)$$

$$= V_{I0} (2+1) - I_+ (2R) + I_- (2R)$$

$$= V_{I0} (3) - 100nA (2R) + 100nA (2R)$$


$$= V_{I0} (3)$$

$$= 2mV (3)$$

$$= 6mV$$

2)


a)

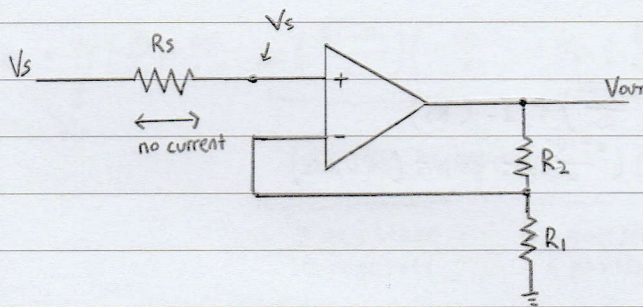

op-amp is ideal

$$V_{OUT} = V_S \left(\frac{R_2 + R_1}{R_1} \right)$$

b)

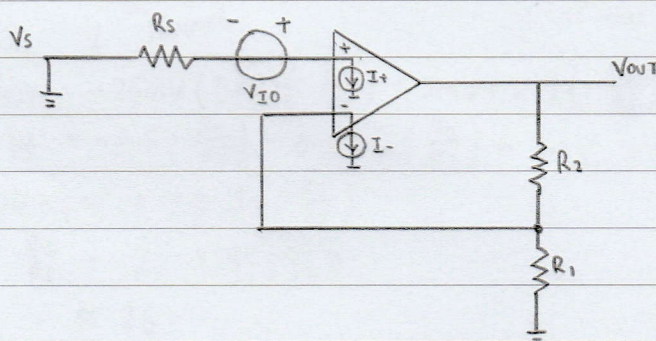


$$\begin{aligned} V_{OUT} &= V_{I0} \left(\frac{R_2 + R_1}{R_1} \right) + (-) I_+ (R_S) \left(\frac{R_2 + R_1}{R_1} \right) \\ &\quad + I_- (R_2) \\ &= V_{I0} \left(\frac{R_2 + R_1}{R_1} \right) - I_+ R_S \left(\frac{R_2 + R_1}{R_1} \right) \\ &\quad + I_- R_2 \end{aligned}$$

$$\begin{aligned}
 c) \quad V_{OUT} &= V_{OUT}|_{V_S} + V_{OUT}|_{V_{IO}} + V_{OUT}|_{I_+} + V_{OUT}|_{I_-} \\
 &= V_S \left(\frac{R_2 + R_1}{R_1} \right) + V_{IO} \left(\frac{R_2 + R_1}{R_1} \right) + (-) I_+ R_S \left(\frac{R_2 + R_1}{R_1} \right) + I_- R_2 \\
 &= (V_S + V_{IO} - I_+ R_S) \left(\frac{R_2 + R_1}{R_1} \right) + I_- R_2
 \end{aligned}$$

$$\begin{aligned}
 d) \quad R_1 &= 25 \text{ k}\Omega & I_{BIAS} &= \frac{I_+ + I_-}{2} & I_+ &= 80 \text{ nA} & V_{IO} &= 2 \text{ mV} \\
 R_2 &= 100 \text{ k}\Omega & &= 100 \text{ nA} - \text{①} & I_- &= 120 \text{ nA} \\
 & & I_+ - I_- &= -40 \text{ nA} - \text{②}
 \end{aligned}$$

$$\begin{aligned}
 V_{OUT} &= V_{IO} \left(\frac{R_1 + R_2}{R_1} \right) - I_+ R_S \left(\frac{R_2 + R_1}{R_1} \right) + I_- R_2 \\
 0 &= 2 \text{ mV} \left(\frac{25 \text{ k}\Omega + 100 \text{ k}\Omega}{25 \text{ k}\Omega} \right) - 80 \text{ nA} (R_S) \left(\frac{100 \text{ k}\Omega + 25 \text{ k}\Omega}{25 \text{ k}\Omega} \right) + 120 \text{ nA} (100 \text{ k}\Omega) \\
 4 \times 10^{-7} R_S &= 0.022 \\
 R_S &= 55 \text{ k}\Omega
 \end{aligned}$$


3)

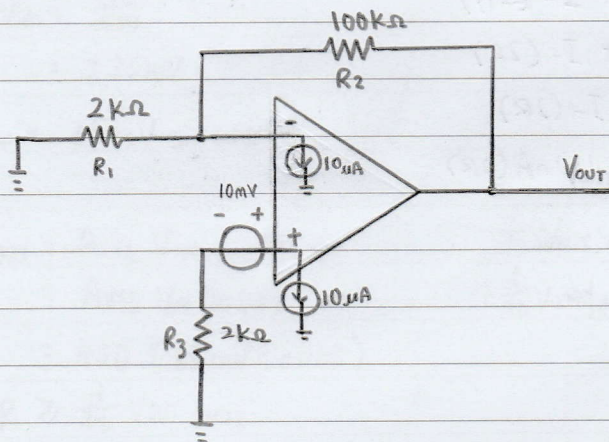slew rate = $1 \text{ V} / \mu\text{s}$

→ not used in this question as this question is for DC component and slew rate is for AC signal that is moving

$$\begin{aligned}
 V_{OUT} &= V_{OUT}|_{V_{IO}} + V_{OUT}|_{I_+} + V_{OUT}|_{I_-} \\
 &= V_{IO} \left(\frac{R_1 + R_2}{R_1} \right) + (-) I_+ (R_3) \left(\frac{R_1 + R_2}{R_1} \right) + I_- (R_2) \\
 &= 10 \text{ mV} \left(\frac{2 + 100}{2} \right) + (-) 10 \mu\text{A} (2 \text{ k}\Omega) \left(\frac{2 + 100}{2} \right) + 10 \mu\text{A} (100 \text{ k}\Omega) \\
 &= 0.49 \text{ V} \\
 &= 490 \text{ mV}
 \end{aligned}$$

→ The output has a DC voltage of 490mV caused by the non-ideal input source

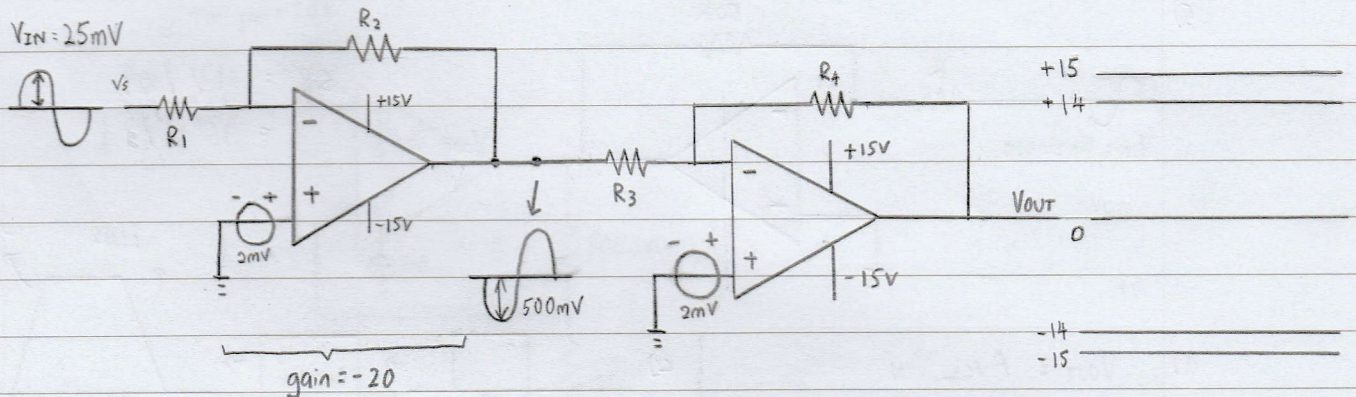4) $V_{IN} = 25\text{mV}$ 

$$a) V_{OUT} = V_{OUT}/V_S + V_{OUT}/V_{IO} + V_{OUT}/V_{IN}$$

$$= V_S \left(-\frac{R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_1+R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_3+R_4}{R_3} \right)$$

$$V_{OUT1} = V_S \left(-\frac{R_2}{R_1} \right) + V_{IO} \left(\frac{R_1+R_2}{R_1} \right)$$

$$V_{OUT2} = V_S \left(-\frac{R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_2+R_1}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_3+R_4}{R_3} \right)$$

$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) - V_{IO} \left(\frac{R_1+R_2}{R_1} \right) \left(\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_3+R_4}{R_3} \right)$$

$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) + V_{IO} \left[\left(\frac{R_1+R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + \frac{R_3+R_4}{R_3} \right]$$

$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) + V_{IO} \left[\frac{R_1}{R_1} \left(-\frac{R_4}{R_3} \right) + \frac{R_2}{R_1} \left(-\frac{R_4}{R_3} \right) + \frac{R_3}{R_3} + \frac{R_4}{R_3} \right]$$

$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) + V_{IO} \left[-\frac{R_4}{R_3} - \frac{R_2 R_4}{R_1 R_3} + 1 + \frac{R_4}{R_3} \right]$$

$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) + V_{IO} \left[1 - \frac{R_2 R_4}{R_1 R_3} \right]$$


$$= V_S \left(\frac{R_2 R_4}{R_1 R_3} \right) + V_{IO} - V_{IO} \left[\frac{R_2 R_4}{R_1 R_3} \right]$$

$$= \frac{R_4}{R_3} \left[\frac{R_2}{R_1} V_S - \frac{R_2}{R_1} V_{IO} \right] + V_{IO}$$

$$b) V_{OUT} = V_S \left(-\frac{R_2}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_2+R_1}{R_1} \right) \left(-\frac{R_4}{R_3} \right) + V_{IO} \left(\frac{R_3+R_4}{R_3} \right)$$

 \downarrow
 V_{IN}

DC component

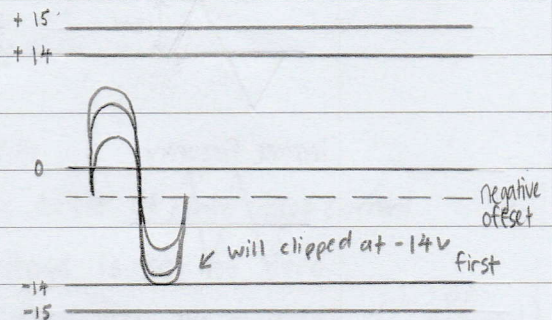2 gain stage
(negative)1 gain stage
(positive)net value = negative
DC offsetnegative
because
inverted

$$V_{OUT} = -25\text{mV} \left(-20 \right) \left(-\frac{R_4}{R_3} \right) + 2\text{mV} \left(21 \right) \left(-\frac{R_4}{R_3} \right) + 2\text{mV} \left(1 + \frac{R_4}{R_3} \right)$$

$$-14 = -0.5 \left(\frac{R_4}{R_3} \right) - 0.042 \left(\frac{R_4}{R_3} \right) + 2\text{mV} + 0.002 \left(\frac{R_4}{R_3} \right)$$


$$-14 - 2\text{mV} = -0.54 \left(\frac{R_4}{R_3} \right)$$

$$\frac{R_4}{R_3} = 25.92962963$$

$$\approx 26$$

 \therefore second-stage gain = 26 v/v

5)

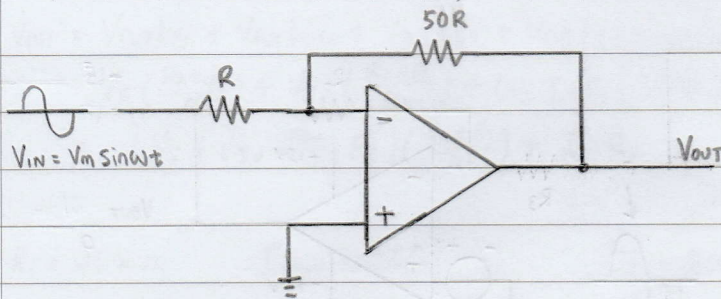

$$SR = 1V/\mu s$$

$$= 10^6 V/s$$

a)

$$V_{OUT} = A_{VOL} V_{IN}$$

$$= A_{VOL} V_m \sin \omega t$$

$$\frac{d}{dt} V_{OUT} = \omega A_{VOL} V_m \cos \omega t$$

$$SR = \left| \frac{d}{dt} V_{OUT} \right|_{\max}$$

$$= \omega A_{VOL} V_m (1)$$

$$SR \geq \left| \frac{d}{dt} V_{OUT} \right|_{\max}$$

$$SR \geq \omega A_{VOL} V_m$$

$$\omega_{\max} = \frac{SR}{A_{VOL} V_m}$$

(max frequency that the signal
can go through without distortion)

$$f = \frac{\omega}{2\pi}$$


$$f_{\max} = \frac{SR}{2\pi A_{VOL} V_m}$$

$$= \frac{10^6 V/s}{2\pi (50)(10mV)}$$

$$= 318.3098862 \times 10^3 \text{ Hz}$$

$$= 318 \text{ kHz}$$


c)

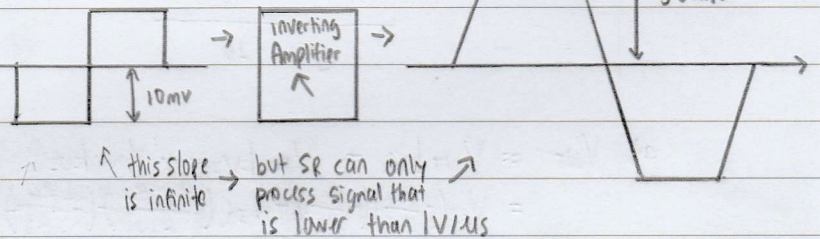

* if frequency increase



output

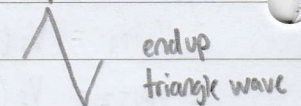


frequency = answer
in part B
500kHz


increase beyond
this

input → output
not linear related → amplitude drop

b) input

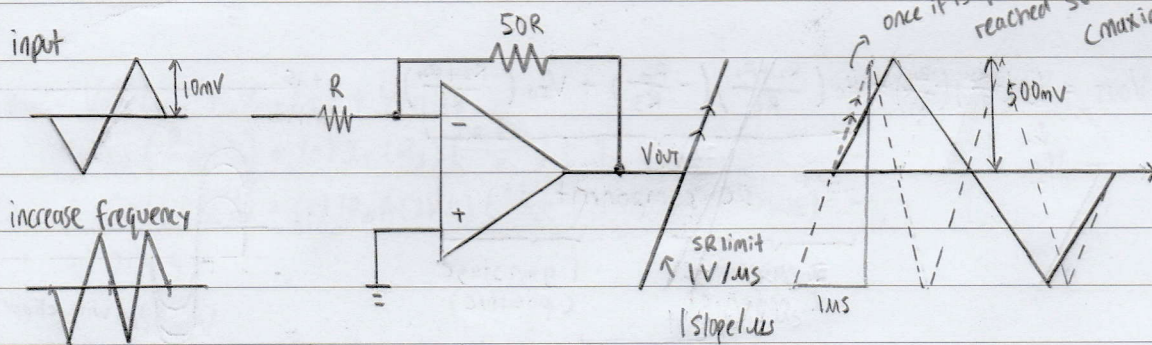

increase frequency

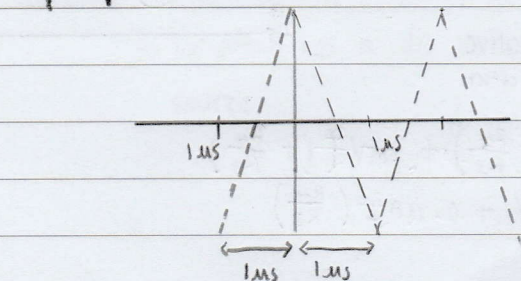

$$f = \frac{1}{T}$$

$$= \frac{1}{2\mu s}$$

$$= 500 \text{ kHz}$$

$$f \leq 500 \text{ kHz}$$

Sine wave = 318kHz


why?

triangle wave = 500kHz

Sine wave zero crossing a lot steeper than triangle wave
∴ triangle wave can move on to a higher frequency

6)


For part (B)

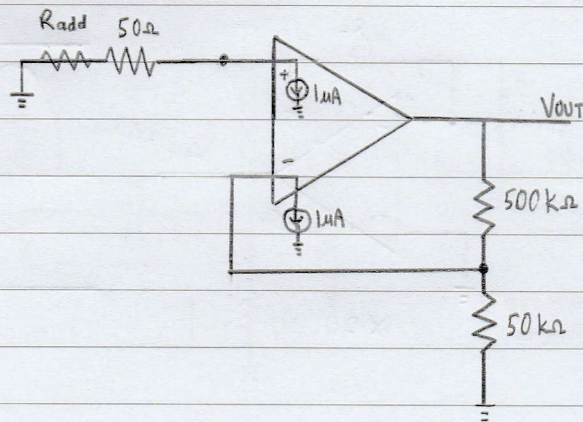

$$\begin{aligned}
 V_{out|oc} &= V_{out|I_+} + V_{out|I_-} \\
 &= -I_+(50\Omega)(11) + I_-(500k\Omega) \\
 &= -1\mu A(50)(11) + 1\mu A(500k\Omega) \\
 &= 0.49945V \\
 &= 499.45mV
 \end{aligned}$$

$$\begin{aligned}
 b) \quad V_{out|oc} &= V_{out|I_+} + V_{out|I_-} \\
 0 &= -I_+(R_{add} + 50)(11) + I_-(500k\Omega) \\
 &= -1\mu A(R_{add} + 50)(11) + 1\mu A(500k\Omega) \\
 &= \left[-1\mu A R_{add} + \left(-\frac{1}{20000}\right) \right](11) + 0.5 \\
 1.1 \times 10^{-5} R_{add} &= -\frac{11}{20000} + 0.5 \\
 R_{add} &= 45404.54545\Omega \\
 &= 45.4k\Omega
 \end{aligned}$$

Page 20

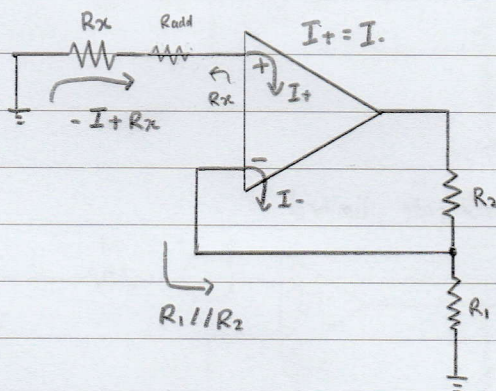if $R_x = R_1 || R_2$

cancels the effect of input bias current

Input voltage is set to zero

→ Both end will see the same thing (no input differential)

$$V_+ = V_- \quad V_+ - V_- = 0 \quad \therefore \text{output} = 0$$

if and only if $I_+ = I_-$


$$50 + R_{add} = R_1 || R_2$$

$$R_{add} = R_1 || R_2 - 50$$

$$= 50k\Omega || 500k\Omega - 50$$

$$= 45.4k\Omega$$

7)

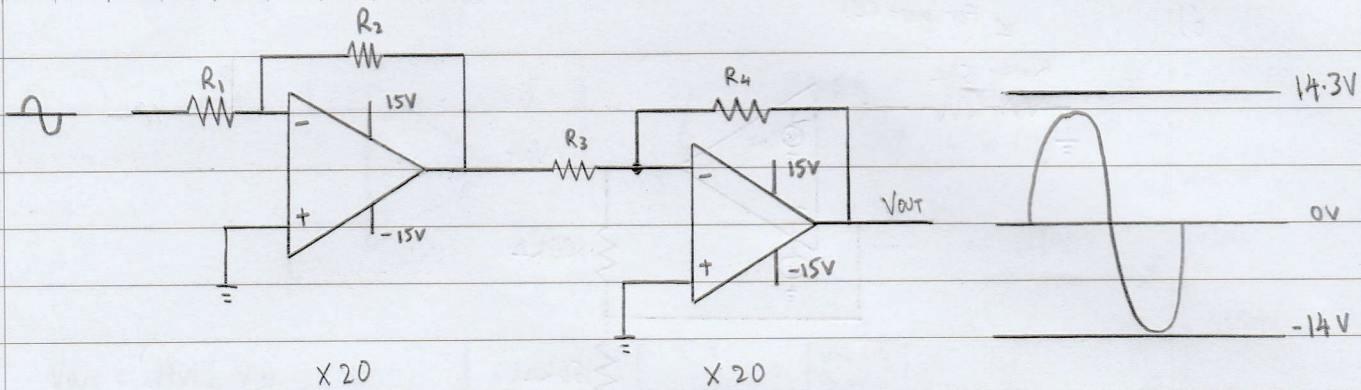

$$SR = 1V/\mu s$$

$$\pm V_{OUT} = \pm V_{IN}(-20)(-20)$$

$$\pm 14 = \pm V_{IN}(400)$$

$$\pm V_{IN} = \frac{\pm 14}{400}$$

$$= \pm 35mV$$

$$V_{IN} = 35mV \sin \omega t$$

$$\begin{aligned} b) \quad V_{OUT} &= A_{VOL} V_{IN} \\ &= A_{VOL} V_m \sin \omega t \\ &= 400 (35mV \sin \omega t) \end{aligned}$$

$$\frac{d}{dt} V_{OUT} = \omega A_{VOL} V_m \sin \omega t$$

$$\frac{d}{dt} V_{OUT} |_{max} = \omega A_{VOL} V_m$$

$$= 2\pi f_{max} A_{VOL} V_m$$

$$SR \geq \frac{d}{dt} V_{OUT} |_{max}$$

$$\begin{aligned} f_{max} &= \frac{SR}{2\pi A_{VOL} V_m} \\ &= \frac{10^6}{2\pi (400)(35mV)} \end{aligned}$$

$$= 11368.21022 \text{ Hz}$$

$$\approx 11.368 \text{ kHz}$$

$$\approx 11.4 \text{ kHz}$$

→ anything higher than this
the output become slew rate limited