

TUTORIAL 4 (with answers at the back)

- 1.a) Determine the empirical diode junction equation for a 1N4005 diode given the following voltage and current values:
 $V_{D1} = 0.6\text{V}$ @ $I_{D1} = 2.3\text{mA}$
 $V_{D2} = 0.8\text{V}$ @ $I_{D2} = 245\text{mA}$
- 1.b) Use the empirical diode junction equation, obtained in 1(a), to calculate the diode voltage V_D for a 1N4005 diode when the diode currents is
 $I_D = 20\text{mA}$
 $I_D = 300\text{mA}$
- 1.c) A 1N4005 diode is used in the circuit shown in Fig.1, determine the diode voltage and current by means of successive iteration method.

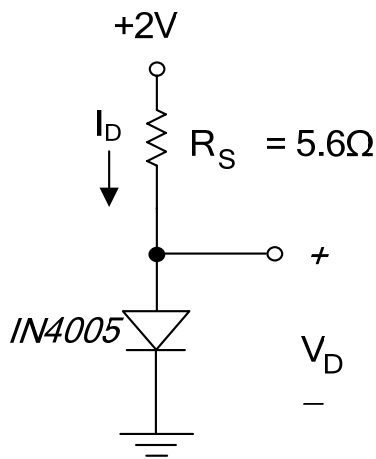


Fig. 1

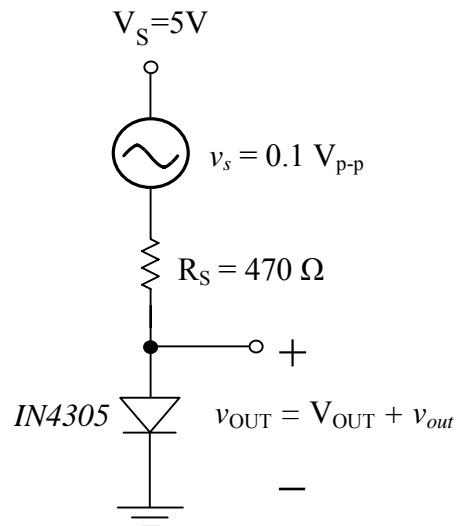


Fig. 2

2. Determine the AC component of the output voltage, v_{out} , for the circuit in Fig. 2 when $V_S = 5\text{V}$. The I-V characteristic of the IN4305 diode has the following voltage and current values:
 $V_{D1} = 0.50\text{V}$ at $I_{D1} = 250\mu\text{A}$
 $V_{D2} = 0.70\text{V}$ at $I_{D2} = 10\text{mA}$

3. Find the Q-points (I_D , V_D) of the diodes in the circuits of Fig. 3. Using the simple model for forward biased diode, the diode voltage is given as 0.75V.

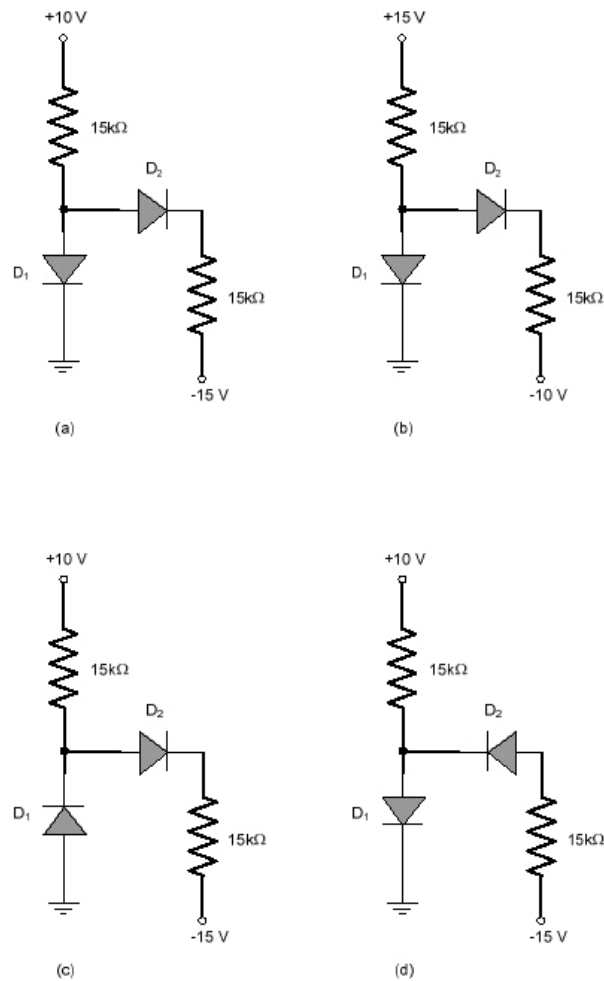


Fig. 3

Answers to Tutorial 4

- 1(a) The empirical junction equation for the IN4005 diode is

$$I_D \approx (1.90\text{nA})e^{\frac{V_D}{(42.8\text{mV})}} \quad \text{or} \quad V_D \approx (42.8\text{mV})\ln\left[\frac{I_D}{1.90\text{nA}}\right]$$

- 1(b) (i) For $I_D=20\text{ mA}$, $V_D=0.692\text{ V}$
(ii) For $I_D=300\text{ mA}$, $V_D=0.808\text{ V}$

- 1(c) $I_D = 215\text{ mA}$, $V_D=0.794\text{ V}$

2. $v_{out} = 1.24\text{ mV}_{P-P}$

	D_1	D_2
5(a)	0A, -2.13V	0.808mA, 0.75V
5(b)	0.283mA, 0.75V	0.667mA, 0.75V
5(c)	0.183mA, 0.75V	0.9mA, 0.75V
5(d)	0.617mA, 0.75V	0A, -15.75V