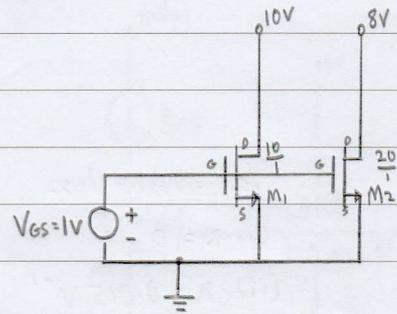


Esmund Lim

A.E Tutorial 9

i)

(i) $\lambda = 0$ (ii) $\lambda = 0.015 \text{ V}^{-1}$

$$I_D = \frac{k'n'}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2 (1 + \lambda V_{DS})$$

i) When $\lambda = 0$

$$I_{D1} = \frac{k'n'}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2$$

$$I_{D2} = \frac{k'n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2$$

$$\begin{aligned} \text{Since } V_{GS1} = V_{GS2} &= \frac{I_{D2}}{I_{D1}} \\ &= \frac{\frac{k'n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS} - V_{TN})^2}{\frac{k'n'}{2} \left(\frac{W}{L} \right)_1 (V_{GS} - V_{TN})^2} \\ &= \frac{\left(\frac{W}{L} \right)_2}{\left(\frac{W}{L} \right)_1} \\ &= \frac{20}{10} \\ &= 2 \end{aligned}$$

For the ideal case, when $\lambda = 0$, the drain current of a NMOS, I_D depends only on V_{GS} , V_{TN} , $k'n'$ and $\left(\frac{W}{L} \right)$ ratio. Of these, only V_{GS} and $\left(\frac{W}{L} \right)$ can be modified for different transistors while the other two are constant.

ii) When $\lambda \neq 0$

$$I_{D1} = \frac{k'n'}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1})$$


$$I_{D2} = \frac{k'n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2})$$

For the non-ideal case, when $\lambda \neq 0$, I_D also depends on V_{DS} and λ . Of these, only V_{DS} can be modified for different transistor but λ is a constant.

$$\begin{aligned} \frac{I_{D2}}{I_{D1}} &= \frac{\frac{k'n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2})}{\frac{k'n'}{2} \left(\frac{W}{L} \right)_1 (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1})} \\ &= \frac{\left(\frac{W}{L} \right)_2 (1 + \lambda V_{DS2})}{\left(\frac{W}{L} \right)_1 (1 + \lambda V_{DS1})} \\ &= \frac{20 (1 + 0.015 (8))}{10 (1 + 0.015 (10))} \\ &= 1.947826087 \\ &\approx 1.948 \end{aligned}$$

The ratio $\frac{I_{D2}}{I_{D1}}$ is independent of V_{GS} but the value of I_{D1} or I_{D2} itself is dependent on V_{GS} .

b)

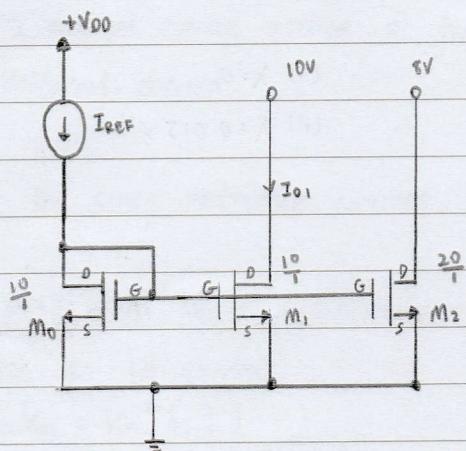

$$V_{GS0} = V_{GS1} = V_{GS2}$$

$$(i) \lambda = 0$$

$$(ii) \lambda = 0.015 \text{ V}^{-1}$$

same size

since there is no gate current in MOSFET, $I_{D1} = I_{REF}$

Also, all the transistors have the same V_{GS}

i) When $\lambda = 0$

$$\frac{I_{D1}}{I_{D0}} = \frac{k_p' \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2}{k_p' \left(\frac{W}{L}\right)_0 (V_{GS0} - V_{TN})^2}$$

$$= \frac{\left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2}{\left(\frac{W}{L}\right)_0 (V_{GS0} - V_{TN})^2}$$

$$= \frac{10}{10}$$

$$= 1$$


ii) When $\lambda \neq 0$

$$\frac{I_{D1}}{I_{D0}} = \frac{k_p' \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1})}{k_p' \left(\frac{W}{L}\right)_0 (V_{GS0} - V_{TN})^2 (1 + \lambda V_{DS0})}$$

$$= \frac{\left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})}{\left(\frac{W}{L}\right)_0 (1 + \lambda V_{DS0})}$$

$$= \frac{10 (1 + 0.015 (10))}{10 (1 + 0.015 (V_{GS}))}$$

2)

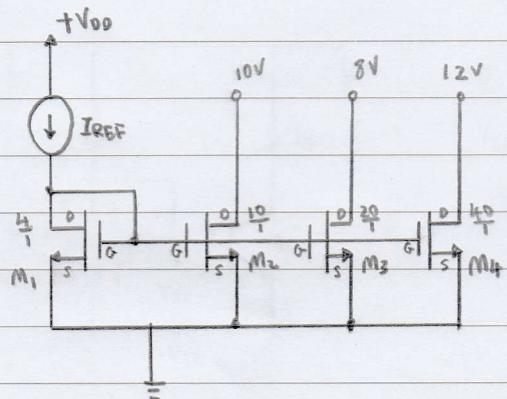

$$I_{REF} = 30 \mu A$$

$$k_n' = 25 \mu A/V^2$$

$$V_{TN} = 0.75 V$$

$$\lambda = 0.015 V^{-1}$$

Since there is no gate current in MOSFET, $I_D = I_{REF} = 30 \mu A$

All NMOS transistors have the same V_{GS}

For the diode connected transistors M_1 , $V_{DS1} = V_{GS}$

$$I_D = \frac{k_n'}{2} \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2 \quad * \text{Ignore } (1 + \lambda V_{DS1}) \text{ if not have to solve quadratic equation}$$

$$I_D \times \frac{2}{k_n'} \times \frac{L}{W} = (V_{GS} - V_{TN})^2$$

$$\sqrt{I_D \left(\frac{2}{k_n'} \right) \left(\frac{L}{W} \right)} = V_{GS} - V_{TN}$$

$$V_{GS} = \sqrt{I_D \left(\frac{2}{k_n'} \right) \left(\frac{L}{W} \right)} + V_{TN}$$

$$= \sqrt{30 \times 10^{-6} \left(\frac{2}{25 \times 10^{-6}} \right) \left(\frac{1}{4} \right)} + 0.75$$

$$= 1.524596669 V$$

$$\approx 1.52 V$$

$$\frac{I_{D2}}{I_{D1}} = \frac{k_n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS2} - V_{TN})^2 (1 + \lambda V_{DS2})$$

$$\frac{k_n'}{2} \left(\frac{W}{L} \right)_2 (V_{GS1} - V_{TN})^2 (1 + \lambda V_{DS1})$$

$$= \frac{10}{4} (1 + 0.015(10))$$

$$= 2.810911224$$

$$I_{D2} = 2.810911224 (30 \mu A)$$

$$= 84.32733672 \mu A$$

$$\approx 84.33 \mu A$$

$$r_{O2} = \frac{\left(\frac{1}{\lambda} + V_{DS2} \right)}{I_{D2}}$$

$$= \frac{\frac{1}{0.015} + 10}{84.33 \mu A}$$

$$= 909.126843 k\Omega$$

$$\approx 909 k\Omega$$

$$\frac{I_{D3}}{I_{D1}} = \left(\frac{W}{L}\right)_3 \left(1 + \lambda V_{DS3}\right)$$

$$\left(\frac{W}{L}\right)_1 \left(1 + \lambda V_{DS1}\right)$$

$$= \frac{20 (1 + 0.015(8))}{4 (1 + 0.015(1.52))}$$

$$= 5.47516621$$

$$I_{D3} = 5.47516621 (30\text{mA})$$

$$= 164.2549863\text{mA}$$

$$\approx 164\text{mA}$$

$$r_{o3} = \frac{\frac{1}{k} + V_{OS}}{I_{D3}}$$

$$= \frac{\frac{1}{0.015} + 8}{164\text{mA}}$$

$$= 454.5777778\text{k}\Omega$$

$$\approx 455\text{k}\Omega$$

$$\frac{I_{D4}}{I_{D1}} = \frac{40 (1 + 0.015(12))}{4 (1 + 0.015(1.52))}$$

$$= 11.53645737$$

$$I_{D4} = 11.53645737 \times 30\text{mA}$$

$$= 346.1087212\text{mA}$$


$$\approx 346\text{mA}$$

$$r_{o4} = \frac{\frac{1}{0.015} + 12}{346\text{mA}}$$

$$= 227.2888889\text{k}\Omega$$

$$\approx 227\text{k}\Omega$$

3a)

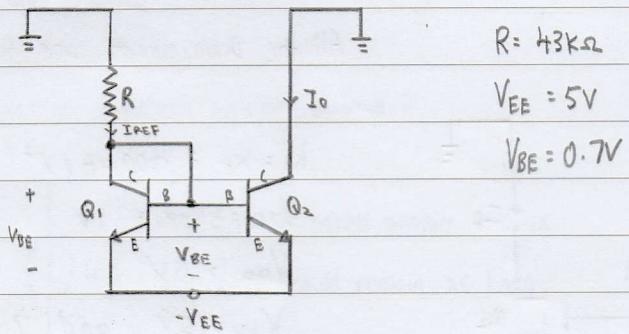

$$R = 43\text{k}\Omega$$

$$V_{EE} = 5\text{V} \text{ and } 7.5\text{V}$$

$$V_{BE} = 0.7\text{V}$$

* If it is a good constant current source
→ change in voltage source should not have a big change in the current

Assume base current negligible and both transistors are identical

$$I_o = I_{REF}$$

$$\text{For } -V_{EE} = -5\text{V}$$

$$I_o = \frac{0 - (-V_{EE} + V_{BE})}{R}$$

$$= \frac{5 - 0.7}{43\text{k}\Omega}$$

$$= 100\text{nA}$$

$$\text{For } -V_{EE} = -7.5\text{V}$$

$$I_o = \frac{0 - (-V_{EE} + V_{BE})}{R}$$

$$= \frac{7.5 - 0.7}{43\text{k}\Omega}$$

$$= 158.1395349 \times 10^{-6}$$


$$\approx 158\text{nA}$$

The change in the current is linearly related to the change in power supply

$$0 + V_{CE} - V_{EE} + I_o R_{REF}$$

$$I_o R = \frac{V_{EE} - V_{BE}}{R}$$

b)

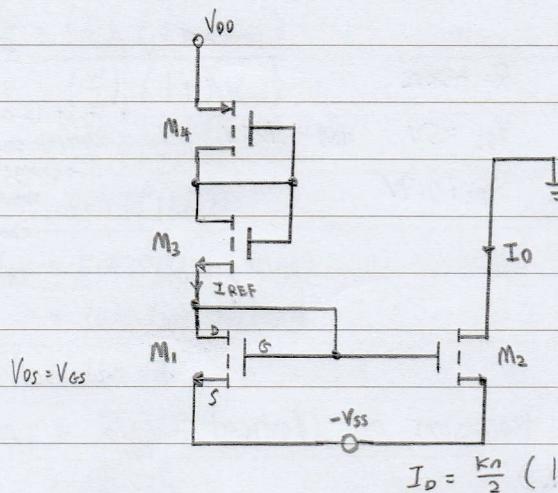

All the Drain current are the same

$$k_n = k_p = 400 \mu A/V^2$$

$$V_{TN} = -V_{TP} = 1V$$

$$V_{DD} = 0V$$

$$V_{SS} = 5V \text{ and } 7.5V$$

$$I_D = \frac{k_n}{2} (|V_{GS}| - |V_T|)^2$$

Assume all NMOS transistors are identical

$$|I_{D1}| = |I_{D3}| = |I_{D4}| = |I_{REF}|$$

$$\therefore |V_{GS1}| = |V_{GS3}| = |V_{GS4}| = |V_{GS}|$$

$$|V_{GS1}| + |V_{GS3}| + |V_{GS4}| = V_{DD} - (-V_{SS})$$

$$3|V_{GS}| = V_{DD} + V_{SS}$$

$$|V_{GS}| = \frac{V_{DD} + V_{SS}}{3}$$

$$= \frac{0+5}{3}$$

$$= 1.667V$$

Hence

$$I_{D2} = I_{D1} = \frac{400 \mu A}{2} (1.667 - 1)^2$$

$$= 88.9778 \times 10^{-6} A$$

$$\approx 89 \mu A$$

For $V_{DD} = 0V$ and $V_{SS} = -7.5V$

$$|V_{GS}| = \frac{0 + 7.5}{3}$$

$$= 2.5V$$

$$I_{D2} = I_{D1} = \frac{400 \mu A}{2} (2.5 - 1)^2$$

$$= 450 \mu A$$


not a good implementation

Note that the variation of current in this case is related to the square of change in supply voltage due to the square law relationship of I_D and $|V_{GS}|$ of MOSFET



Concept for this tutorial

current mirror
deal with ratio

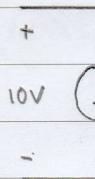→ How to build a constant current source?




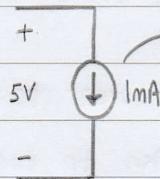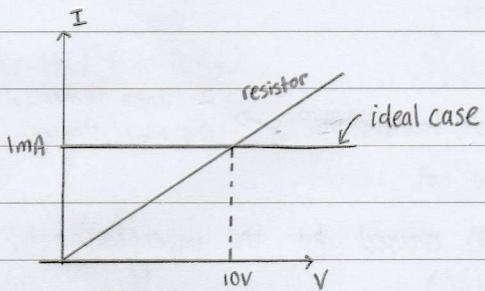When I put it across another voltage
source it should remain as 1mA




How to implement this using component I already know
by resistor?

- not a good design

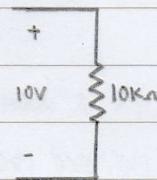

→ When the voltage fluctuate, current also fluctuate

BJT

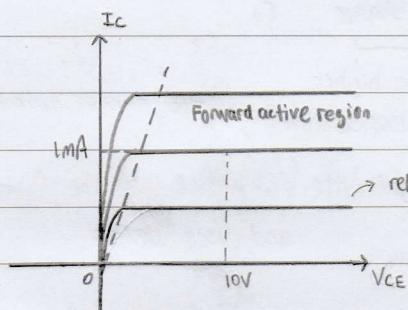


→ relatively flat, doesn't change with respect to voltage that much

∴ change in voltage, current change very little

→ better implementation of a constant current source

as compare to a resistor

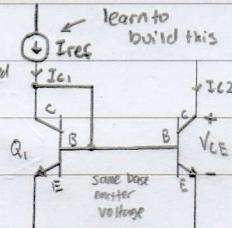by making it diode connected
it is unconditionally in
forward active region



→ make it diode connected

I_{ref} → part of it will go base → base current very small


and part of it will go

collector

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \left(1 + \frac{V_{CE}}{V_A}\right)$$

ideal case $V_A = \infty$

MOSFET

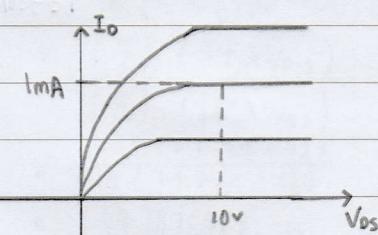

Use this
to control
current
across
another
terminal


Current mirror?

→ If everything equal, $I_S, V_{BE}, V_T, V_{CE}, V_A$

$$I_{C1} = I_{C2}$$

but this will be
slightly different

will study
the
infection

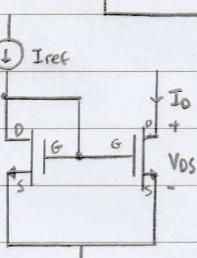

$$I_D = \frac{k_n}{2} (V_{DS} - V_{TN})^2 (1 + \lambda V_{DS})$$

$k_n = k_n' (\frac{W}{L})$

ideal case
 $R_L = 0$

Saturation: $V_{DS} \geq V_{GS} - V_{TN}$

* V_A , λ } cause the
BJT MOSFET } graph to have
slope → depend on V_{DS}

If you need 2 constant current source at two different branch with different terminal voltage and different current

Can I use the same reference current to control it? Yes

How? \rightarrow Don't want to be exact copy but larger / smaller

\rightarrow Use k_n to control

$$k_n = k_n' \left(\frac{W}{L} \right)$$

size of transistor \rightarrow 2 times larger, current also 2 time larger
0.5 times smaller, current also 0.5 time smaller

Slope mentioned before that was caused by the imperfection, λ , V_A



Slope is the ac resistance r_o

must be higher

to be less sensitive \rightarrow better constant current source

the higher the resistance = the flatter the slope is
and vice versa