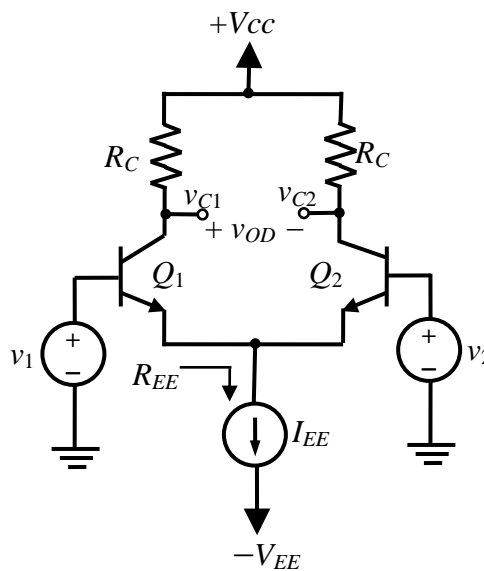



**Nanyang Technological University**  
**School of Electrical & Electronic Engineering**  
**E2002 Analog Electronics – Tutorial 8**

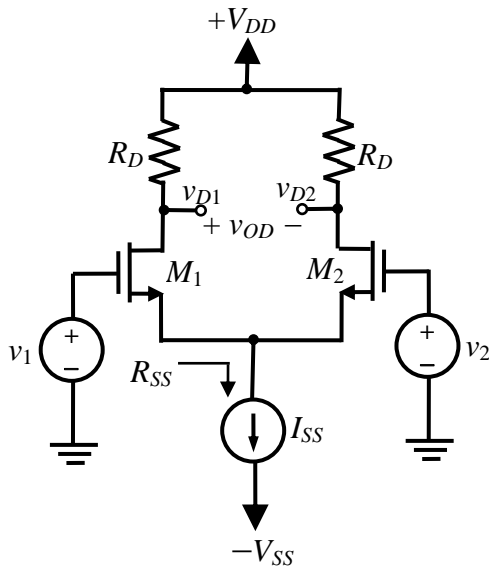1. (a) What are the Q-points for the transistors in the amplifier in Figure 2 if  $V_{CC} = V_{EE} = 12\text{ V}$ ,  $\beta = 100$ ,  $I_{EE} = 400\mu\text{A}$ ,  $R_{EE} = 200\text{ k}\Omega$ , and  $R_C = 39\text{ k}\Omega$ ,  $V_A = \infty$ ?  
 (Ans:  $198\mu\text{A}$ ,  $4.98\text{ V}$ )
- (b) What are the differential-mode and common-mode gains, common-mode rejection ratios (CMRRs) and output resistances for the cases of differential and single-ended outputs, respectively? What are the differential-mode and common-mode input resistances?  
 (Ans: differential output:  $-309$ ,  $0$ ,  $\infty$ ,  $78.0\text{ k}\Omega$ ; single-ended output:  $-154.5$ ,  $-0.0965$ ,  $64.1\text{ dB}$ ,  $38\text{ k}\Omega$ ;  $25.2\text{ k}\Omega$ ,  $20.2\text{ M}\Omega$ )

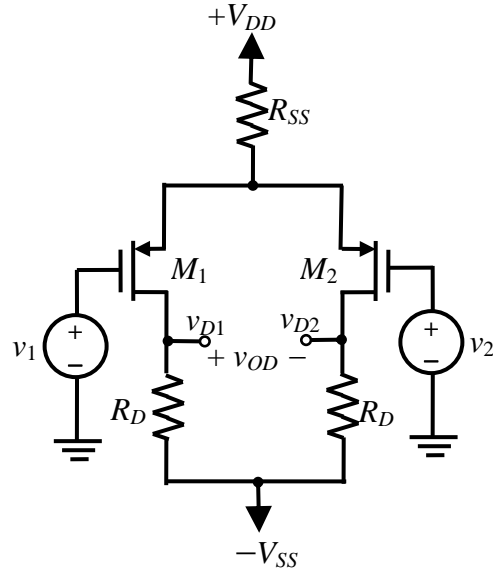


**Figure 1**

2. (a) What are the Q-points for the transistors in the amplifier in Figure 2 if  $V_{DD} = V_{SS} = 15\text{ V}$ ,  $I_{SS} = 300\mu\text{A}$ ,  $R_{SS} = 160\text{ k}\Omega$  and  $R_D = 75\text{ k}\Omega$ ? Assume that  $K_n = 400\mu\text{A/V}^2$  and  $V_{TN} = 1\text{ V}$ .  
 (Ans:  $150\mu\text{A}$ ,  $5.62\text{ V}$ )
- (b) What are the differential-mode and common-mode gains, common-mode rejection ratios (CMRRs) and output resistances for the cases of single-ended and differential outputs, respectively? What are the differential-mode and common-mode input resistances?  
 (Ans: differential output:  $-26$ ,  $0$ ,  $\infty$ ,  $150\text{ k}\Omega$ ; single-ended output:  $-13$ ,  $-0.0232$ ,  $35\text{ dB}$ ,  $75\text{ k}\Omega$ ;  $\infty$ ,  $\infty$ )



**Figure 2**



**Figure 3**

3. (a) What are the Q-points for the transistors in the amplifier in the Figure 3 if  $V_{DD} = V_{SS} = 18 \text{ V}$ ,  $R_{SS} = 56 \text{ k}\Omega$  and  $R_D = 91 \text{ k}\Omega$ ? Assume that  $K_p = 200 \mu\text{A}/\text{V}^2$  and  $V_{TP} = -1 \text{ V}$ .  
Ans: (142  $\mu\text{A}$ , 7.27 V)

(b) What are the differential-mode and common-mode gains, common-mode rejection ratios (CMRRs) and output resistances for the cases of single-ended and differential outputs, respectively? What are the differential-mode and common-mode input resistances?

Ans: (differential output: -21.57, 0,  $\infty$ , 182 k $\Omega$ ; single-ended output: -10.78, -0.78, 22.81 dB, 91 k $\Omega$ ;  $\infty$ ,  $\infty$ )