

Nanyang Technological University
School of Electrical & Electronic Engineering
E2002 Analog Electronics – Tutorial 6

1. The DC operating point of the common-emitter amplifier in Figure 1 has been calculated in Question 3 of Tutorial 5 to be $I_C = 50 \mu A$ and $V_{EC} = 10.86 V$. The pnp transistor Q_1 has $\beta = 100$ and $V_A = 75V$. Assume that the capacitors have infinite value, what are the voltage gain, input resistance, output resistance and current gain if $V_{CC} = V_{EE} = 15 V$, $R_I = 750 \Omega$, $R_1 = R_2 = 200 k\Omega$, $R_L = 100 k\Omega$, $R_C = 100 k\Omega$, $R_{E1} = 30 k\Omega$ and $R_{E2} = 250 k\Omega$.

(Ans: $A_v = -1.62$, $R_{in} = 96.86 k\Omega$, $R_{out} = 100 k\Omega$, $A_i = -1.58$; For fully bypassed R_E : $A_v = -95.04$, $R_{in} = 33.33 k\Omega$, $R_{out} = 100 k\Omega$).

What is the amplitude of the largest ac signal that can appear at the output that satisfies the small-signal limit?

(Ans: 505.12 mV)

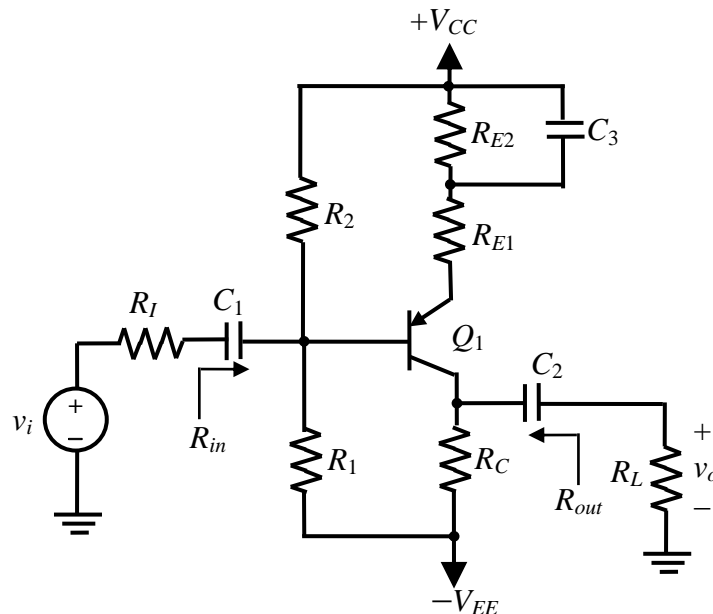


Figure 1

2. The DC operating point of the common-drain amplifier in Figure 2 has been calculated in Question 4 of Tutorial 5 to be $I_D = 1.87 mA$ and $V_{DS} = 9.39 V$. The n -MOS transistor M_1 has $K_n = 1 mA/V^2$, $V_{TN} = 1 V$ and $\lambda = 0.02 V^{-1}$. Assume that the capacitors have infinite value, $R_I = 100 \Omega$, $R_1 = 1.2 M\Omega$, $R_2 = 910 k\Omega$, $R_S = 3 k\Omega$, $R_L = 250 \Omega$ and $V_{DD} = 15 V$, calculate the voltage gain, input resistance and output resistance of the amplifier.

(Ans: $A_v = 0.31$, $R_{in} = 517.54 k\Omega$, $R_{out} = 434.6 \Omega$)

What is the maximum input signal amplitude for small signal operation?

(Ans: 556.52 mV)

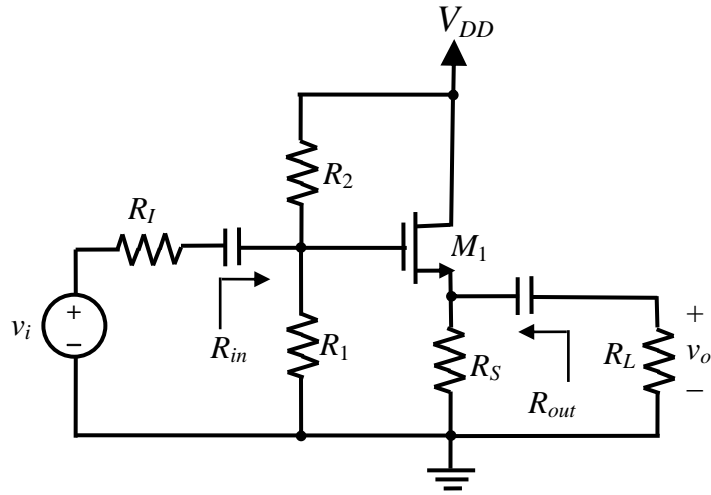


Figure 2

3. What are the voltage gain, input resistance and output resistance for the amplifier in Figure 3 if $R_I = 250\Omega$, $R_S = 68\text{ k}\Omega$, $R_L = 200\text{ k}\Omega$, $R_D = 43\text{ k}\Omega$ and $V_{DD} = V_{SS} = 15\text{ V}$? What is the maximum input signal for the amplifier that satisfies the small-signal limit? Use $K_p = 200\text{ }\mu\text{A/V}^2$ and $V_{TP} = -1\text{ V}$ for your calculation.
(Ans: $A_v = 8.98$, $R_{in} = 3.47\text{ k}\Omega$, $R_{out} = 43\text{ k}\Omega$, $v_i \leq 0.292\text{ V}$)

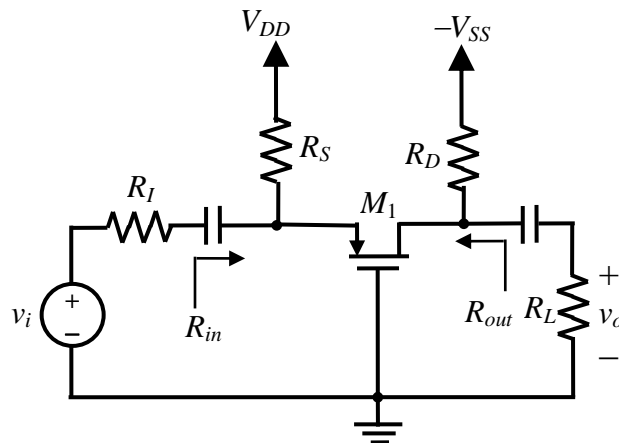


Figure 3