

TUTORIAL 3 (with answers at the back)

1.a) The op-amp in Fig. T 3.1 has a unity-gain frequency of 1.2MHz.

- i) What is the closed loop BW?
- ii) What is the closed-loop gain at 600kHz ?

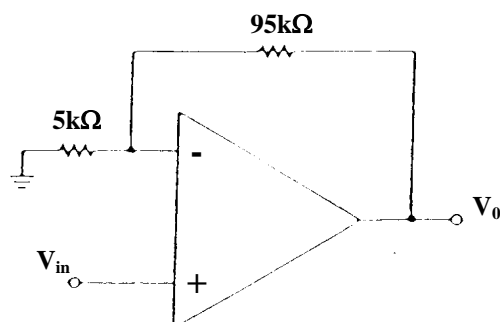


Fig. T3-1

1.b) The op-amp shown in Fig. T3-2 has a SR of 4 V/μS and a unity-gain frequency of 2MHz. Determine whether the amplifier will distort the input signal shown.

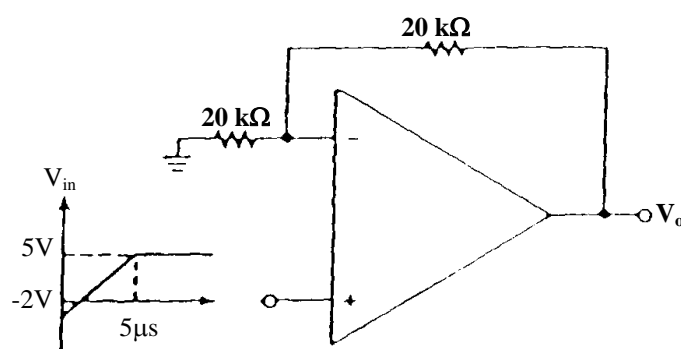


Fig. T3-2

2. The op-amp in Fig T3-3 has a slew rate of 0.50V/μS. The amplifier must be capable of amplifying the following input signals:

$$v_1 = 0.01\sin(10^6 t)$$

$$v_2 = 0.05\sin(350 \times 10^3 t)$$

$$v_3 = 0.10\sin(200 \times 10^3 t)$$

$$v_4 = 0.20\sin(50 \times 10^3 t)$$

- a) Determine whether the output will be distorted due to slew-rate limitations on any input.
- b) If so, find a remedy (other than changing the input signals).

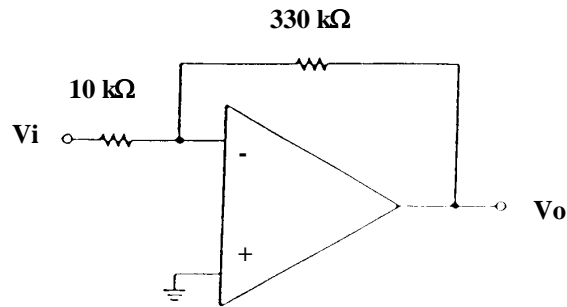


Fig. T3-3

- 3.a) What minimum SR is necessary for a unity-gain amplifier that must pass, without distortion, the input waveform shown in Fig T3-4.

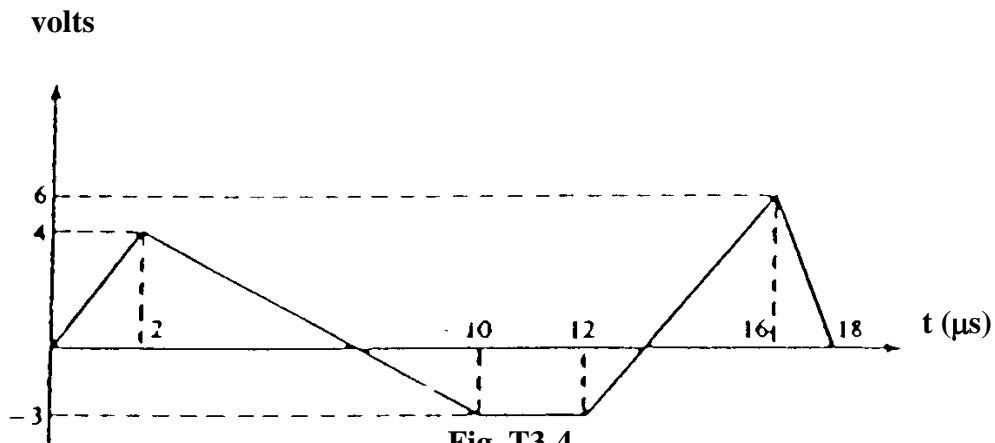


Fig. T3-4

- 3.b) Repeat (a), if the amplifier is in a noninverting configuration with $R_1=50\text{k}\Omega$ and $R_f=100\text{k}\Omega$.
4. In a certain application, a signal source having $60\text{k}\Omega$ of source resistance produces a 1-V-rms signal. The signal must be amplified to 2.5V rms and drive a $1\text{k}\Omega$ load. Assuming that the phase of the load voltage is of no concern, design an op-amp circuit for the application.

Answers to Tutorial 3

1. (a)
 - (i) $BW_{CL} = 60 \text{ kHz}$
 - (ii) $\frac{V_o}{V_{in}}(600\text{kHz}) = 2.0 \text{ V/V}$
- (b) No distortion will occur
2. (a) The output due to v_2 and v_3 will be distorted.
(b) There are only two remedies:
 - (i) find an amp with greater SR, a SR of at least $0.66 \text{ V}/\mu\text{s}$
 - (ii) reduce the A_{CL} of the present amplifier to 25 V/V .
3. (a) The minimum SR is $3.0 \text{ V}/\mu\text{s}$
(b) The $(SR)_{min} = 9 \text{ V}/\mu\text{s}$
4. Many right answers.